

EE101: BJT circuits (Part 1)




M. B. Patil


mbpatil@ee.iitb.ac.in

Department of Electrical Engineering
Indian Institute of Technology Bombay

BJT amplifier: basic operation

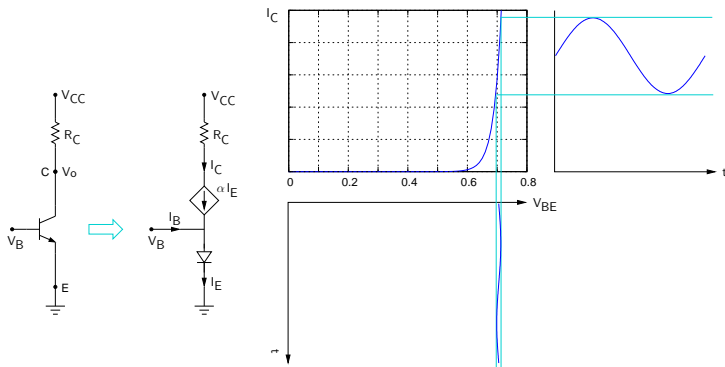


BJT amplifier: basic operation

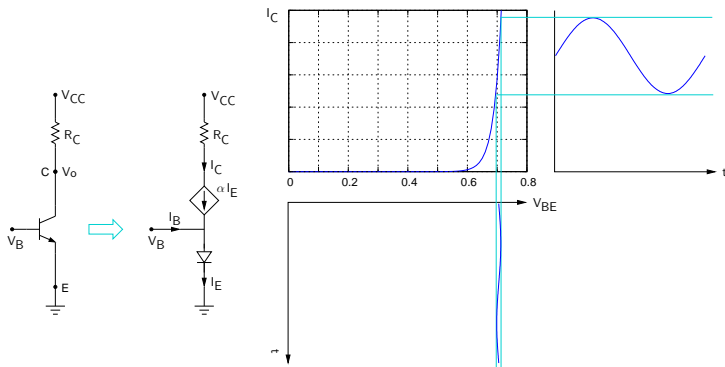


- * In the active mode, I_C changes exponentially with V_{BE} .

BJT amplifier: basic operation

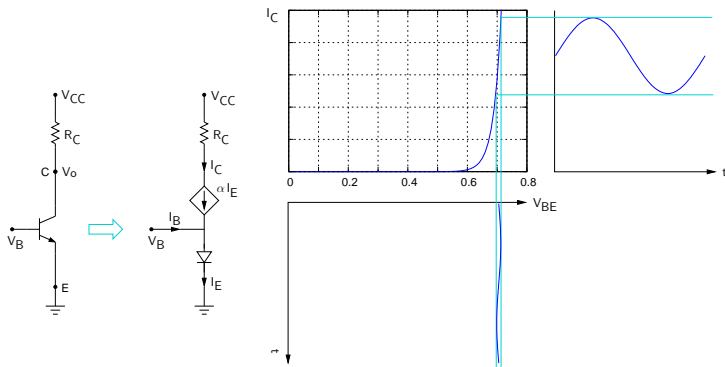


- * In the active mode, I_C changes exponentially with V_{BE} .
- * $V_o = V_{CC} - I_C R_C \Rightarrow$ the amplitude of V_o is simply $\hat{I}_C R_C$ which can be made much larger than the input amplitude.

BJT amplifier: basic operation

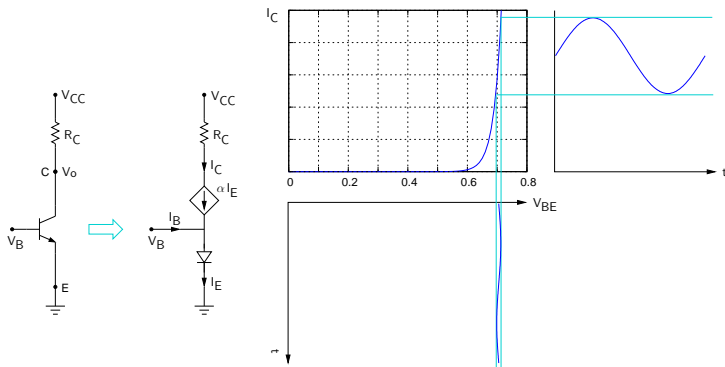


- * In the active mode, I_C changes exponentially with V_{BE} .
- * $V_o = V_{CC} - I_C R_C \Rightarrow$ the amplitude of V_o is simply $\hat{I}_C R_C$ which can be made much larger than the input amplitude.
- * Note that both the input (V_{BE}) and output (V_o) voltages have DC ("bias") components.

BJT amplifier biasing: why?

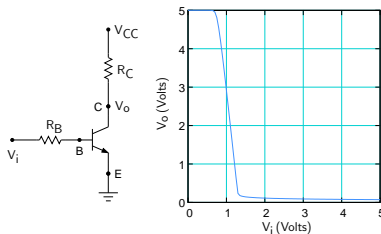

Consider a more realistic BJT amplifier circuit, with R_B added to limit the base current (and thus protect the transistor).


BJT amplifier biasing: why?

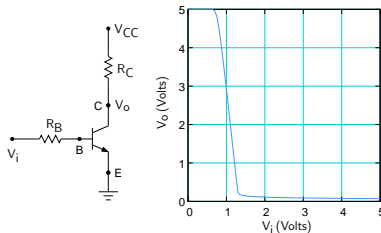

Consider a more realistic BJT amplifier circuit, with R_B added to limit the base current (and thus protect the transistor).

- * The gain of the amplifier is given by $\frac{dV_o}{dV_i}$.


BJT amplifier biasing: why?

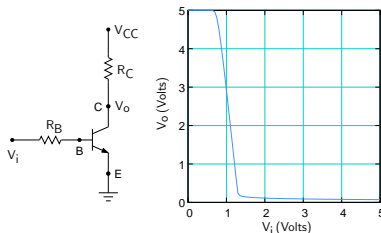

Consider a more realistic BJT amplifier circuit, with R_B added to limit the base current (and thus protect the transistor).

- * The gain of the amplifier is given by $\frac{dV_o}{dV_i}$.
- * Since V_o is nearly constant for $V_i < 0.7$ V (due to cut-off) and $V_i > 1.3$ V (due to saturation), the circuit will not work as an amplifier in this range.



BJT amplifier biasing: why?

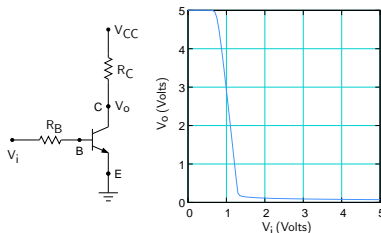

Consider a more realistic BJT amplifier circuit, with R_B added to limit the base current (and thus protect the transistor).


- * The gain of the amplifier is given by $\frac{dV_o}{dV_i}$.
- * Since V_o is nearly constant for $V_i < 0.7$ V (due to cut-off) and $V_i > 1.3$ V (due to saturation), the circuit will not work as an amplifier in this range.
- * Further, to get a large swing in V_o without distortion, the DC bias of V_i should be at the centre of the amplifying region, i.e., $V_i \approx 1$ V.

BJT amplifier biasing: why?

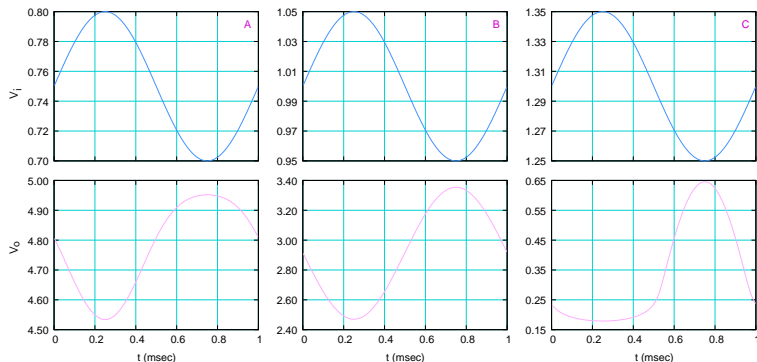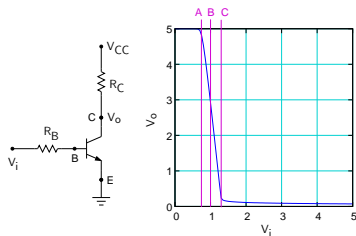


(SEQUEL file: ee101_bjt_amp1.sqproj)

BJT amplifier

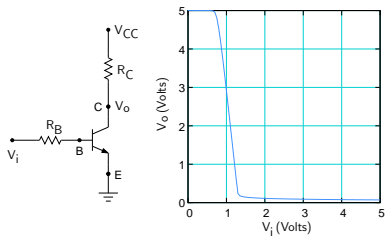


- * The key challenges in realizing this amplifier in practice are

BJT amplifier

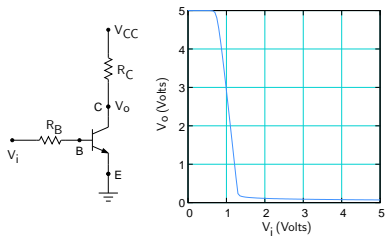


- * The key challenges in realizing this amplifier in practice are
 - adjusting the input DC bias to ensure that the BJT remains in the linear (active) region with a certain bias value of I_C .

BJT amplifier

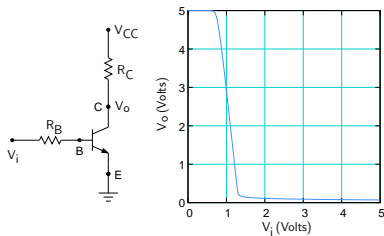


- * The key challenges in realizing this amplifier in practice are
 - adjusting the input DC bias to ensure that the BJT remains in the linear (active) region with a certain bias value of I_C .
 - mixing the input DC bias with the signal voltage.

BJT amplifier

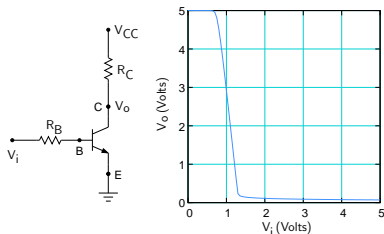


- * The key challenges in realizing this amplifier in practice are
 - adjusting the input DC bias to ensure that the BJT remains in the linear (active) region with a certain bias value of I_C .
 - mixing the input DC bias with the signal voltage.
- * The first issue is addressed by using a suitable biasing scheme, and the second by using “coupling” capacitors.

BJT amplifier: a simple biasing scheme

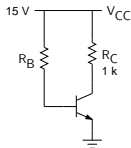

“Biasing” an amplifier \Rightarrow selection of component values for a certain DC value of I_C (i.e., when no signal is applied).


BJT amplifier: a simple biasing scheme

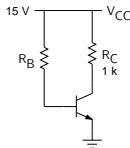

“Biasing” an amplifier \Rightarrow selection of component values for a certain DC value of I_C (i.e., when no signal is applied).

Equivalently, we may bias an amplifier for a certain DC value of V_{CE} , since I_C and V_{CE} are related: $V_{CE} + I_C R_C = V_{CC}$.

BJT amplifier: a simple biasing scheme

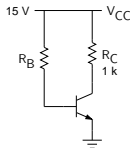


“Biasing” an amplifier \Rightarrow selection of component values for a certain DC value of I_C (i.e., when no signal is applied).

Equivalently, we may bias an amplifier for a certain DC value of V_{CE} , since I_C and V_{CE} are related: $V_{CE} + I_C R_C = V_{CC}$.

As an example, for $R_C = 1\text{ k}$, $\beta = 100$, let us calculate R_B which will give $I_C = 3.3\text{ mA}$, assuming the BJT to be operating in the active mode.

BJT amplifier: a simple biasing scheme

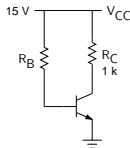


“Biasing” an amplifier \Rightarrow selection of component values for a certain DC value of I_C (i.e., when no signal is applied).

Equivalently, we may bias an amplifier for a certain DC value of V_{CE} , since I_C and V_{CE} are related: $V_{CE} + I_C R_C = V_{CC}$.

As an example, for $R_C = 1\text{ k}\Omega$, $\beta = 100$, let us calculate R_B which will give $I_C = 3.3\text{ mA}$, assuming the BJT to be operating in the active mode.

$$I_B = \frac{I_C}{\beta} = \frac{3.3\text{ mA}}{100} = 33\text{ }\mu\text{A} = \frac{V_{CC} - V_{BE}}{R_B}$$

BJT amplifier: a simple biasing scheme

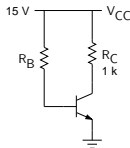

“Biasing” an amplifier \Rightarrow selection of component values for a certain DC value of I_C (i.e., when no signal is applied).


Equivalently, we may bias an amplifier for a certain DC value of V_{CE} , since I_C and V_{CE} are related: $V_{CE} + I_C R_C = V_{CC}$.

As an example, for $R_C = 1\text{ k}\Omega$, $\beta = 100$, let us calculate R_B which will give $I_C = 3.3\text{ mA}$, assuming the BJT to be operating in the active mode.

$$I_B = \frac{I_C}{\beta} = \frac{3.3\text{ mA}}{100} = 33\text{ }\mu\text{A} = \frac{V_{CC} - V_{BE}}{R_B}$$


$$\rightarrow R_B = \frac{14.3\text{ V}}{33\text{ }\mu\text{A}} = 430\text{ k}\Omega.$$

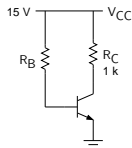BJT amplifier: a simple biasing scheme (continued)



With $R_B = 430 \text{ k}$, we expect $I_C = 3.3 \text{ mA}$, assuming $\beta = 100$.

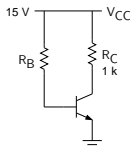
BJT amplifier: a simple biasing scheme (continued)



With $R_B = 430 \text{ k}$, we expect $I_C = 3.3 \text{ mA}$, assuming $\beta = 100$.

However, in practice, there is a substantial variation in the β value (even for the same transistor type). The manufacturer may specify the nominal value of β as 100, but the actual value may be 150, for example.

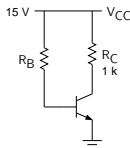BJT amplifier: a simple biasing scheme (continued)



With $R_B = 430\text{ k}$, we expect $I_C = 3.3\text{ mA}$, assuming $\beta = 100$.


However, in practice, there is a substantial variation in the β value (even for the same transistor type). The manufacturer may specify the nominal value of β as 100, but the actual value may be 150, for example.

With $\beta = 150$, the actual I_C is,

$$I_C = \beta \times \frac{V_{CC} - V_{BE}}{R_B} = 150 \times \frac{(15 - 0.7)\text{ V}}{430\text{ k}} = 5\text{ mA},$$

which is significantly different than the intended value, 3.3 mA.

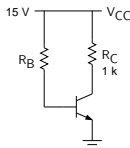BJT amplifier: a simple biasing scheme (continued)



With $R_B = 430 \text{ k}$, we expect $I_C = 3.3 \text{ mA}$, assuming $\beta = 100$.

However, in practice, there is a substantial variation in the β value (even for the same transistor type). The manufacturer may specify the nominal value of β as 100, but the actual value may be 150, for example.


With $\beta = 150$, the actual I_C is,

$$I_C = \beta \times \frac{V_{CC} - V_{BE}}{R_B} = 150 \times \frac{(15 - 0.7) \text{ V}}{430 \text{ k}} = 5 \text{ mA},$$


which is significantly different than the intended value, 3.3 mA.

\Rightarrow need a biasing scheme which is not so sensitive to β .


BJT amplifier: improved biasing scheme

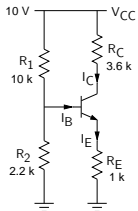


BJT amplifier: improved biasing scheme

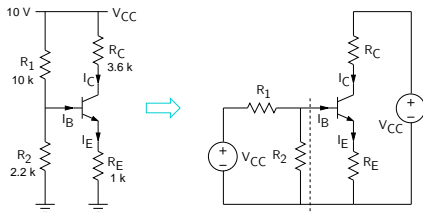

BJT amplifier: improved biasing scheme

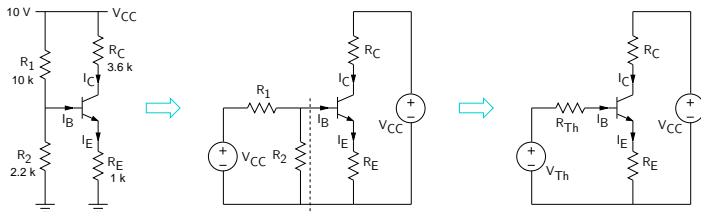


BJT amplifier: improved biasing scheme

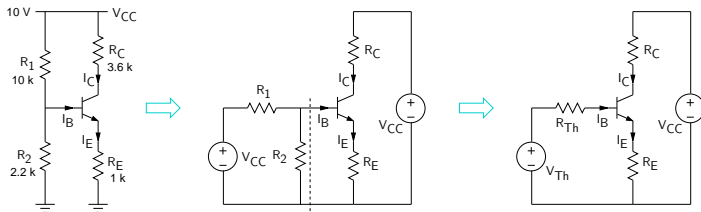

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2\text{ k}}{10\text{ k} + 2.2\text{ k}} \times 10\text{ V} = 1.8\text{ V}, \quad R_{Th} = R_1 \parallel R_2 = 1.8\text{ k}$$

BJT amplifier: improved biasing scheme

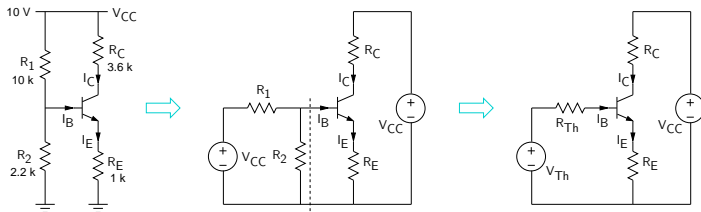


$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2\text{ k}}{10\text{ k} + 2.2\text{ k}} \times 10\text{ V} = 1.8\text{ V}, \quad R_{Th} = R_1 \parallel R_2 = 1.8\text{ k}$$

Assuming the BJT to be in the active mode,

$$\text{KCL: } V_{Th} = R_{Th} I_B + V_{BE} + R_E I_E = R_{Th} I_B + V_{BE} + (\beta + 1) I_B R_E$$

BJT amplifier: improved biasing scheme

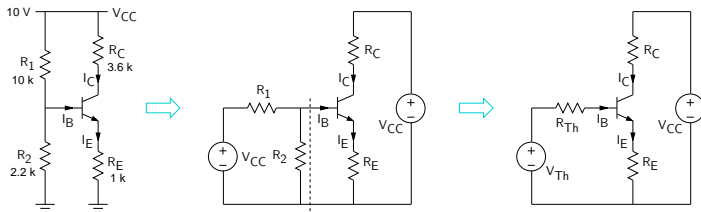


$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2\text{ k}}{10\text{ k} + 2.2\text{ k}} \times 10\text{ V} = 1.8\text{ V}, \quad R_{Th} = R_1 \parallel R_2 = 1.8\text{ k}$$

Assuming the BJT to be in the active mode,

$$\text{KCL: } V_{Th} = R_{Th} I_B + V_{BE} + R_E I_E = R_{Th} I_B + V_{BE} + (\beta + 1) I_B R_E$$

$$\rightarrow I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}, \quad I_C = \beta I_B = \frac{\beta (V_{Th} - V_{BE})}{R_{Th} + (\beta + 1) R_E}.$$

BJT amplifier: improved biasing scheme

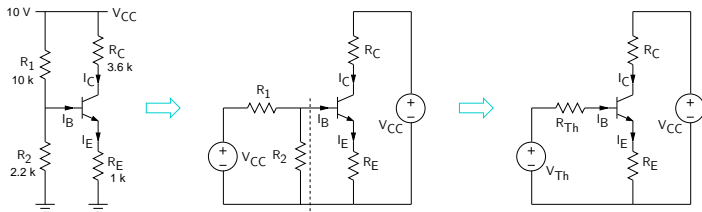

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2\text{ k}}{10\text{ k} + 2.2\text{ k}} \times 10\text{ V} = 1.8\text{ V}, \quad R_{Th} = R_1 \parallel R_2 = 1.8\text{ k}$$


Assuming the BJT to be in the active mode,

$$\text{KCL: } V_{Th} = R_{Th} I_B + V_{BE} + R_E I_E = R_{Th} I_B + V_{BE} + (\beta + 1) I_B R_E$$

$$\rightarrow I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}, \quad I_C = \beta I_B = \frac{\beta (V_{Th} - V_{BE})}{R_{Th} + (\beta + 1) R_E}.$$

For $\beta = 100$, $I_C = 1.07\text{ mA}$.

BJT amplifier: improved biasing scheme

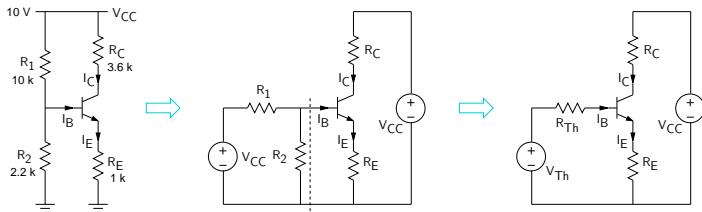

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2\text{ k}}{10\text{ k} + 2.2\text{ k}} \times 10\text{ V} = 1.8\text{ V}, \quad R_{Th} = R_1 \parallel R_2 = 1.8\text{ k}$$

Assuming the BJT to be in the active mode,


$$\text{KCL: } V_{Th} = R_{Th} I_B + V_{BE} + R_E I_E = R_{Th} I_B + V_{BE} + (\beta + 1) I_B R_E$$

$$\rightarrow I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}, \quad I_C = \beta I_B = \frac{\beta (V_{Th} - V_{BE})}{R_{Th} + (\beta + 1) R_E}.$$

For $\beta = 100$, $I_C = 1.07\text{ mA}$.


For $\beta = 200$, $I_C = 1.085\text{ mA}$.

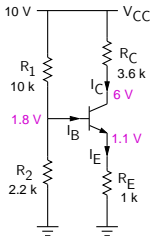BJT amplifier: improved biasing scheme (continued)



With $I_C = 1.1\text{ mA}$, the various DC (“bias”) voltages are,

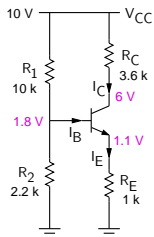
BJT amplifier: improved biasing scheme (continued)



With $I_C = 1.1\text{ mA}$, the various DC (“bias”) voltages are,

$$V_E = I_E R_E \approx 1.1\text{ mA} \times 1\text{ k} = 1.1\text{ V},$$

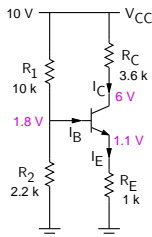BJT amplifier: improved biasing scheme (continued)




With $I_C = 1.1\text{ mA}$, the various DC (“bias”) voltages are,

$$V_E = I_E R_E \approx 1.1\text{ mA} \times 1\text{ k} = 1.1\text{ V},$$

$$V_B = V_E + V_{BE} \approx 1.1\text{ V} + 0.7\text{ V} = 1.8\text{ V},$$

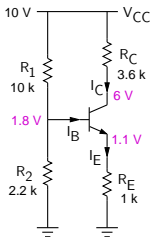BJT amplifier: improved biasing scheme (continued)




With $I_C = 1.1$ mA, the various DC (“bias”) voltages are,

$$V_E = I_E R_E \approx 1.1 \text{ mA} \times 1 \text{ k} = 1.1 \text{ V},$$

$$V_B = V_E + V_{BE} \approx 1.1 \text{ V} + 0.7 \text{ V} = 1.8 \text{ V},$$

$$V_C = V_{CC} - I_C R_C = 10 \text{ V} - 1.1 \text{ mA} \times 3.6 \text{ k} \approx 6 \text{ V},$$

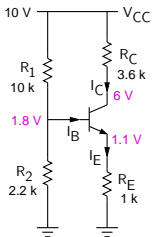BJT amplifier: improved biasing scheme (continued)



With $I_C = 1.1$ mA, the various DC (“bias”) voltages are,


$$V_E = I_E R_E \approx 1.1 \text{ mA} \times 1 \text{ k} = 1.1 \text{ V},$$

$$V_B = V_E + V_{BE} \approx 1.1 \text{ V} + 0.7 \text{ V} = 1.8 \text{ V},$$

$$V_C = V_{CC} - I_C R_C = 10 \text{ V} - 1.1 \text{ mA} \times 3.6 \text{ k} \approx 6 \text{ V},$$


$$V_{CE} = V_C - V_E = 6 - 1.1 = 4.9 \text{ V}.$$

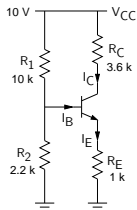BJT amplifier: improved biasing scheme (continued)



A quick estimate of the bias values can be obtained by ignoring I_B (which is fair if β is large). In that case,

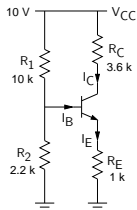
BJT amplifier: improved biasing scheme (continued)



A quick estimate of the bias values can be obtained by ignoring I_B (which is fair if β is large). In that case,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2 \text{ k}}{10 \text{ k} + 2.2 \text{ k}} \times 10 \text{ V} = 1.8 \text{ V}.$$

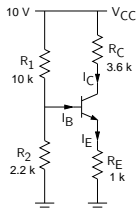BJT amplifier: improved biasing scheme (continued)




A quick estimate of the bias values can be obtained by ignoring I_B (which is fair if β is large). In that case,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2 \text{ k}}{10 \text{ k} + 2.2 \text{ k}} \times 10 \text{ V} = 1.8 \text{ V}.$$

$$V_E = V_B - V_{BE} \approx 1.8 \text{ V} - 0.7 \text{ V} = 1.1 \text{ V}.$$

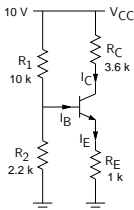BJT amplifier: improved biasing scheme (continued)




A quick estimate of the bias values can be obtained by ignoring I_B (which is fair if β is large). In that case,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2 \text{ k}}{10 \text{ k} + 2.2 \text{ k}} \times 10 \text{ V} = 1.8 \text{ V}.$$

$$V_E = V_B - V_{BE} \approx 1.8 \text{ V} - 0.7 \text{ V} = 1.1 \text{ V}.$$

$$I_E = \frac{V_E}{R_E} = \frac{1.1 \text{ V}}{1 \text{ k}} = 1.1 \text{ mA}.$$

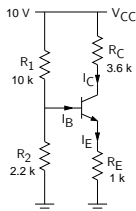BJT amplifier: improved biasing scheme (continued)



A quick estimate of the bias values can be obtained by ignoring I_B (which is fair if β is large). In that case,


$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2 \text{ k}}{10 \text{ k} + 2.2 \text{ k}} \times 10 \text{ V} = 1.8 \text{ V}.$$

$$V_E = V_B - V_{BE} \approx 1.8 \text{ V} - 0.7 \text{ V} = 1.1 \text{ V}.$$

$$I_E = \frac{V_E}{R_E} = \frac{1.1 \text{ V}}{1 \text{ k}} = 1.1 \text{ mA}.$$

$$I_C = \alpha I_E \approx I_E = 1.1 \text{ mA}.$$

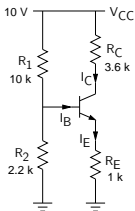BJT amplifier: improved biasing scheme (continued)



A quick estimate of the bias values can be obtained by ignoring I_B (which is fair if β is large). In that case,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2\text{ k}}{10\text{ k} + 2.2\text{ k}} \times 10\text{ V} = 1.8\text{ V}.$$


$$V_E = V_B - V_{BE} \approx 1.8\text{ V} - 0.7\text{ V} = 1.1\text{ V}.$$

$$I_E = \frac{V_E}{R_E} = \frac{1.1\text{ V}}{1\text{ k}} = 1.1\text{ mA}.$$


$$I_C = \alpha I_E \approx I_E = 1.1\text{ mA}.$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 10\text{ V} - (3.6\text{ k} \times 1.1\text{ mA}) - (1\text{ k} \times 1.1\text{ mA}) \approx 5\text{ V}.$$

Adding signal to bias

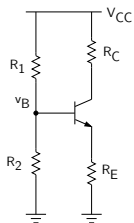


Adding signal to bias

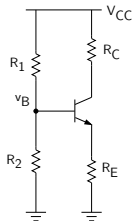


- * As we have seen earlier, the input signal $v_s(t) = \hat{V} \sin \omega t$ (for example) needs to be mixed with the desired bias value V_B so that the net voltage at the base is $v_B(t) = V_B + \hat{V} \sin \omega t$.

Adding signal to bias

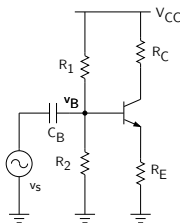


- * As we have seen earlier, the input signal $v_s(t) = \hat{V} \sin \omega t$ (for example) needs to be mixed with the desired bias value V_B so that the net voltage at the base is $v_B(t) = V_B + \hat{V} \sin \omega t$.
- * This can be achieved by using a coupling capacitor C_B .

Adding signal to bias

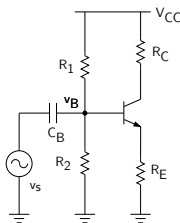

- * As we have seen earlier, the input signal $v_s(t) = \hat{V} \sin \omega t$ (for example) needs to be mixed with the desired bias value V_B so that the net voltage at the base is $v_B(t) = V_B + \hat{V} \sin \omega t$.
- * This can be achieved by using a coupling capacitor C_B .
- * Let us take a simple circuit to illustrate how a coupling capacitor works.


Coupling capacitor: example

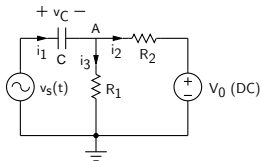

Let v_A be the instantaneous node voltage at A. KCL gives,

$$-i_1 + i_3 + i_2 = 0 \rightarrow -C \frac{dv_C}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0.$$

Coupling capacitor: example

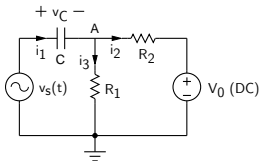


Let v_A be the instantaneous node voltage at A. KCL gives,

$$-i_1 + i_3 + i_2 = 0 \rightarrow -C \frac{dv_C}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0.$$

$$-C \frac{d(v_s - v_A)}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0. \quad (1)$$

Coupling capacitor: example

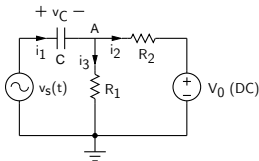


Let v_A be the instantaneous node voltage at A. KCL gives,

$$-i_1 + i_3 + i_2 = 0 \rightarrow -C \frac{dv_C}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0.$$

$$-C \frac{d(v_s - v_A)}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0. \quad (1)$$

Let $v_A = V_A + v_a(t)$, where $V_A = \text{constant (DC)}$.

Coupling capacitor: example

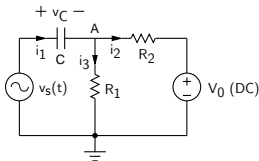

Let v_A be the instantaneous node voltage at A. KCL gives,


$$-i_1 + i_3 + i_2 = 0 \rightarrow -C \frac{dv_C}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0.$$

$$-C \frac{d(v_s - v_A)}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0. \quad (1)$$

Let $v_A = V_A + v_a(t)$, where $V_A = \text{constant (DC)}$.

Since Eq. (1) is valid at all times, the DC and time-dependent components of the equation can be separately written:

Coupling capacitor: example

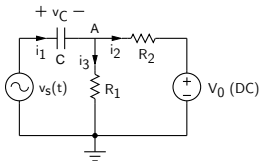

Let v_A be the instantaneous node voltage at A. KCL gives,

$$-i_1 + i_3 + i_2 = 0 \rightarrow -C \frac{dv_C}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0.$$


$$-C \frac{d(v_s - v_A)}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0. \quad (1)$$

Let $v_A = V_A + v_a(t)$, where $V_A = \text{constant (DC)}$.

Since Eq. (1) is valid at all times, the DC and time-dependent components of the equation can be separately written:

$$-C \frac{d(v_s - v_a)}{dt} + \frac{v_a}{R_1} + \frac{v_a}{R_2} = 0, \text{ and}$$

Coupling capacitor: example

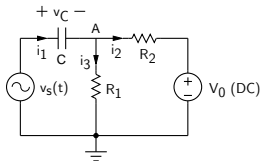

Let v_A be the instantaneous node voltage at A. KCL gives,

$$-i_1 + i_3 + i_2 = 0 \rightarrow -C \frac{dv_C}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0.$$

$$-C \frac{d(v_s - v_A)}{dt} + \frac{v_A}{R_1} + \frac{v_A - V_0}{R_2} = 0. \quad (1)$$


Let $v_A = V_A + v_a(t)$, where $V_A = \text{constant (DC)}$.

Since Eq. (1) is valid at all times, the DC and time-dependent components of the equation can be separately written:

$$-C \frac{d(v_s - v_a)}{dt} + \frac{v_a}{R_1} + \frac{v_a}{R_2} = 0, \text{ and}$$

$$-C \frac{d(-V_A)}{dt} + \frac{V_A}{R_1} + \frac{V_A - V_0}{R_2} = 0.$$

Coupling capacitor: example (continued)

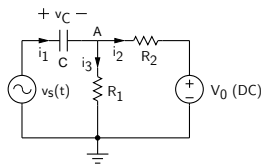


Since $\frac{dV_A}{dt} = 0$ (V_A being constant), we get

$$\frac{V_A}{R_1} + \frac{V_A - V_0}{R_2} = 0, \text{ and}$$

$$v_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = C \frac{d(v_s - v_a)}{dt}.$$

Coupling capacitor: example (continued)

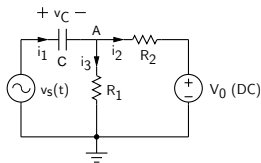


Since $\frac{dV_A}{dt} = 0$ (V_A being constant), we get


$$\frac{V_A}{R_1} + \frac{V_A - V_0}{R_2} = 0, \text{ and}$$

$$v_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = C \frac{d(v_s - v_a)}{dt}.$$

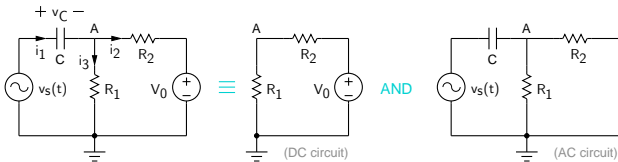In other words, the original circuit can be thought of as,



Coupling capacitor: example (continued)

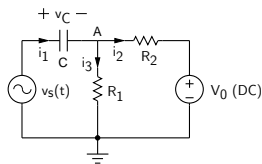


Since $\frac{dV_A}{dt} = 0$ (V_A being constant), we get

$$\frac{V_A}{R_1} + \frac{V_A - V_0}{R_2} = 0, \text{ and}$$

$$v_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = C \frac{d(v_s - v_a)}{dt}.$$

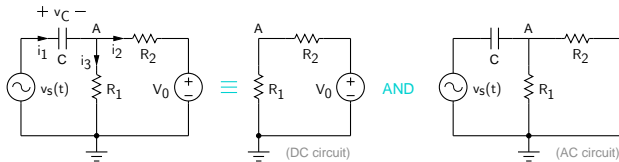In other words, the original circuit can be thought of as,



We can get V_A from the first circuit, $v_a(t)$ from the second, and then combine them to get the actual $v_A(t)$: $v_A(t) = V_A + v_a(t)$

Capacitors in an amplifier circuit

- * Split the original circuit into two circuits:
 - DC circuit: replace each capacitor with an open circuit.
 - AC circuit: replace each DC voltage source with a short circuit.

Capacitors in an amplifier circuit

- * Split the original circuit into two circuits:
 - DC circuit: replace each capacitor with an open circuit.
 - AC circuit: replace each DC voltage source with a short circuit.
- * Analyse the two circuits separately.


Capacitors in an amplifier circuit

- * Split the original circuit into two circuits:
 - DC circuit: replace each capacitor with an open circuit.
 - AC circuit: replace each DC voltage source with a short circuit.
- * Analyse the two circuits separately.
- * Combine the results of the two circuits to obtain the instantaneous voltages and currents.


Capacitors in an amplifier circuit

- * Split the original circuit into two circuits:
 - DC circuit: replace each capacitor with an open circuit.
 - AC circuit: replace each DC voltage source with a short circuit.
- * Analyse the two circuits separately.
- * Combine the results of the two circuits to obtain the instantaneous voltages and currents.
- * The procedure described above also applies to a non-linear circuit such as a BJT amplifier. We have already looked at DC analysis of an amplifier; we will now look at how to handle the time-dependent (AC) part.


Common-emitter amplifier

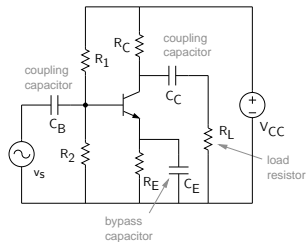


Common-emitter amplifier

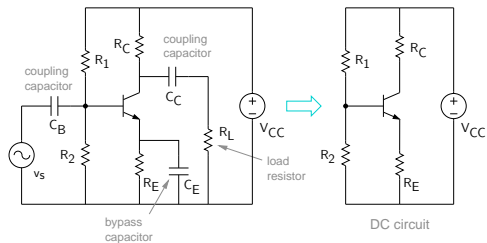

Common-emitter amplifier

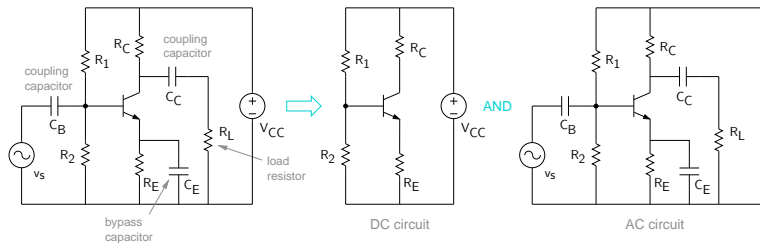


Common-emitter amplifier

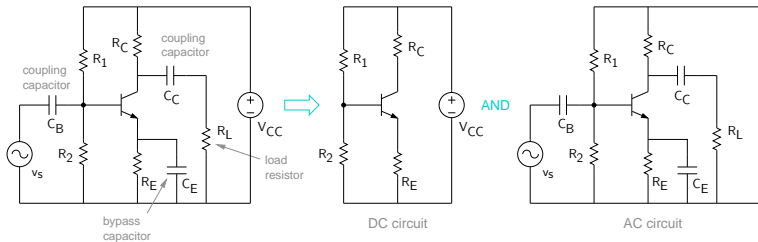


- * The coupling capacitors ensure that the signal source and the load resistor do not affect the DC bias of the amplifier. (We will see the purpose of C_E a little later.)

Common-emitter amplifier

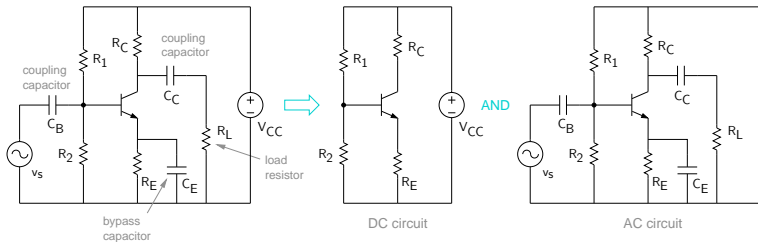


- * The coupling capacitors ensure that the signal source and the load resistor do not affect the DC bias of the amplifier. (We will see the purpose of C_E a little later.)
- * This enables us to bias the amplifier without worrying about what load it is going to drive.

Common-emitter amplifier: AC circuit

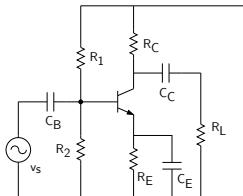

Common-emitter amplifier: AC circuit

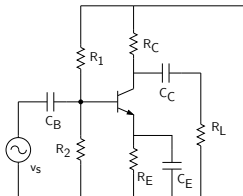

- * The coupling and bypass capacitors are “large” (typically, a few μF), and at frequencies of interest, their impedance is small.


For example, for $C = 10 \mu F$, $f = 1 \text{ kHz}$,

$$Z_C = \frac{1}{2\pi \times 10^3 \times 10 \times 10^{-6}} = 16 \Omega,$$

which is much smaller than typical values of R_1 , R_2 , R_C , R_E (a few $k\Omega$).

$\Rightarrow C_B$, C_C , C_E can be replaced by short circuits at the frequencies of interest.

Common-emitter amplifier: AC circuit

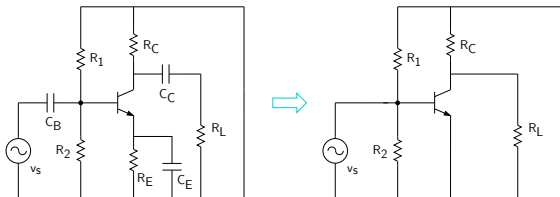

- * The coupling and bypass capacitors are “large” (typically, a few μF), and at frequencies of interest, their impedance is small.


For example, for $C = 10 \mu F$, $f = 1 \text{ kHz}$,

$$Z_C = \frac{1}{2\pi \times 10^3 \times 10 \times 10^{-6}} = 16 \Omega,$$

which is much smaller than typical values of R_1 , R_2 , R_C , R_E (a few $\text{k}\Omega$).

$\Rightarrow C_B$, C_C , C_E can be replaced by short circuits at the frequencies of interest.

Common-emitter amplifier: AC circuit

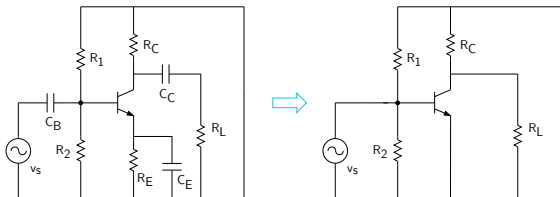

- * The coupling and bypass capacitors are “large” (typically, a few μF), and at frequencies of interest, their impedance is small.

For example, for $C = 10 \mu F$, $f = 1 \text{ kHz}$,


$$Z_C = \frac{1}{2\pi \times 10^3 \times 10 \times 10^{-6}} = 16 \Omega,$$

which is much smaller than typical values of R_1 , R_2 , R_C , R_E (a few $k\Omega$).

$\Rightarrow C_B$, C_C , C_E can be replaced by short circuits at the frequencies of interest.

- * The circuit can be re-drawn in a more friendly format.

Common-emitter amplifier: AC circuit

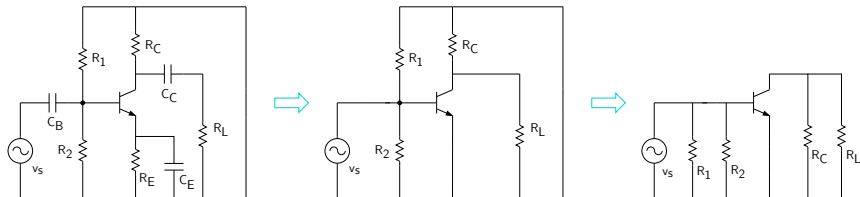

- * The coupling and bypass capacitors are “large” (typically, a few μF), and at frequencies of interest, their impedance is small.

For example, for $C = 10 \mu F$, $f = 1 \text{ kHz}$,


$$Z_C = \frac{1}{2\pi \times 10^3 \times 10 \times 10^{-6}} = 16 \Omega,$$

which is much smaller than typical values of R_1 , R_2 , R_C , R_E (a few $\text{k}\Omega$).

$\Rightarrow C_B$, C_C , C_E can be replaced by short circuits at the frequencies of interest.

- * The circuit can be re-drawn in a more friendly format.

Common-emitter amplifier: AC circuit

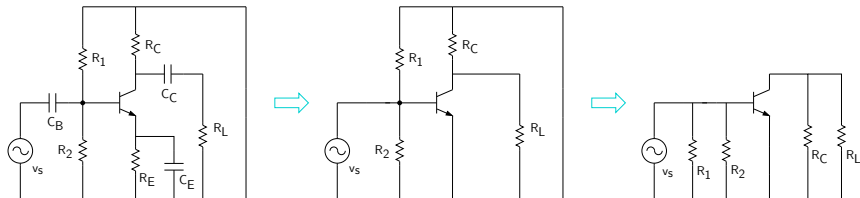

- * The coupling and bypass capacitors are “large” (typically, a few μF), and at frequencies of interest, their impedance is small.

For example, for $C = 10 \mu F$, $f = 1 \text{ kHz}$,


$$Z_C = \frac{1}{2\pi \times 10^3 \times 10 \times 10^{-6}} = 16 \Omega,$$

which is much smaller than typical values of R_1 , R_2 , R_C , R_E (a few $k\Omega$).

$\Rightarrow C_B$, C_C , C_E can be replaced by short circuits at the frequencies of interest.


- * The circuit can be re-drawn in a more friendly format.
- * We now need to figure out the AC description of a BJT.

BJT amplifier: basic operation

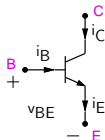


$$v_{BE}(t) = V_0 + V_m \sin \omega t$$
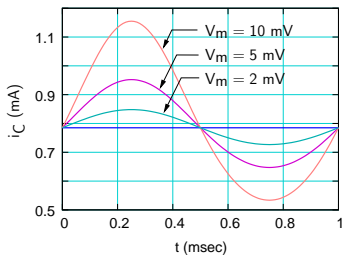
$$V_0 = 0.65 \text{ V}, f = 1 \text{ kHz}$$




BJT amplifier: basic operation

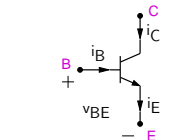


$$v_{BE}(t) = V_0 + V_m \sin \omega t$$
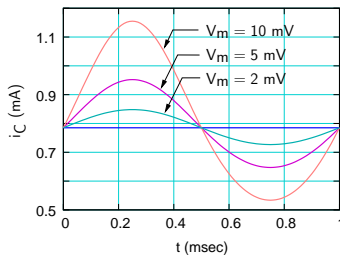
$$V_0 = 0.65 \text{ V}, f = 1 \text{ kHz}$$




- * As the v_{BE} amplitude increases, the shape of $i_C(t)$ deviates from a sinusoid \rightarrow distortion.

BJT amplifier: basic operation

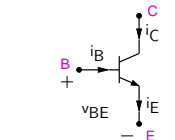


$$v_{BE}(t) = V_0 + V_m \sin \omega t$$
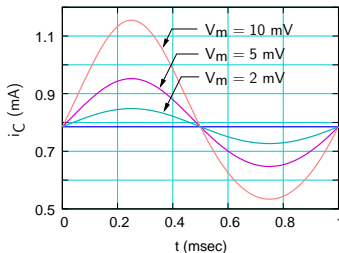
$$V_0 = 0.65 \text{ V}, f = 1 \text{ kHz}$$




- * As the v_{BE} amplitude increases, the shape of $i_C(t)$ deviates from a sinusoid \rightarrow distortion.
- * If $v_{be}(t)$, i.e., the time-varying part of v_{BE} , is kept small, i_C varies linearly with v_{BE} . How small? Let us look at this in more detail.

BJT: small-signal model

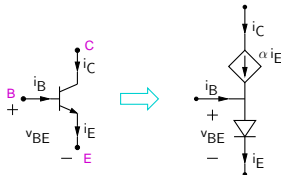

Let $v_{BE}(t) = V_{BE} + v_{be}(t)$ (bias+signal), and $i_C(t) = I_C + i_c(t)$.


BJT: small-signal model

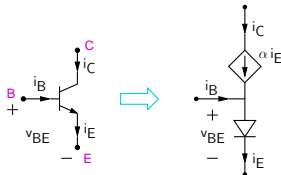

Let $v_{BE}(t) = V_{BE} + v_{be}(t)$ (bias+signal), and $i_C(t) = I_C + i_c(t)$.

Assuming active mode, $i_C(t) = \alpha i_E(t) = \alpha I_{ES} \left[\exp \left(\frac{v_{BE}(t)}{V_T} \right) - 1 \right]$.

BJT: small-signal model

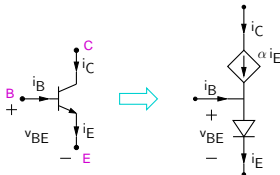


Let $v_{BE}(t) = V_{BE} + v_{be}(t)$ (bias+signal), and $i_C(t) = I_C + i_c(t)$.

Assuming active mode, $i_C(t) = \alpha i_E(t) = \alpha I_{ES} \left[\exp \left(\frac{v_{BE}(t)}{V_T} \right) - 1 \right]$.

Since the B-E junction is forward-biased, $\exp \left(\frac{v_{BE}(t)}{V_T} \right) \gg 1$, and we get

$$\begin{aligned} i_C(t) &= \alpha I_{ES} \exp \left(\frac{v_{BE}(t)}{V_T} \right) = \alpha I_{ES} \exp \left(\frac{V_{BE} + v_{be}(t)}{V_T} \right) \\ &= \alpha I_{ES} \exp \left(\frac{V_{BE}}{V_T} \right) \times \exp \left(\frac{v_{be}(t)}{V_T} \right) \end{aligned}$$

BJT: small-signal model

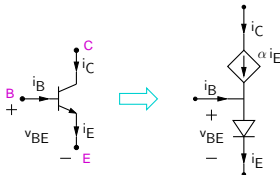

Let $v_{BE}(t) = V_{BE} + v_{be}(t)$ (bias+signal), and $i_C(t) = I_C + i_c(t)$.

Assuming active mode, $i_C(t) = \alpha i_E(t) = \alpha I_{ES} \left[\exp\left(\frac{v_{BE}(t)}{V_T}\right) - 1 \right]$.


Since the B-E junction is forward-biased, $\exp\left(\frac{v_{BE}(t)}{V_T}\right) \gg 1$, and we get

$$\begin{aligned} i_C(t) &= \alpha I_{ES} \exp\left(\frac{v_{BE}(t)}{V_T}\right) = \alpha I_{ES} \exp\left(\frac{V_{BE} + v_{be}(t)}{V_T}\right) \\ &= \alpha I_{ES} \exp\left(\frac{V_{BE}}{V_T}\right) \times \exp\left(\frac{v_{be}(t)}{V_T}\right) \end{aligned}$$

If $v_{be}(t) = 0$, $i_C(t) = I_C$ (the bias value of i_C), i.e.,


$$I_C = \alpha I_{ES} \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right).$$

BJT: small-signal model

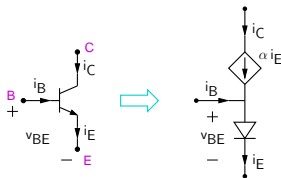

$$i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right) = I_C [1 + x + x^2 + \dots], \quad x = v_{be}(t)/V_T.$$

BJT: small-signal model

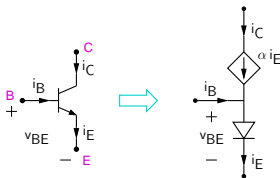


$$i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right) = I_C [1 + x + x^2 + \dots], \quad x = v_{be}(t)/V_T.$$

If x is small, i.e., if the amplitude of $v_{be}(t)$ is small compared to the thermal voltage V_T , we get

$$i_C(t) = I_C \left[1 + \frac{v_{be}(t)}{V_T}\right].$$

BJT: small-signal model

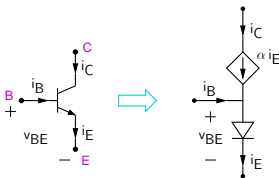


$$i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right) = I_C [1 + x + x^2 + \dots], \quad x = v_{be}(t)/V_T.$$

If x is small, i.e., if the amplitude of $v_{be}(t)$ is small compared to the thermal voltage V_T , we get

$$i_C(t) = I_C \left[1 + \frac{v_{be}(t)}{V_T}\right].$$

We can now see that, for $|v_{be}(t)| \ll V_T$, the relationship between $i_C(t)$ and $v_{be}(t)$ is linear, as we have observed previously.

BJT: small-signal model

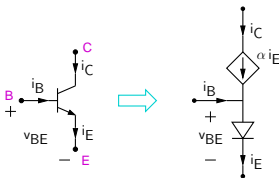

$$i_C(t) = I_C \exp\left(\frac{v_{be}(t)}{V_T}\right) = I_C [1 + x + x^2 + \dots], \quad x = v_{be}(t)/V_T.$$


If x is small, i.e., if the amplitude of $v_{be}(t)$ is small compared to the thermal voltage V_T , we get

$$i_C(t) = I_C \left[1 + \frac{v_{be}(t)}{V_T}\right].$$

We can now see that, for $|v_{be}(t)| \ll V_T$, the relationship between $i_C(t)$ and $v_{be}(t)$ is linear, as we have observed previously.


$$i_C(t) = I_C + i_c(t) = I_C \left[1 + \frac{v_{be}(t)}{V_T}\right] \Rightarrow \boxed{i_c(t) = \frac{I_C}{V_T} v_{be}(t)}$$

BJT: small-signal model

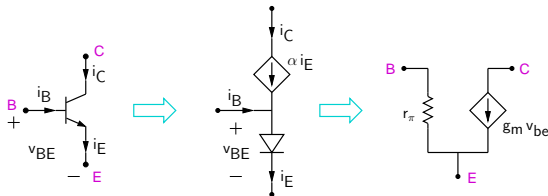

The relationship, $i_c(t) = \frac{I_C}{V_T} v_{be}(t)$ can be represented by a VCCS, $i_c(t) = g_m v_{be}(t)$, where $g_m = I_C/V_T$.

BJT: small-signal model

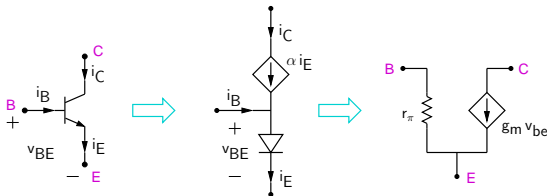


The relationship, $i_c(t) = \frac{I_C}{V_T} v_{be}(t)$ can be represented by a VCCS, $i_c(t) = g_m v_{be}(t)$, where $g_m = I_C/V_T$.

For the base current, we have,

$$i_B(t) = I_B + i_b(t) = \frac{1}{\beta} [I_C + i_c(t)]$$

$$\rightarrow i_b(t) = \frac{1}{\beta} i_c(t) = \frac{1}{\beta} g_m v_{be}(t) \rightarrow v_{be}(t) = (\beta/g_m) i_b(t).$$

BJT: small-signal model

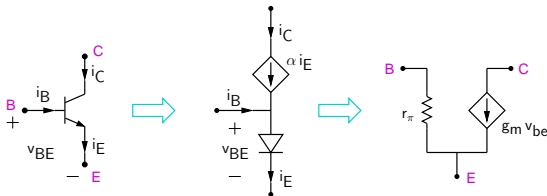

The relationship, $i_c(t) = \frac{I_C}{V_T} v_{be}(t)$ can be represented by a VCCS, $i_c(t) = g_m v_{be}(t)$, where $g_m = I_C/V_T$.


For the base current, we have,

$$i_B(t) = I_B + i_b(t) = \frac{1}{\beta} [I_C + i_c(t)]$$

$$\rightarrow i_b(t) = \frac{1}{\beta} i_c(t) = \frac{1}{\beta} g_m v_{be}(t) \rightarrow v_{be}(t) = (\beta/g_m) i_b(t).$$

The above relationship is represented by a resistance, $r_\pi = \beta/g_m$, connected between B and E.

BJT: small-signal model

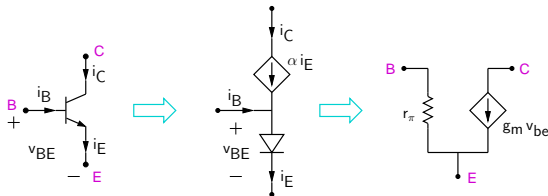

The relationship, $i_c(t) = \frac{I_C}{V_T} v_{be}(t)$ can be represented by a VCCS, $i_c(t) = g_m v_{be}(t)$, where $g_m = I_C / V_T$.

For the base current, we have,


$$i_B(t) = I_B + i_b(t) = \frac{1}{\beta} [I_C + i_c(t)]$$

$$\rightarrow i_b(t) = \frac{1}{\beta} i_c(t) = \frac{1}{\beta} g_m v_{be}(t) \rightarrow v_{be}(t) = (\beta / g_m) i_b(t).$$

The above relationship is represented by a resistance, $r_\pi = \beta / g_m$, connected between B and E.


The resulting model is called the π -model for small-signal description of a BJT.

BJT: small-signal model

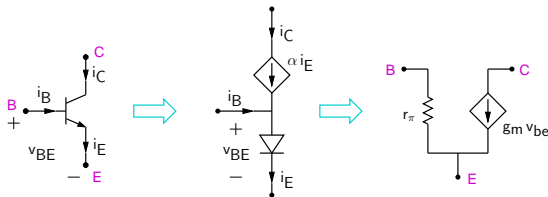


- * The transconductance g_m depends on the biasing of the BJT, since $g_m = I_C/V_T$. For $I_C = 1\text{ mA}$, $V_T \approx 25\text{ mV}$ (room temperature), $g_m = 1\text{ mA}/25\text{ mV} = 40\text{ mS}$.

BJT: small-signal model

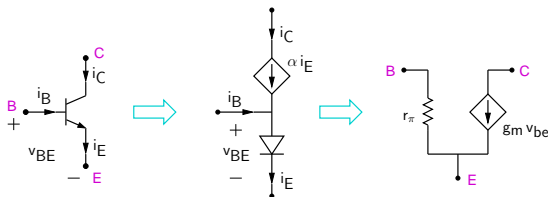


- * The transconductance g_m depends on the biasing of the BJT, since $g_m = I_C / V_T$. For $I_C = 1 \text{ mA}$, $V_T \approx 25 \text{ mV}$ (room temperature), $g_m = 1 \text{ mA} / 25 \text{ mV} = 40 \text{ mS}$.
- * r_π also depends on I_C , since $r_\pi = \beta / g_m = \beta V_T / I_C$. For $I_C = 1 \text{ mA}$, $V_T \approx 25 \text{ mV}$, $\beta = 100$, $r_\pi = 2.5 \text{ k}\Omega$.

BJT: small-signal model

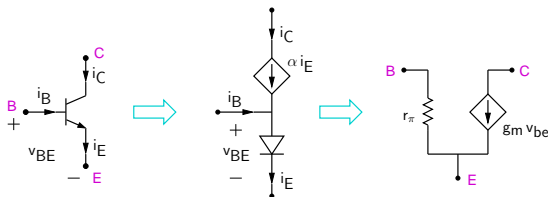


- * The transconductance g_m depends on the biasing of the BJT, since $g_m = I_C/V_T$. For $I_C = 1\text{ mA}$, $V_T \approx 25\text{ mV}$ (room temperature), $g_m = 1\text{ mA}/25\text{ mV} = 40\text{ mS}$.
- * r_π also depends on I_C , since $r_\pi = \beta/g_m = \beta V_T/I_C$. For $I_C = 1\text{ mA}$, $V_T \approx 25\text{ mV}$, $\beta = 100$, $r_\pi = 2.5\text{ k}\Omega$.
- * Note that the small-signal model is valid only for small v_{be} (compared to V_T), as we have seen earlier.

BJT: small-signal model

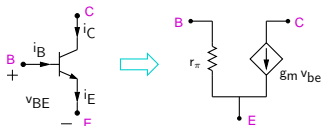


* In the above model, note that i_C is independent of v_{ce} .

BJT: small-signal model

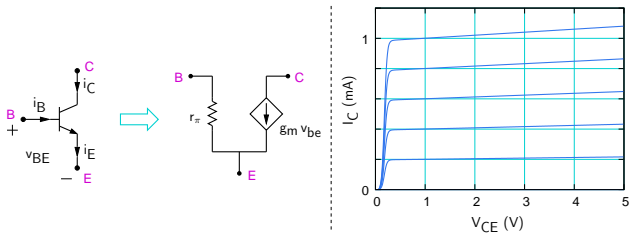


- * In the above model, note that i_c is independent of v_{ce} .
- * In practice, i_c does depend on v_{ce} because of the Early effect, and $\frac{dI_C}{dV_{CE}} \approx \text{constant} = 1/r_o$, where r_o is called the output resistance.

BJT: small-signal model

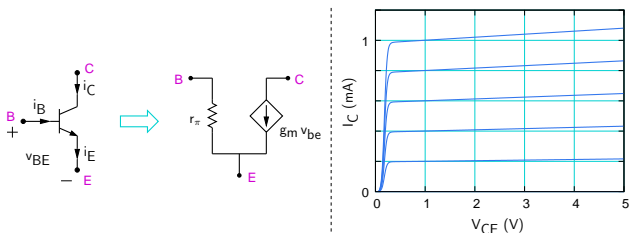


- * In the above model, note that i_c is independent of v_{ce} .
- * In practice, i_c does depend on v_{ce} because of the Early effect, and $\frac{dI_C}{dV_{CE}} \approx \text{constant} = 1/r_o$, where r_o is called the output resistance.
- * A more accurate model includes r_o as well.

BJT: small-signal model

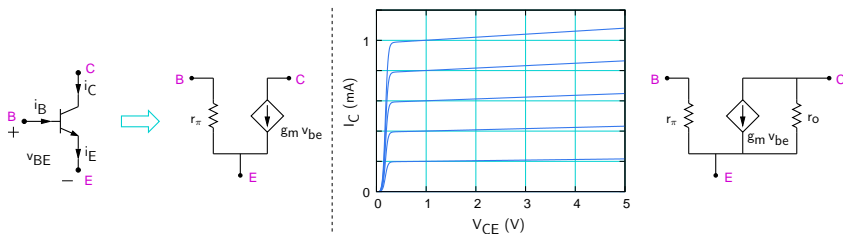

- * In the above model, note that i_c is independent of v_{ce} .
- * In practice, i_c does depend on v_{ce} because of the Early effect, and $\frac{dI_C}{dV_{CE}} \approx \text{constant} = 1/r_o$, where r_o is called the output resistance.
- * A more accurate model includes r_o as well.

BJT: small-signal model

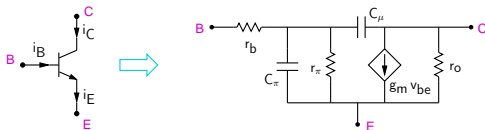


- * A few other components are required to make the small-signal model complete:

r_b : base spreading resistance

C_π : base charging capacitance + B-E junction capacitance


C_μ : B-C junction capacitance

BJT: small-signal model

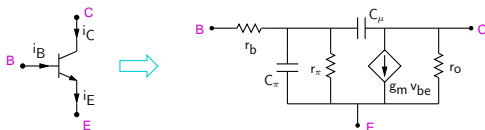

- * A few other components are required to make the small-signal model complete:
 - r_b : base spreading resistance
 - C_π : base charging capacitance + B-E junction capacitance
 - C_μ : B-C junction capacitance
- * The capacitances are typically in the pF range. At low frequencies, $1/\omega C$ is large, and the capacitances can be replaced by open circuits.

BJT: small-signal model

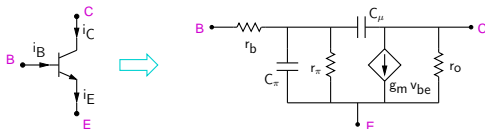

- * A few other components are required to make the small-signal model complete:
 - r_b : base spreading resistance
 - C_π : base charging capacitance + B-E junction capacitance
 - C_μ : B-C junction capacitance
- * The capacitances are typically in the pF range. At low frequencies, $1/\omega C$ is large, and the capacitances can be replaced by open circuits.
- * Note that the small-signal models we have described are valid in the active region only.