

EE101: Op Amp circuits (Part 2)




M. B. Patil


mbpatil@ee.iitb.ac.in

Department of Electrical Engineering
Indian Institute of Technology Bombay

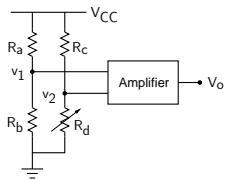Common-mode and differential-mode voltages



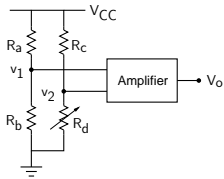
Common-mode and differential-mode voltages



Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

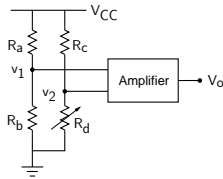Common-mode and differential-mode voltages




Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.

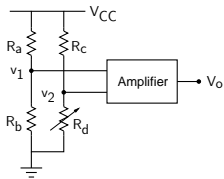Common-mode and differential-mode voltages




Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,

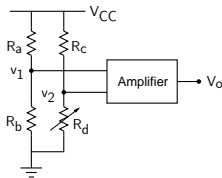Common-mode and differential-mode voltages



Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.


$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,

$$v_1 = \frac{R}{R + R} V_{CC} = \frac{1}{2} V_{CC} .$$

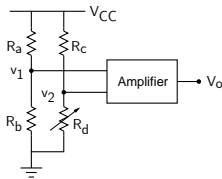Common-mode and differential-mode voltages



Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.


Assuming that the amplifier has a large input resistance,

$$v_1 = \frac{R}{R + R} V_{CC} = \frac{1}{2} V_{CC}.$$

$$v_2 = \frac{(R + \Delta R)}{R + (R + \Delta R)} V_{CC} = \frac{1}{2} \frac{1 + x}{1 + x/2} V_{CC} \approx \frac{1}{2} (1 + x) (1 - x/2) V_{CC} = \frac{1}{2} (1 + x/2) V_{CC},$$

where $x = \Delta R/R$.

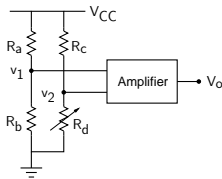Common-mode and differential-mode voltages



Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,

$$v_1 = \frac{R}{R + R} V_{CC} = \frac{1}{2} V_{CC} .$$

$$v_2 = \frac{(R + \Delta R)}{R + (R + \Delta R)} V_{CC} = \frac{1}{2} \frac{1 + x}{1 + x/2} V_{CC} \approx \frac{1}{2} (1 + x) (1 - x/2) V_{CC} = \frac{1}{2} (1 + x/2) V_{CC} ,$$


where $x = \Delta R/R$.

For example, with $V_{CC} = 15 \text{ V}$, $R = 1 \text{ k}$, $\Delta R = 0.01 \text{ k}$,

$$v_1 = 7.5 \text{ V} ,$$


$$v_2 = 7.5 + 0.0375 \text{ V} .$$

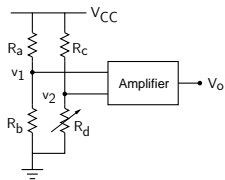Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

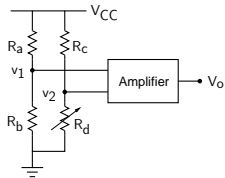
Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

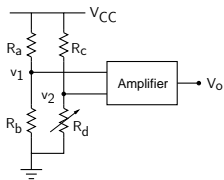Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).


Definitions:

Given v_1 and v_2 ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$

$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$

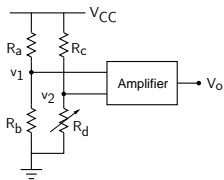Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

Definitions:

Given v_1 and v_2 ,


$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$

$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$

v_1 and v_2 can be rewritten as,

$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$

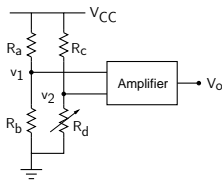Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

Definitions:

Given v_1 and v_2 ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$


$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$

v_1 and v_2 can be rewritten as,

$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$

In the above example, $v_c \approx 7.5 \text{ V}$, $v_d = 37.5 \text{ mV}$.

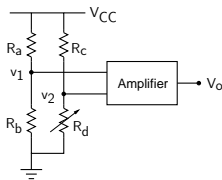Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

Definitions:

Given v_1 and v_2 ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$

$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$

v_1 and v_2 can be rewritten as,


$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$

In the above example, $v_c \approx 7.5 \text{ V}$, $v_d = 37.5 \text{ mV}$.

Note that the common-mode voltage is quite large compared to the differential-mode voltage.

This is a common situation in transducer circuits.

Common-Mode Rejection Ratio

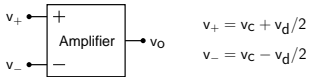


An ideal amplifier would only amplify the difference ($v_+ - v_-$), giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$

where A_d is called the "differential gain" or simply the gain (A_V).

Common-Mode Rejection Ratio

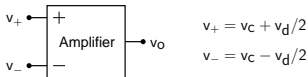

An ideal amplifier would only amplify the difference ($v_+ - v_-$), giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$


where A_d is called the “differential gain” or simply the gain (A_V).

In practice, the output can also have a common-mode component:

$$v_o = A_d v_d + A_c v_c,$$

where A_c is called the “common-mode gain”.

Common-Mode Rejection Ratio

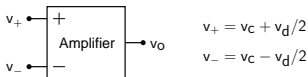

An ideal amplifier would only amplify the difference ($v_+ - v_-$), giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$

where A_d is called the “differential gain” or simply the gain (A_V).

In practice, the output can also have a common-mode component:


$$v_o = A_d v_d + A_c v_c,$$

where A_c is called the “common-mode gain”.

The ability of an amplifier to *reject* the common-mode signal is given by the Common-Mode Rejection Ratio (CMRR):

$$\text{CMRR} = \frac{A_d}{A_c}.$$

Common-Mode Rejection Ratio

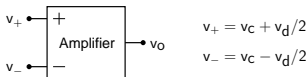

An ideal amplifier would only amplify the difference ($v_+ - v_-$), giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$

where A_d is called the “differential gain” or simply the gain (A_V).

In practice, the output can also have a common-mode component:

$$v_o = A_d v_d + A_c v_c,$$


where A_c is called the “common-mode gain”.

The ability of an amplifier to *reject* the common-mode signal is given by the Common-Mode Rejection Ratio (CMRR):


$$\text{CMRR} = \frac{A_d}{A_c}.$$

For the 741 Op Amp, the CMRR is 90 dB ($\simeq 30,000$), which may be considered to be infinite in many applications. In such cases, mismatch between circuit components will determine the overall common-mode rejection performance of the circuit.

Op Amp circuits (linear region)

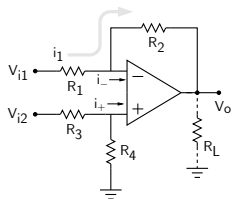


Op Amp circuits (linear region)

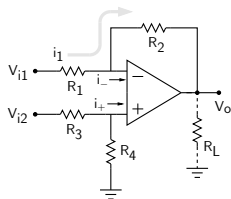

Method 1:

Large input resistance of Op Amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.

Op Amp circuits (linear region)

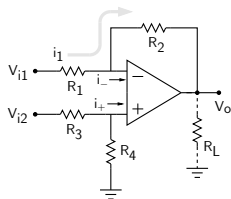


Method 1:

Large input resistance of Op Amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.

Since $V_+ - V_- \approx 0$, $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$.

Op Amp circuits (linear region)

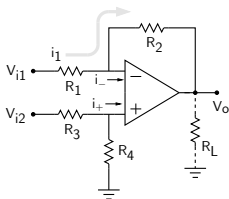


Method 1:

Large input resistance of Op Amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.

Since $V_+ - V_- \approx 0$, $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$.

$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$.

Op Amp circuits (linear region)

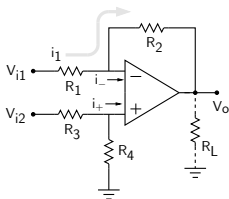

Method 1:

Large input resistance of Op Amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.


Since $V_+ - V_- \approx 0$, $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$.

$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$.

Substituting for V_+ and selecting $R_3/R_4 = R_1/R_2$, we get (show this),

$$V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1}).$$

Op Amp circuits (linear region)

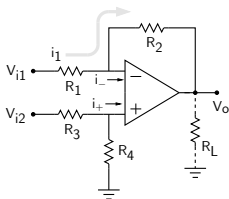

Method 1:

Large input resistance of Op Amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.

Since $V_+ - V_- \approx 0$, $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$.


$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$.

Substituting for V_+ and selecting $R_3/R_4 = R_1/R_2$, we get (show this),

$$V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1}).$$

The circuit is a “difference amplifier.”


Difference amplifier

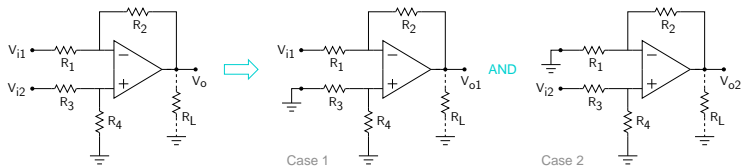

Method 2:

Since the Op Amp is operating in the linear region, we can use superposition:

Difference amplifier

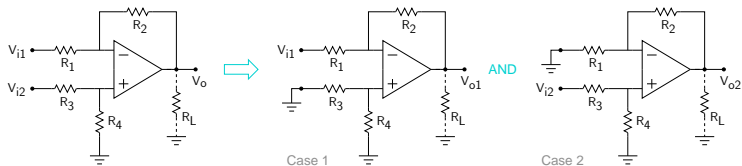


Method 2:

Since the Op Amp is operating in the linear region, we can use superposition:

Case 1: Inverting amplifier (note that $V_+ = 0\text{ V}$).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$

Difference amplifier

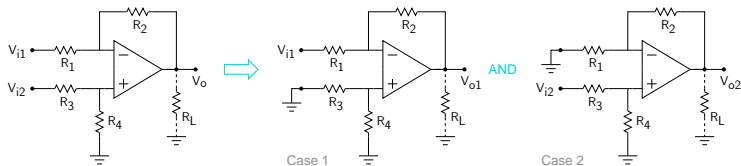

Method 2:

Since the Op Amp is operating in the linear region, we can use superposition:


Case 1: Inverting amplifier (note that $V_+ = 0\text{ V}$).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$

Case 2: Non-inverting amplifier, with $V_i = \frac{R_4}{R_3 + R_4} V_{i2}$.

$$\rightarrow V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2}.$$

Difference amplifier

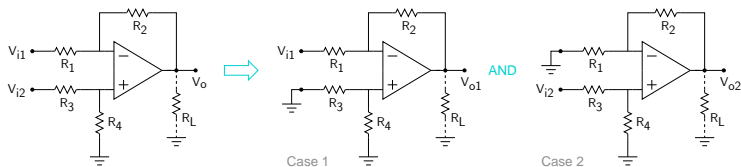

Method 2:

Since the Op Amp is operating in the linear region, we can use superposition:

Case 1: Inverting amplifier (note that $V_+ = 0\text{ V}$).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$


Case 2: Non-inverting amplifier, with $V_i = \frac{R_4}{R_3 + R_4} V_{i2}$.

$$\rightarrow V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2}.$$


The net result is,

$$V_o = V_{o1} + V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1} = \frac{R_2}{R_1} (V_{i2} - V_{i1}), \text{ if } R_3/R_4 = R_1/R_2.$$

Difference amplifier

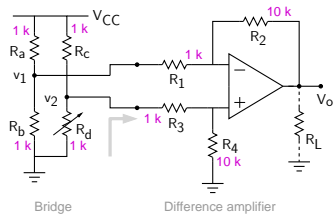


Difference amplifier

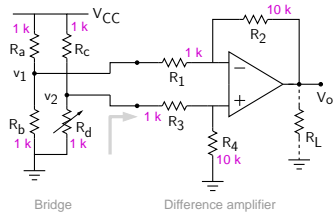

The resistance seen from v_2 is $(R_3 + R_4)$ which is small enough to cause v_2 to change. This is not desirable.


Difference amplifier

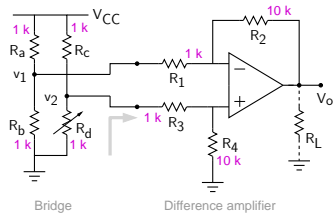

The resistance seen from v_2 is $(R_3 + R_4)$ which is small enough to cause v_2 to change. This is not desirable.

→ need to improve the input resistance of the difference amplifier.

Difference amplifier

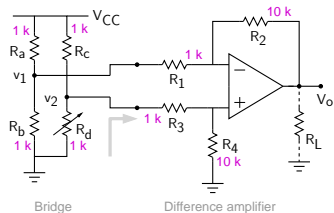


The resistance seen from v_2 is $(R_3 + R_4)$ which is small enough to cause v_2 to change. This is not desirable.


→ need to improve the input resistance of the difference amplifier.

We will discuss an improved difference amplifier later. Before we do that, let us discuss another problem with the above difference amplifier which can be important for some applications (next slide).

Difference amplifier

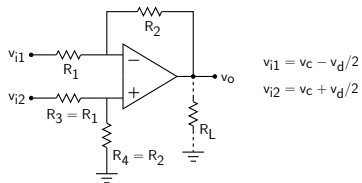


Difference amplifier

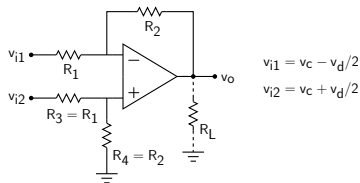

Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.

The output voltage depends only on the differential-mode signal ($v_{i2} - v_{i1}$),
i.e., A_c (common-mode gain) = 0.

Difference amplifier

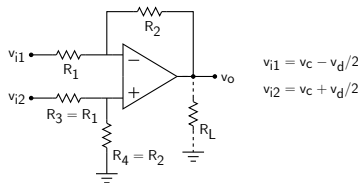


Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.

The output voltage depends only on the differential-mode signal ($v_{i2} - v_{i1}$),
i.e., A_c (common-mode gain) = 0.

In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

Difference amplifier

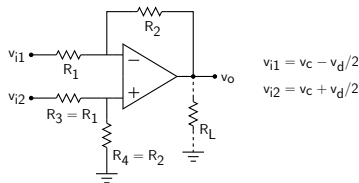


Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.

The output voltage depends only on the differential-mode signal ($v_{i2} - v_{i1}$),
i.e., A_c (common-mode gain) = 0.

In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

$$\begin{aligned} v_o &= \frac{R_2}{R_1 + \Delta R + R_2} \left(1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\ &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this}) \end{aligned}$$

Difference amplifier

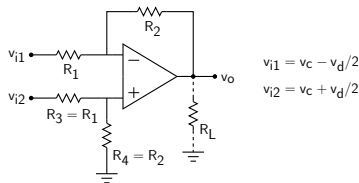

Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.


The output voltage depends only on the differential-mode signal ($v_{i2} - v_{i1}$),
i.e., A_c (common-mode gain) = 0.

In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

$$\begin{aligned} v_o &= \frac{R_2}{R_1 + \Delta R + R_2} \left(1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\ &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this}) \end{aligned}$$

$$|A_c| = x \frac{R_2}{R_1} \ll |A_d| = \frac{R_2}{R_1}, \text{ since } x \sim 0.01 \text{ (with 1\% tolerance resistors).}$$

Difference amplifier

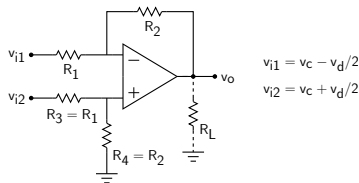

Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.

The output voltage depends only on the differential-mode signal ($v_{i2} - v_{i1}$),
i.e., A_c (common-mode gain) = 0.


In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

$$\begin{aligned} v_o &= \frac{R_2}{R_1 + \Delta R + R_2} \left(1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\ &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this}) \end{aligned}$$

$$|A_c| = x \frac{R_2}{R_1} \ll |A_d| = \frac{R_2}{R_1}, \text{ since } x \sim 0.01 \text{ (with 1\% tolerance resistors).}$$


However, since v_c can be large compared to v_d , the effect of A_c cannot be ignored.

Difference amplifier

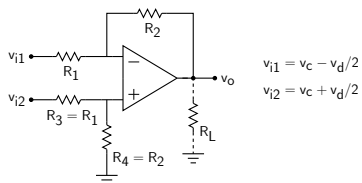

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$


Difference amplifier

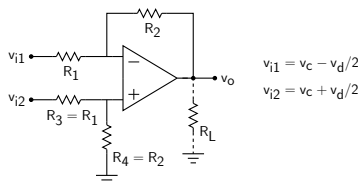

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example, $v_c = 7.5 \text{ V}$ $v_d = 0.0375 \text{ V}$.

Difference amplifier

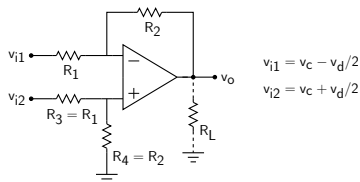


$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example, $v_c = 7.5 \text{ V}$, $v_d = 0.0375 \text{ V}$.

With $R_1 = 1 \text{ k}$, $R_2 = 10 \text{ k}$, $x = 0.01$,

$$|A_c v_c| = x \frac{R_2}{R_1} v_c = 0.01 \times 10 \times 7.5 = 0.75 \text{ V}.$$

Difference amplifier

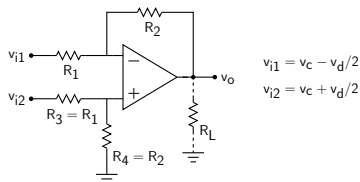

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$


In our earlier example, $v_c = 7.5 \text{ V}$, $v_d = 0.0375 \text{ V}$.

With $R_1 = 1 \text{ k}$, $R_2 = 10 \text{ k}$, $x = 0.01$,

$$|A_c v_c| = x \frac{R_2}{R_1} v_c = 0.01 \times 10 \times 7.5 = 0.75 \text{ V}.$$

$$|A_d v_d| = \frac{R_2}{R_1} v_d = 10 \times 0.0375 = 0.375 \text{ V}.$$

Difference amplifier

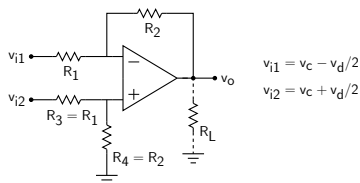

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example, $v_c = 7.5 \text{ V}$, $v_d = 0.0375 \text{ V}$.

With $R_1 = 1 \text{ k}$, $R_2 = 10 \text{ k}$, $x = 0.01$,


$$|A_c v_c| = x \frac{R_2}{R_1} v_c = 0.01 \times 10 \times 7.5 = 0.75 \text{ V}.$$

$$|A_d v_d| = \frac{R_2}{R_1} v_d = 10 \times 0.0375 = 0.375 \text{ V}.$$


The (spurious) common-mode contribution is substantial.

→ need a circuit which will reduce the common-mode component at the output.

Improved difference amplifier

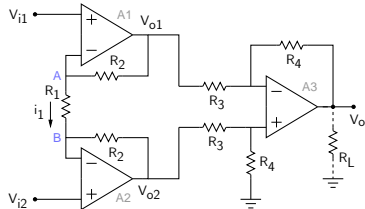


Improved difference amplifier

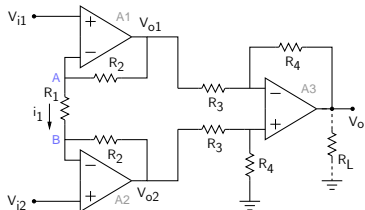

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$


Improved difference amplifier

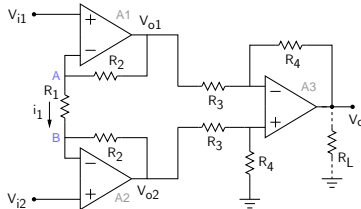

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .


Improved difference amplifier

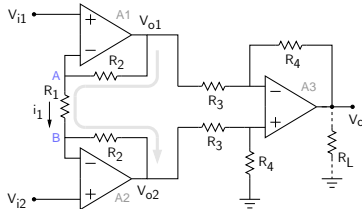

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .

Improved difference amplifier

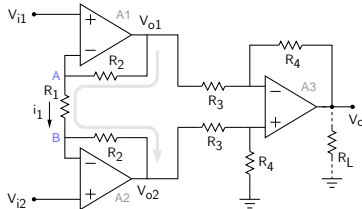


$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2})(R_1 + 2R_2) = (V_{i1} - V_{i2}) \left(1 + \frac{2R_2}{R_1}\right).$$

Improved difference amplifier

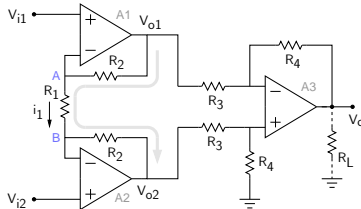


$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2})(R_1 + 2R_2) = (V_{i1} - V_{i2}) \left(1 + \frac{2R_2}{R_1}\right).$$

$$\text{Finally, } V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1}) = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right) (V_{i2} - V_{i1}).$$

Improved difference amplifier

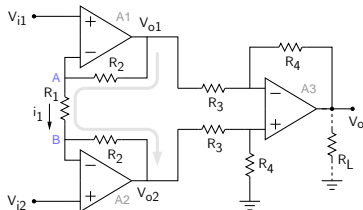

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$


Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2})(R_1 + 2R_2) = (V_{i1} - V_{i2}) \left(1 + \frac{2R_2}{R_1}\right).$$


$$\text{Finally, } V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1}) = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right) (V_{i2} - V_{i1}).$$

This circuit is known as the “instrumentation amplifier.”

Instrumentation amplifier

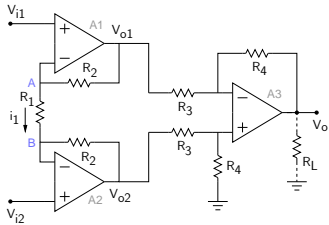


Instrumentation amplifier

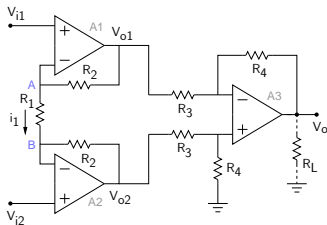

The input resistance seen from V_{i1} or V_{i2} is large (since an Op Amp has a large input resistance).


Instrumentation amplifier

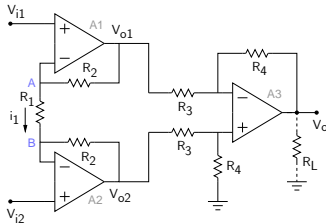

The input resistance seen from V_{i1} or V_{i2} is large (since an Op Amp has a large input resistance).

→ the amplifier will not “load” the preceding stage, a desirable feature.


Instrumentation amplifier

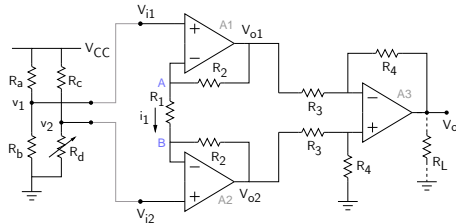

The input resistance seen from V_{i1} or V_{i2} is large (since an Op Amp has a large input resistance).

→ the amplifier will not “load” the preceding stage, a desirable feature.

Instrumentation amplifier

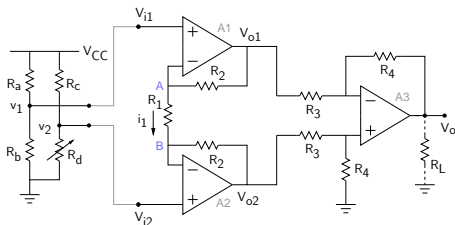


The input resistance seen from V_{i1} or V_{i2} is large (since an Op Amp has a large input resistance).

→ the amplifier will not “load” the preceding stage, a desirable feature.

As a result, the voltages v_1 and v_2 in the bridge circuit will remain essentially the same when the bridge circuit is connected to the instrumentation amplifier.

Instrumentation amplifier

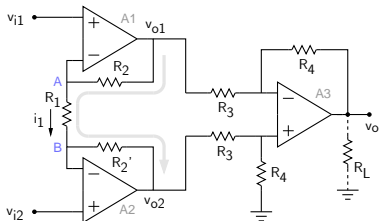


$$v_{i1} = v_c - v_d/2$$

$$v_{i2} = v_c + v_d/2$$

As we have seen earlier, v_{i1} and v_{i2} can have a large common-mode component (v_c).

What is the effect of v_c on the amplifier output v_o ?

Instrumentation amplifier

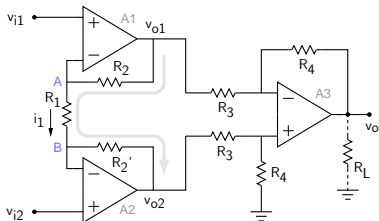

$$v_{i1} = v_c - v_d/2$$


$$v_{i2} = v_c + v_d/2$$

As we have seen earlier, v_{i1} and v_{i2} can have a large common-mode component (v_c).

What is the effect of v_c on the amplifier output v_o ?

$$v_+ \approx v_- \Rightarrow v_A = v_c - v_d/2, \quad v_B = v_c + v_d/2.$$

Instrumentation amplifier

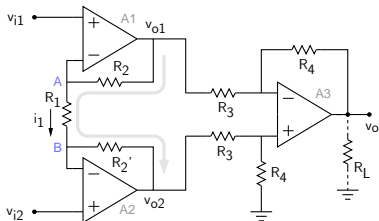

$$v_{i1} = v_c - v_d/2$$

$$v_{i2} = v_c + v_d/2$$


As we have seen earlier, v_{i1} and v_{i2} can have a large common-mode component (v_c).

What is the effect of v_c on the amplifier output v_o ?

$$v_+ \approx v_- \Rightarrow v_A = v_c - v_d/2, \quad v_B = v_c + v_d/2.$$

$$i_1 = \frac{1}{R_1}(v_A - v_B) = \frac{1}{R_1}((v_c - v_d/2) - (v_c + v_d/2)) = -\frac{1}{R_1}v_d.$$

Instrumentation amplifier

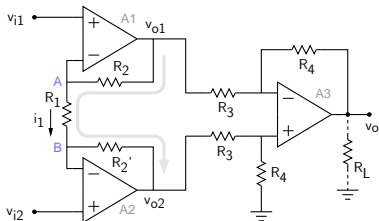

$$v_{i1} = v_c - v_d/2$$

$$v_{i2} = v_c + v_d/2$$

As we have seen earlier, v_{i1} and v_{i2} can have a large common-mode component (v_c).


What is the effect of v_c on the amplifier output v_o ?

$$v_+ \approx v_- \Rightarrow v_A = v_c - v_d/2, \quad v_B = v_c + v_d/2.$$

$$i_1 = \frac{1}{R_1}(v_A - v_B) = \frac{1}{R_1}((v_c - v_d/2) - (v_c + v_d/2)) = -\frac{1}{R_1}v_d.$$

v_c has simply got cancelled! (And this holds even if R_2 and R_2' are not exactly matched.)

Instrumentation amplifier

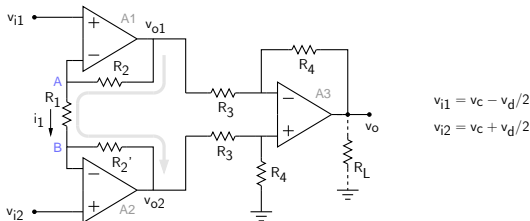

As we have seen earlier, v_{i1} and v_{i2} can have a large common-mode component (v_c).

What is the effect of v_c on the amplifier output v_o ?

$$v_+ \approx v_- \Rightarrow v_A = v_c - v_d/2, \quad v_B = v_c + v_d/2.$$

$$i_1 = \frac{1}{R_1}(v_A - v_B) = \frac{1}{R_1}((v_c - v_d/2) - (v_c + v_d/2)) = -\frac{1}{R_1}v_d.$$

v_c has simply got cancelled! (And this holds even if R_2 and R_2' are not exactly matched.)

→ The instrumentation amplifier is very effective in removing the common-mode signal.


Current-to-voltage conversion

Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.

Current-to-voltage conversion

Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.

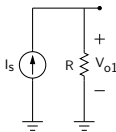
Current-to-voltage conversion can be achieved by simply passing the current through a resistor: $V_{o1} = I_s R$.



Current-to-voltage conversion


Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.

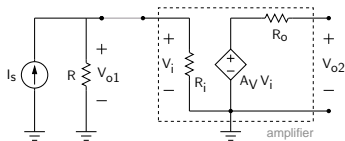Current-to-voltage conversion can be achieved by simply passing the current through a resistor: $V_{o1} = I_s R$.




However, this simple approach will not work if the next stage in the circuit (such as an amplifier) has a finite R_i , since it will modify V_{o1} to $V_{o1} = I_s (R_i \parallel R)$, which is not desirable.

Current-to-voltage conversion

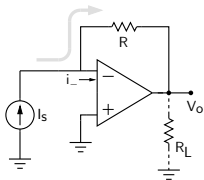


Current-to-voltage conversion

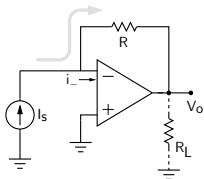

$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$


Current-to-voltage conversion

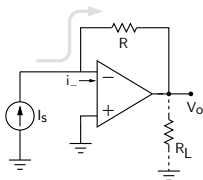

$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of R_L , i.e., irrespective of the next stage.

Current-to-voltage conversion

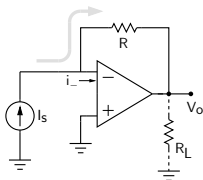


$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of R_L , i.e., irrespective of the next stage.

Example: a photocurrent detector.

Current-to-voltage conversion

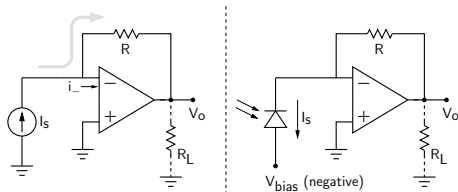


$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of R_L , i.e., irrespective of the next stage.

Example: a photocurrent detector.

Current-to-voltage conversion

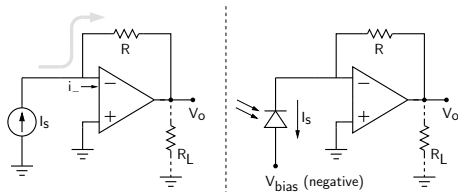


$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of R_L , i.e., irrespective of the next stage.


Example: a photocurrent detector.

$V_o = I_s R$. The diode is under a reverse bias, with $V_n = 0 \text{ V}$ and $V_p = V_{bias}$.

Op Amp circuits (linear region)

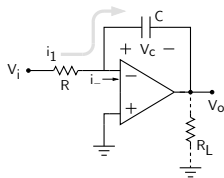


Op Amp circuits (linear region)

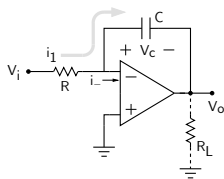

$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i/R.$$

Op Amp circuits (linear region)

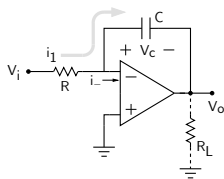


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R.$$

Since $i_- \approx 0$, the current through the capacitor is i_1 .

$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$

Op Amp circuits (linear region)

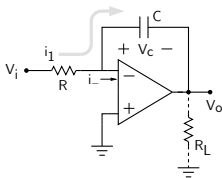


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R.$$

Since $i_- \approx 0$, the current through the capacitor is i_1 .

$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$

$$V_c = V_- - V_o = 0 - V_o = -V_o \rightarrow C \left(-\frac{dV_o}{dt} \right) = \frac{V_i}{R}$$

Op Amp circuits (linear region)

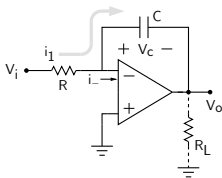

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R.$$

Since $i_- \approx 0$, the current through the capacitor is i_1 .


$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$

$$V_c = V_- - V_o = 0 - V_o = -V_o \rightarrow C \left(-\frac{dV_o}{dt} \right) = \frac{V_i}{R}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

The circuit works as an integrator.


Integrator

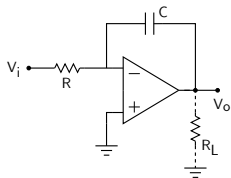

$$R = 1 \text{ k}\Omega, \quad C = 0.2 \mu\text{F}$$


$$V_o = -\frac{1}{RC} \int V_i \, dt$$

Integrator

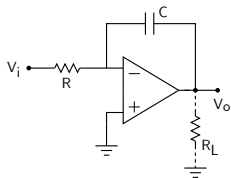


$$R = 1 \text{ k}\Omega, C = 0.2 \mu\text{F}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$


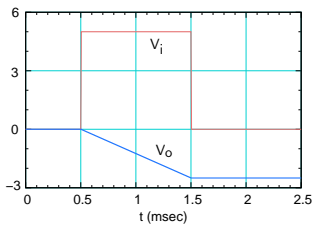


Integrator

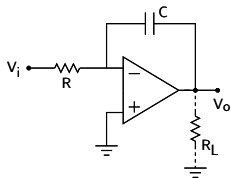


$$R = 1 \text{ k}\Omega, C = 0.2 \mu\text{F}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

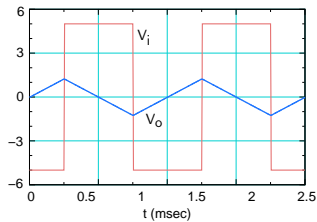
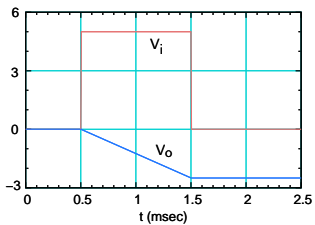


Integrator

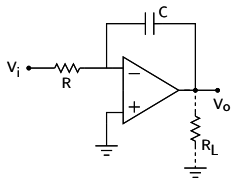



$$R = 1 \text{ k}\Omega, C = 0.2 \mu\text{F}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$



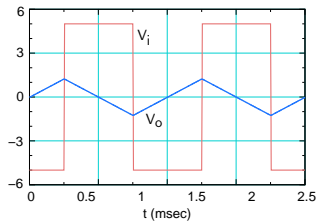
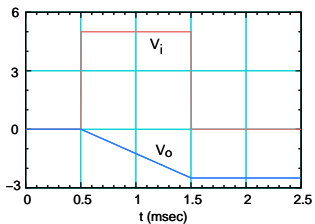


SEQUEL files: ee101_integrator_1.sqproj, ee101_integrator_2.sqproj





Offset voltage

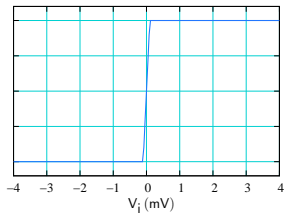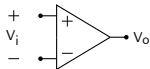

Offset voltage

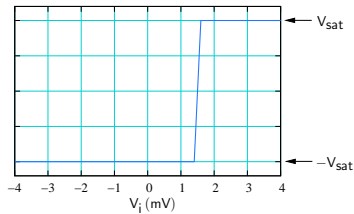
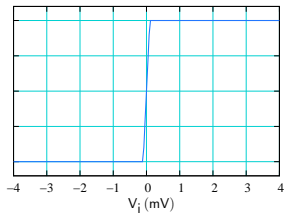
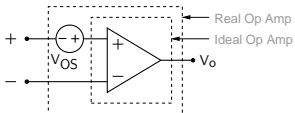
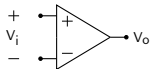


Offset voltage

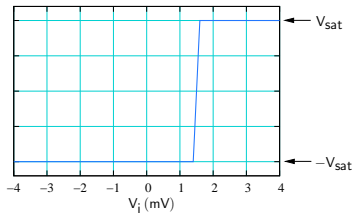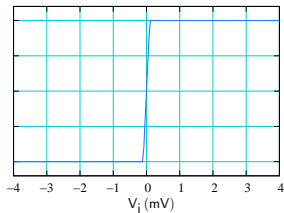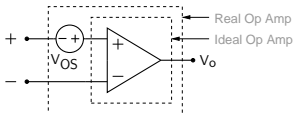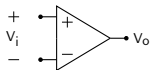

For the real Op Amp, $V_o = A_V((V_+ + V_{OS}) - V_-)$.





Offset voltage

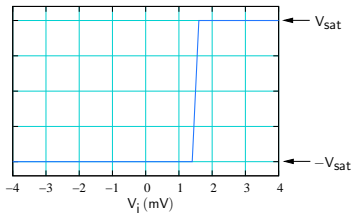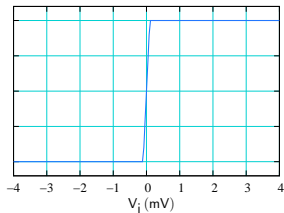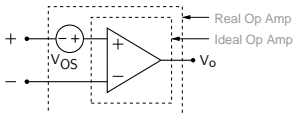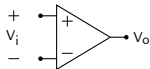

For the real Op Amp, $V_o = A_V((V_+ + V_{OS}) - V_-)$.

For $V_o = 0$ V, $V_+ + V_{OS} - V_- = 0 \rightarrow V_+ - V_- = -V_{OS}$.

Offset voltage

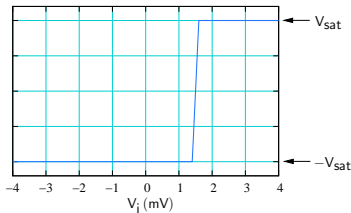
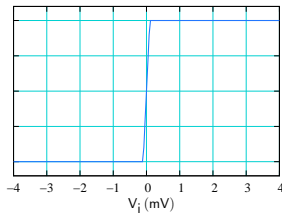
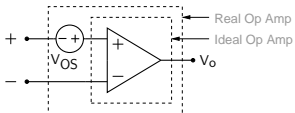
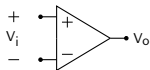


For the real Op Amp, $V_o = A_V((V_+ + V_{OS}) - V_-)$.

For $V_o = 0$ V, $V_+ + V_{OS} - V_- = 0 \rightarrow V_+ - V_- = -V_{OS}$.

V_o versus V_i curve gets shifted.

Offset voltage

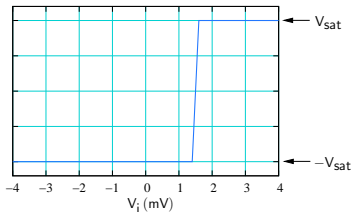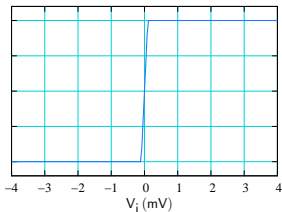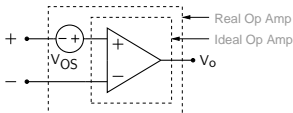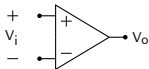

For the real Op Amp, $V_o = A_V((V_+ + V_{OS}) - V_-)$.


For $V_o = 0$ V, $V_+ + V_{OS} - V_- = 0 \rightarrow V_+ - V_- = -V_{OS}$.

V_o versus V_i curve gets shifted.


741: $-6 \text{ mV} < V_{OS} < 6 \text{ mV}$.

OP-77: $-50 \mu\text{V} < V_{OS} < 50 \mu\text{V}$.

Effect of V_{OS}

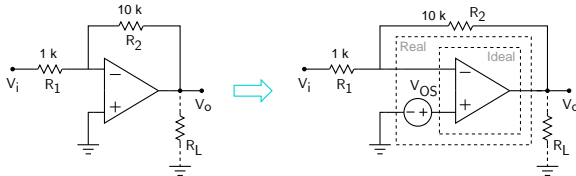


Effect of V_{OS}

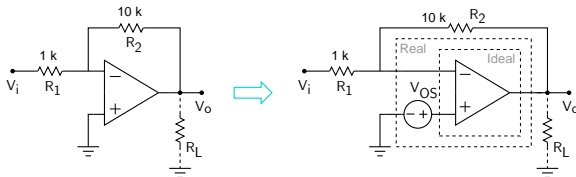

By superposition, $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1} \right).$


Effect of V_{OS}

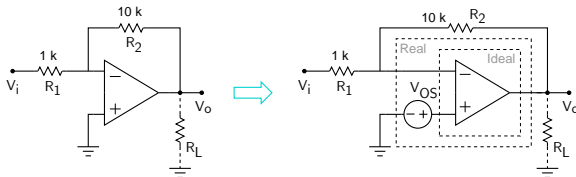

By superposition, $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1} \right)$.

For $V_{OS} = 2\text{ mV}$, the contribution from V_{OS} to V_o is 22 mV ,


Effect of V_{OS}

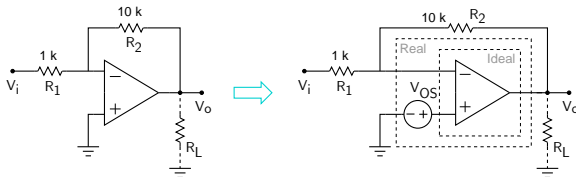


By superposition, $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1} \right)$.

For $V_{OS} = 2\text{ mV}$, the contribution from V_{OS} to V_o is 22 mV ,
i.e., a DC shift of 22 mV .

Effect of V_{OS}

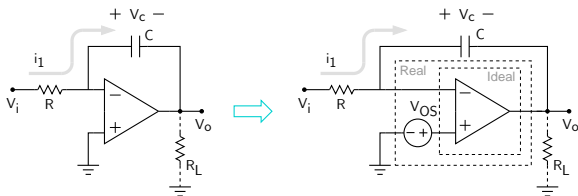


Effect of V_{OS}

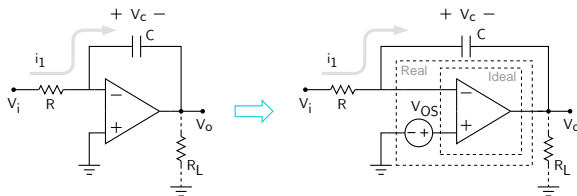

$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$


Effect of V_{OS}

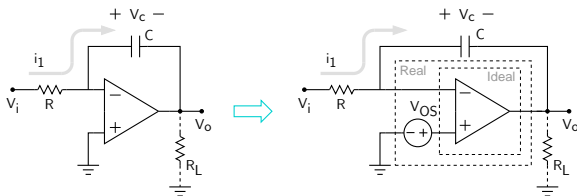

$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$

$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$

Effect of V_{OS}

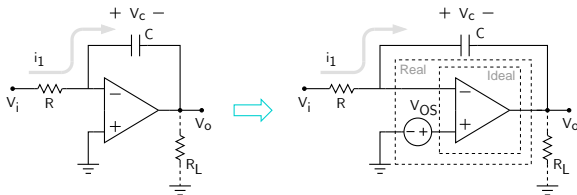


$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$

$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$

Even with $V_i = 0$ V, V_c will keep rising or falling (depending on the sign of V_{OS}).

Eventually, the Op Amp will be driven into saturation.

Effect of V_{OS}

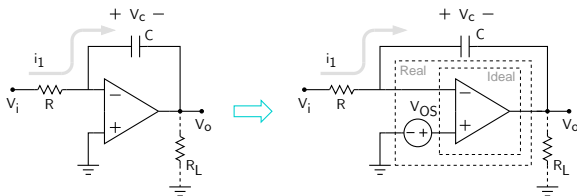

$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$



$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$

Even with $V_i = 0$ V, V_c will keep rising or falling (depending on the sign of V_{OS}).



Eventually, the Op Amp will be driven into saturation.

→ need to address this issue!

Integrator with $V_i = 0$ V:

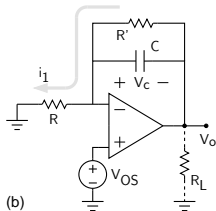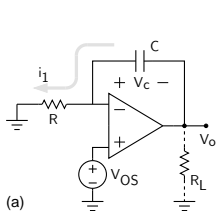



Integrator with $V_i = 0$ V:

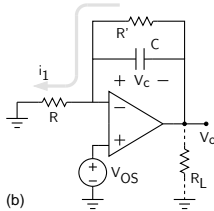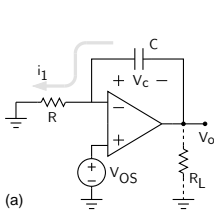

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$

$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{Op Amp saturates.}$$

Integrator with $V_i = 0$ V:

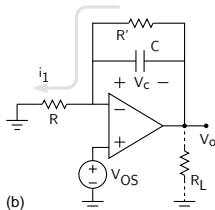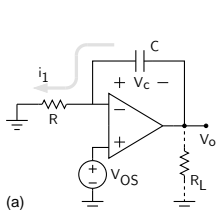



$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$

$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{Op Amp saturates.}$$

(b) There is a DC path for the current.

$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

Integrator with $V_i = 0$ V:

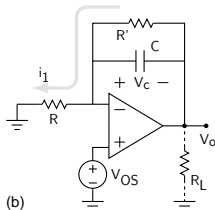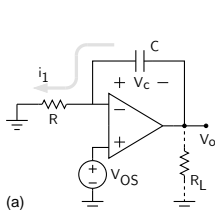

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$

$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{Op Amp saturates.}$$


(b) There is a DC path for the current.

$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$


R' should be small enough to have a negligible effect on V_o .

Effect of V_{OS}

Integrator with $V_i = 0$ V:

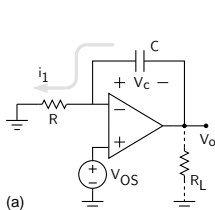

(a)

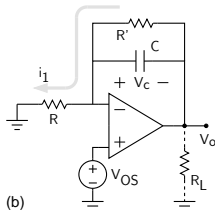

(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$
$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{Op Amp saturates.}$$

(b) There is a DC path for the current.



$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

R' should be small enough to have a negligible effect on V_o .

However, R' must be large enough to ensure that the circuit still functions as an integrator.

Effect of V_{OS}

Integrator with $V_i = 0$ V:

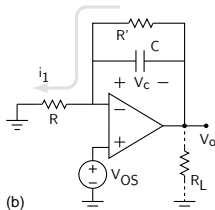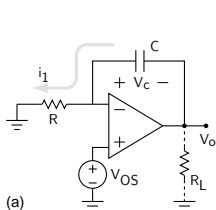

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$
$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{Op Amp saturates.}$$

(b) There is a DC path for the current.


$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

R' should be small enough to have a negligible effect on V_o .



However, R' must be large enough to ensure that the circuit still functions as an integrator.

$\rightarrow R' \gg 1/\omega C$ at the frequency of interest.


Input bias currents

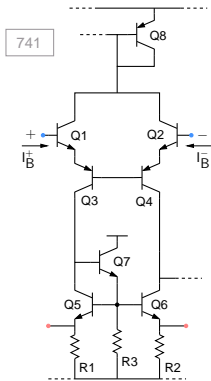

Input bias currents

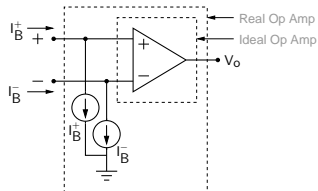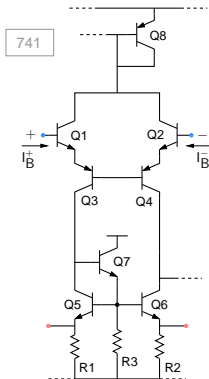

Input bias currents


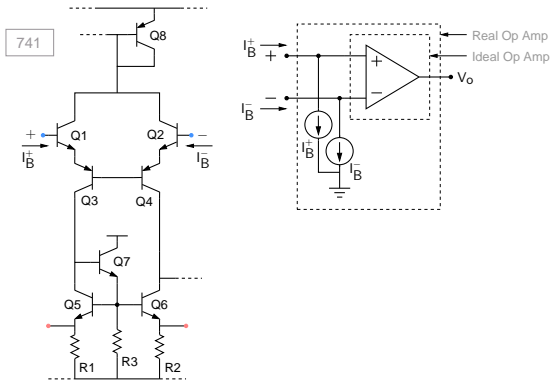


I_B^+ and I_B^- are generally not exactly equal.

$|I_B^+ - I_B^-|$: "offset current" (I_{os})

$(I_B^+ + I_B^-)/2$: "bias current" (I_B).

Input bias currents

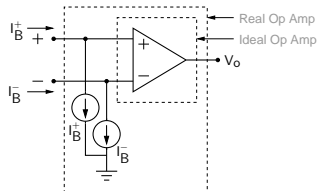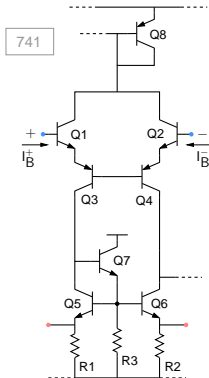

Op Amp	I_B	I_{OS}	V_{OS}	
741	80 nA	20 nA	1 mV	BJT input
OP77	1.2 nA	0.3 nA	10 μ V	BJT input
411	50 pA	25 pA	0.8 mV	FET input


I_B^+ and I_B^- are generally not exactly equal.

$|I_B^+ - I_B^-|$: "offset current" (I_{OS})

$(I_B^+ + I_B^-)/2$: "bias current" (I_B).


Effect of bias currents

Inverting amplifier:

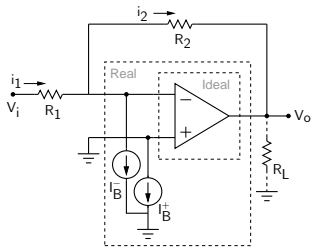

Effect of bias currents


Inverting amplifier:

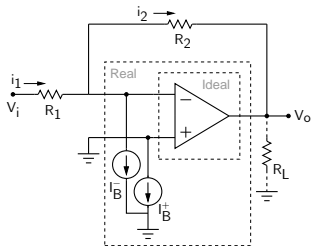

Assume that the Op Amp is ideal in other respects (i.e., $V_{OS} = 0$ V, etc.).

Effect of bias currents


Inverting amplifier:

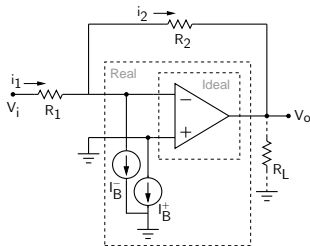

Assume that the Op Amp is ideal in other respects (i.e., $V_{OS} = 0\text{ V}$, etc.).

$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i/R_1.$$

Inverting amplifier:

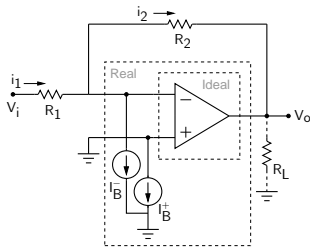


Assume that the Op Amp is ideal in other respects (i.e., $V_{OS} = 0$ V, etc.).

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R_1 .$$

$$i_2 = i_1 - I_B^- \rightarrow V_o = V_- - i_2 R_2 = 0 - \left(\frac{V_i}{R_1} - I_B^- \right) R_2 = -\frac{R_2}{R_1} V_i + I_B^- R_2 ,$$

Inverting amplifier:

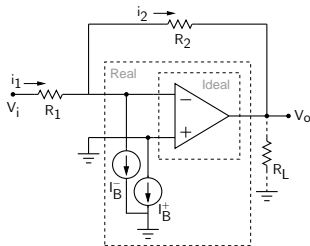

Assume that the Op Amp is ideal in other respects (i.e., $V_{OS} = 0$ V, etc.).

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R_1.$$


$$i_2 = i_1 - I_B^- \rightarrow V_o = V_- - i_2 R_2 = 0 - \left(\frac{V_i}{R_1} - I_B^- \right) R_2 = -\frac{R_2}{R_1} V_i + I_B^- R_2,$$

i.e., the bias current causes a DC shift in V_o .

For $I_B^- = 80$ nA, $R_2 = 10$ k, $\Delta V_o = 0.8$ mV.


Effect of bias currents

Non-inverting amplifier:

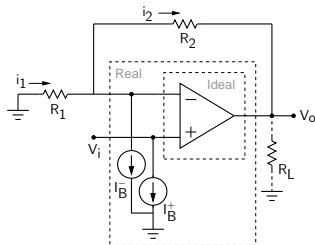

Effect of bias currents


Non-inverting amplifier:

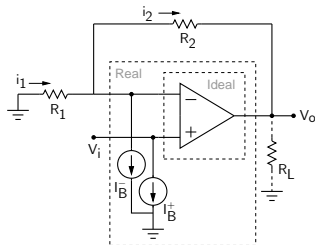

Assume that the Op Amp is ideal in other respects (i.e., $V_{OS} = 0$ V, etc.).

Effect of bias currents

Non-inverting amplifier:

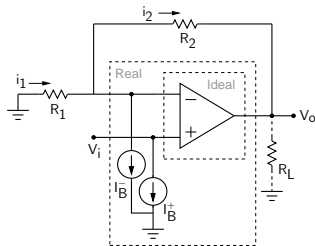


Assume that the Op Amp is ideal in other respects (i.e., $V_{OS} = 0$ V, etc.).

$$V_- \approx V_+ = V_i \rightarrow i_1 = -V_i/R_1.$$

Effect of bias currents

Non-inverting amplifier:

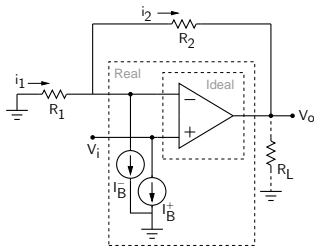


Assume that the Op Amp is ideal in other respects (i.e., $V_{OS} = 0\text{ V}$, etc.).

$$V_- \approx V_+ = V_i \rightarrow i_1 = -V_i/R_1.$$

$$i_2 = i_1 - I_B^- = -\frac{V_i}{R_1} - I_B^-.$$

Effect of bias currents

Non-inverting amplifier:

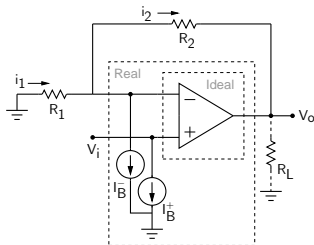

Assume that the Op Amp is ideal in other respects (i.e., $V_{OS} = 0$ V, etc.).

$$V_- \approx V_+ = V_i \rightarrow i_1 = -V_i/R_1.$$


$$i_2 = i_1 - I_B^- = -\frac{V_i}{R_1} - I_B^-.$$

$$V_o = V_i - i_2 R_2 = V_i - \left(-\frac{V_i}{R_1} - I_B^- \right) R_2 = V_i \left(1 + \frac{R_2}{R_1} \right) + I_B^- R_2.$$

→ Again, a DC shift ΔV_o .


Effect of bias currents

Integrator:

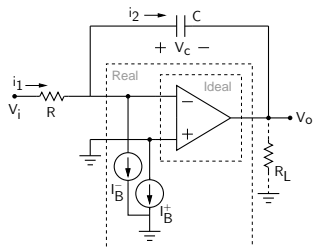

Effect of bias currents


Integrator:

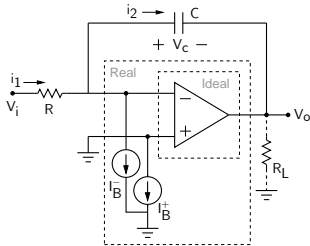

Even with $V_i = 0\text{ V}$, $V_c = \frac{1}{C} \int -I_B^- dt$ will drive the Op Amp into saturation.

Effect of bias currents

Integrator:

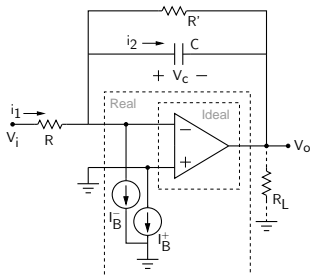


Even with $V_i = 0\text{ V}$, $V_c = \frac{1}{C} \int -I_B^- dt$ will drive the Op Amp into saturation.

Connecting R' across C provides a DC path for the current, and results in a DC shift $\Delta V_o = I_B^- R'$ at the output.

Effect of bias currents

Integrator:

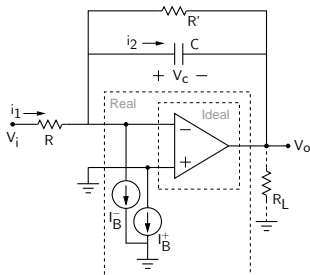

Even with $V_i = 0\text{ V}$, $V_c = \frac{1}{C} \int -I_B^- dt$ will drive the Op Amp into saturation.

Connecting R' across C provides a DC path for the current, and results in a DC shift $\Delta V_o = I_B^- R'$ at the output.

As we have discussed earlier, R' should be small enough to have a negligible effect on V_o . However, R' must be large enough to ensure that the circuit still functions as an integrator.