

EE101: RLC Circuits (with DC sources)




M. B. Patil


mbpatil@ee.iitb.ac.in

Department of Electrical Engineering
Indian Institute of Technology Bombay

Series RLC circuit

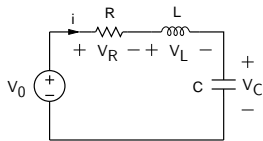


Series RLC circuit

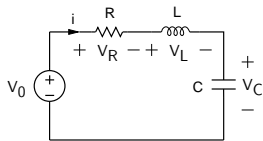

$$\text{KVL: } V_R + V_L + V_C = V_0 \Rightarrow iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_0$$

Series RLC circuit

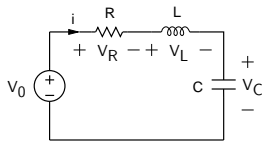


$$\text{KVL: } V_R + V_L + V_C = V_0 \Rightarrow iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_0$$

Differentiating w. r. t. t , we get,

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i = 0.$$

Series RLC circuit

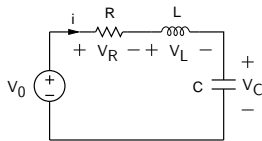

$$\text{KVL: } V_R + V_L + V_C = V_0 \Rightarrow iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_0$$


Differentiating w. r. t. t , we get,

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0.$$


$$\text{i.e., } \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0,$$

a second-order ODE with constant coefficients.

Parallel RLC circuit

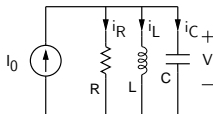


Parallel RLC circuit

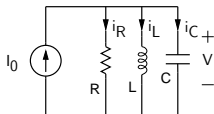

$$\text{KCL: } i_R + i_L + i_C = i_0 \Rightarrow \frac{1}{R} V + \frac{1}{L} \int V dt + C \frac{dV}{dt} = i_0$$

Parallel RLC circuit

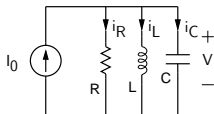


$$\text{KCL: } i_R + i_L + i_C = i_0 \Rightarrow \frac{1}{R} V + \frac{1}{L} \int V dt + C \frac{dV}{dt} = i_0$$

Differentiating w. r. t. t , we get,

$$\frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + C \frac{d^2 V}{dt^2} = 0.$$

Parallel RLC circuit

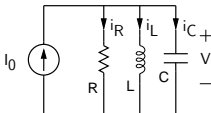

$$\text{KCL: } i_R + i_L + i_C = i_0 \Rightarrow \frac{1}{R} V + \frac{1}{L} \int V dt + C \frac{dV}{dt} = i_0$$


Differentiating w. r. t. t , we get,

$$\frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + C \frac{d^2 V}{dt^2} = 0.$$


$$\text{i.e., } \frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0,$$

a second-order ODE with constant coefficients.

Series/Parallel RLC circuits

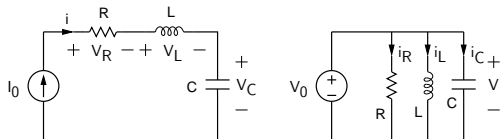


Series/Parallel *RLC* circuits

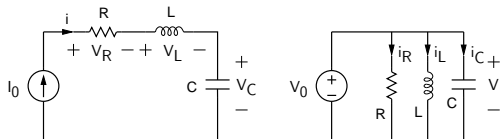

- * A series RLC circuit driven by a constant current source is trivial to analyze.


Series/Parallel *RLC* circuits

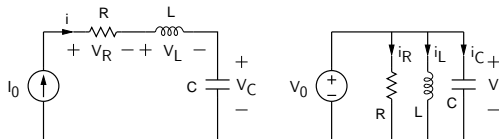

- * A series RLC circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = i R, \quad V_L = L \frac{di}{dt}, \quad V_C = \frac{1}{C} \int i dt.$$

Series/Parallel RLC circuits

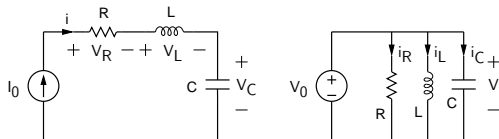


- * A series RLC circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = i R, \quad V_L = L \frac{di}{dt}, \quad V_C = \frac{1}{C} \int i dt.$$

- * A parallel RLC circuit driven by a constant voltage source is trivial to analyze.

Series/Parallel RLC circuits

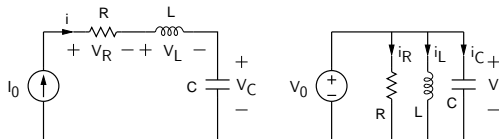


- * A series RLC circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = iR, \quad V_L = L \frac{di}{dt}, \quad V_C = \frac{1}{C} \int i dt.$$

- * A parallel RLC circuit driven by a constant voltage source is trivial to analyze. Since the voltage across each element is known, the current can be found in a straightforward manner.

$$i_R = V/R, \quad i_C = C \frac{dV}{dt}, \quad i_L = \frac{1}{L} \int V dt.$$

Series/Parallel RLC circuits

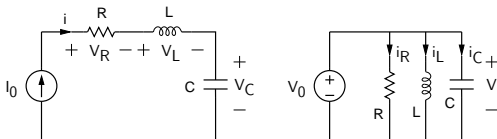

- * A series RLC circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = iR, \quad V_L = L \frac{di}{dt}, \quad V_C = \frac{1}{C} \int i dt.$$

- * A parallel RLC circuit driven by a constant voltage source is trivial to analyze. Since the voltage across each element is known, the current can be found in a straightforward manner.


$$i_R = V/R, \quad i_C = C \frac{dV}{dt}, \quad i_L = \frac{1}{L} \int V dt.$$

- * The above equations hold even if the applied voltage or current is not constant, and the variables of interest can still be easily obtained without solving a differential equation.


A general RLC circuit (with one inductor and one capacitor) also leads to a second-order ODE. As an example, consider the following circuit:

Series/Parallel RLC circuits

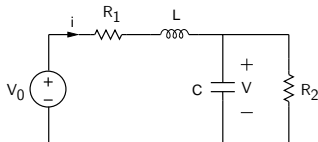A general RLC circuit (with one inductor and one capacitor) also leads to a second-order ODE. As an example, consider the following circuit:



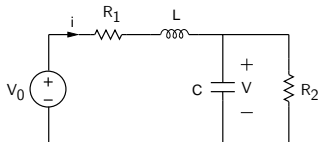
A general RLC circuit (with one inductor and one capacitor) also leads to a second-order ODE. As an example, consider the following circuit:



$$V_0 = R_1 i + L \frac{di}{dt} + V \quad (1)$$

$$i = C \frac{dV}{dt} + \frac{1}{R_2} V \quad (2)$$

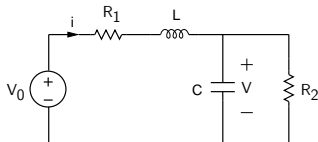A general *RLC* circuit (with one inductor and one capacitor) also leads to a second-order ODE. As an example, consider the following circuit:



$$V_0 = R_1 i + L \frac{di}{dt} + V \quad (1)$$

$$i = C \frac{dV}{dt} + \frac{1}{R_2} V \quad (2)$$

Substituting (2) in (1), we get

$$V_0 = R_1 [CV' + V/R_2] + L [CV'' + V'/R_2] + V, \quad (3)$$

$$V'' [LC] + V' [R_1 C + L/R_2] + V [1 + R_1/R_2] = V_0. \quad (4)$$

Consider the second-order ODE with constant coefficients,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = K \text{ (constant)}.$$

Consider the second-order ODE with constant coefficients,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = K \text{ (constant)}.$$

The general solution $y(t)$ can be written as,

$$y(t) = y^{(h)}(t) + y^{(p)}(t),$$

where $y^{(h)}(t)$ is the solution of the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0,$$

and $y^{(p)}(t)$ is a particular solution.

General solution

Consider the second-order ODE with constant coefficients,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = K \text{ (constant)} .$$

The general solution $y(t)$ can be written as,

$$y(t) = y^{(h)}(t) + y^{(p)}(t) ,$$

where $y^{(h)}(t)$ is the solution of the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0 ,$$

and $y^{(p)}(t)$ is a particular solution.

Since $K = \text{constant}$, a particular solution is simply $y^{(p)}(t) = K/b$.

Consider the second-order ODE with constant coefficients,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = K \text{ (constant)}.$$

The general solution $y(t)$ can be written as,

$$y(t) = y^{(h)}(t) + y^{(p)}(t),$$

where $y^{(h)}(t)$ is the solution of the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0,$$

and $y^{(p)}(t)$ is a particular solution.

Since $K = \text{constant}$, a particular solution is simply $y^{(p)}(t) = K/b$.

In the context of *RLC* circuits, $y^{(p)}(t)$ is the steady-state value of the variable of interest, i.e.,

$$y^{(p)} = \lim_{t \rightarrow \infty} y(t),$$

which can be often found by inspection.

For the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0,$$

we first find the roots of the associated *characteristic equation*,

$$r^2 + a r + b = 0.$$

Let the roots be r_1 and r_2 . We have the following possibilities:

For the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0,$$

we first find the roots of the associated *characteristic equation*,

$$r^2 + a r + b = 0.$$

Let the roots be r_1 and r_2 . We have the following possibilities:

- * r_1, r_2 are real, $r_1 \neq r_2$ (“overdamped”)

$$y^{(h)}(t) = C_1 \exp(r_1 t) + C_2 \exp(r_2 t).$$

For the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0,$$

we first find the roots of the associated *characteristic equation*,

$$r^2 + a r + b = 0.$$

Let the roots be r_1 and r_2 . We have the following possibilities:

- * r_1, r_2 are real, $r_1 \neq r_2$ (“overdamped”)

$$y^{(h)}(t) = C_1 \exp(r_1 t) + C_2 \exp(r_2 t).$$

- * r_1, r_2 are complex, $r_{1,2} = \alpha \pm j\omega$ (“underdamped”)

$$y^{(h)}(t) = \exp(\alpha t) [C_1 \cos(\omega t) + C_2 \sin(\omega t)].$$

For the homogeneous equation,

$$\frac{d^2 y}{dt^2} + a \frac{dy}{dt} + b y = 0,$$

we first find the roots of the associated *characteristic equation*,

$$r^2 + a r + b = 0.$$

Let the roots be r_1 and r_2 . We have the following possibilities:

- * r_1, r_2 are real, $r_1 \neq r_2$ (“overdamped”)

$$y^{(h)}(t) = C_1 \exp(r_1 t) + C_2 \exp(r_2 t).$$


- * r_1, r_2 are complex, $r_{1,2} = \alpha \pm j\omega$ (“underdamped”)

$$y^{(h)}(t) = \exp(\alpha t) [C_1 \cos(\omega t) + C_2 \sin(\omega t)].$$

- * $r_1 = r_2 = \alpha$ (“critically damped”)

$$y^{(h)}(t) = \exp(\alpha t) [C_1 t + C_2].$$

Parallel RLC circuit

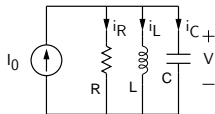


$$R=10\,\Omega$$

$$C=1\,\mu\text{F}$$

$$L=0.44\,\text{mH}$$

$$I_0 = 100\,\text{mA}$$

Parallel RLC circuit

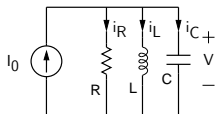

$$R=10\,\Omega$$

$$C=1\,\mu\text{F}$$


$$L=0.44\,\text{mH}$$

$$I_0=100\,\text{mA}$$

$$i_L(0^-) = 0\,\text{A} \Rightarrow i_L(0^+) = 0\,\text{A}.$$

$$V(0^-) = 0\,\text{V} \Rightarrow V(0^+) = 0\,\text{V}.$$

Parallel RLC circuit

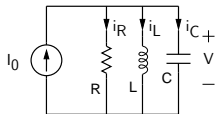

$$R=10\,\Omega$$

$$C=1\,\mu\text{F}$$

$$L=0.44\,\text{mH}$$


$$I_0 = 100\,\text{mA}$$

$$i_L(0^-) = 0\,\text{A} \Rightarrow i_L(0^+) = 0\,\text{A}.$$

$$V(0^-) = 0\,\text{V} \Rightarrow V(0^+) = 0\,\text{V}.$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (\text{as derived earlier})$$

Parallel RLC circuit

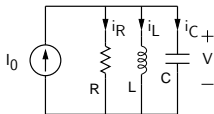

$$R=10\,\Omega$$

$$C=1\,\mu\text{F}$$

$$L=0.44\,\text{mH}$$

$$I_0=100\,\text{mA}$$

$$i_L(0^-) = 0\,\text{A} \Rightarrow i_L(0^+) = 0\,\text{A}.$$


$$V(0^-) = 0\,\text{V} \Rightarrow V(0^+) = 0\,\text{V}.$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (\text{as derived earlier})$$

The roots of the characteristic equation are (show this):

$$r_1 = -0.65 \times 10^5\,\text{s}^{-1}, \quad r_2 = -0.35 \times 10^5\,\text{s}^{-1}.$$

Parallel RLC circuit

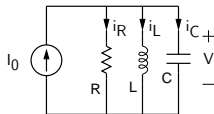

$$R=10\,\Omega$$

$$C=1\,\mu\text{F}$$

$$L=0.44\,\text{mH}$$

$$I_0 = 100\,\text{mA}$$

$$i_L(0^-) = 0\,\text{A} \Rightarrow i_L(0^+) = 0\,\text{A}.$$

$$V(0^-) = 0\,\text{V} \Rightarrow V(0^+) = 0\,\text{V}.$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (\text{as derived earlier})$$


The roots of the characteristic equation are (show this):

$$r_1 = -0.65 \times 10^5\,\text{s}^{-1}, \quad r_2 = -0.35 \times 10^5\,\text{s}^{-1}.$$

The general expression for $V(t)$ is,

$$V(t) = A \exp(r_1 t) + B \exp(r_2 t) + V(\infty),$$

Parallel RLC circuit

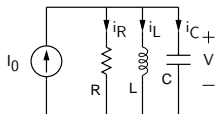

$$R=10\,\Omega$$

$$C=1\,\mu\text{F}$$

$$L=0.44\,\text{mH}$$

$$I_0 = 100\,\text{mA}$$

$$i_L(0^-) = 0\,\text{A} \Rightarrow i_L(0^+) = 0\,\text{A}.$$

$$V(0^-) = 0\,\text{V} \Rightarrow V(0^+) = 0\,\text{V}.$$

$$\frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0 \quad (\text{as derived earlier})$$

The roots of the characteristic equation are (show this):

$$r_1 = -0.65 \times 10^5\,\text{s}^{-1}, \quad r_2 = -0.35 \times 10^5\,\text{s}^{-1}.$$

The general expression for $V(t)$ is,

$$V(t) = A \exp(r_1 t) + B \exp(r_2 t) + V(\infty),$$

$$\text{i.e., } V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2) + V(\infty),$$

$$\text{where } \tau_1 = -1/r_1 = 15.4\,\mu\text{s}, \quad \tau_2 = -1/r_2 = 28.6\,\mu\text{s}.$$

Parallel RLC circuit

$$\text{As } t \rightarrow \infty, V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}.$$

Parallel RLC circuit

As $t \rightarrow \infty$, $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}.$

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2),$

As $t \rightarrow \infty$, $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}.$

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2),$

Since $V(0^+) = 0 \text{ V}$, we have,

$$A + B = 0. \quad (1)$$

Parallel RLC circuit

As $t \rightarrow \infty$, $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$.

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$,

Since $V(0^+) = 0 \text{ V}$, we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is $i_L(0^+) = 0 \text{ A}$, which can be used to obtain $\frac{dV}{dt}(0^+)$.

Parallel RLC circuit

As $t \rightarrow \infty$, $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$.

$$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2),$$

Since $V(0^+) = 0 \text{ V}$, we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is $i_L(0^+) = 0 \text{ A}$, which can be used to obtain $\frac{dV}{dt}(0^+)$.

$$i_L(0^+) = I_0 - \frac{1}{R} V(0^+) - C \frac{dV}{dt}(0^+) = 0 \text{ A, which gives}$$

Parallel RLC circuit

As $t \rightarrow \infty$, $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$.

$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2)$,

Since $V(0^+) = 0 \text{ V}$, we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is $i_L(0^+) = 0 \text{ A}$, which can be used to obtain $\frac{dV}{dt}(0^+)$.

$i_L(0^+) = I_0 - \frac{1}{R} V(0^+) - C \frac{dV}{dt}(0^+) = 0 \text{ A}$, which gives

$$(A/\tau_1) + (B/\tau_2) = -I_0/C. \quad (2)$$

Parallel RLC circuit

As $t \rightarrow \infty$, $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$.

$$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2),$$

Since $V(0^+) = 0 \text{ V}$, we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is $i_L(0^+) = 0 \text{ A}$, which can be used to obtain $\frac{dV}{dt}(0^+)$.

$$i_L(0^+) = I_0 - \frac{1}{R} V(0^+) - C \frac{dV}{dt}(0^+) = 0 \text{ A, which gives}$$

$$(A/\tau_1) + (B/\tau_2) = -I_0/C. \quad (2)$$

From (1) and (2), we get the values of A and B , and

$$V(t) = -3.3 [\exp(-t/\tau_1) - \exp(-t/\tau_2)] \text{ V}. \quad (3)$$

(SEQUEL file: ee101_rlc_1.sqproj)

Parallel RLC circuit

As $t \rightarrow \infty$, $V = L \frac{di_L}{dt} = 0 \text{ V} \Rightarrow V(\infty) = 0 \text{ V}$.

$$\Rightarrow V(t) = A \exp(-t/\tau_1) + B \exp(-t/\tau_2),$$

Since $V(0^+) = 0 \text{ V}$, we have,

$$A + B = 0. \quad (1)$$

Our other initial condition is $i_L(0^+) = 0 \text{ A}$, which can be used to obtain $\frac{dV}{dt}(0^+)$.


$$i_L(0^+) = I_0 - \frac{1}{R} V(0^+) - C \frac{dV}{dt}(0^+) = 0 \text{ A, which gives}$$

$$(A/\tau_1) + (B/\tau_2) = -I_0/C. \quad (2)$$


From (1) and (2), we get the values of A and B , and

$$V(t) = -3.3 [\exp(-t/\tau_1) - \exp(-t/\tau_2)] \text{ V}. \quad (3)$$


(SEQUEL file: ee101_rlc_1.sqproj)

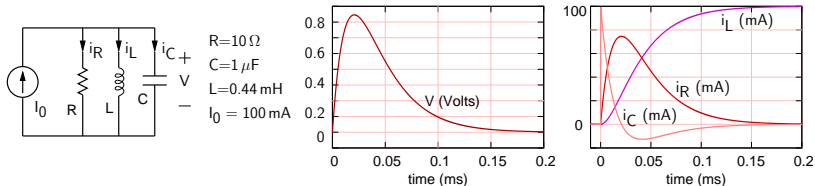

Series RLC circuit: home work

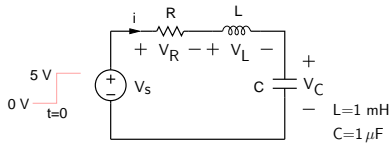


Series RLC circuit: home work

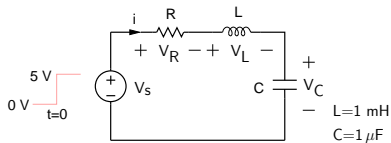


(a) Show that the condition for critically damped response is $R = 63.2 \Omega$.

Series RLC circuit: home work

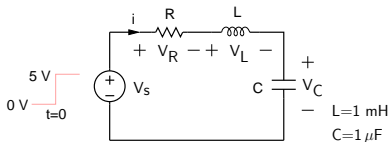


- (a) Show that the condition for critically damped response is $R = 63.2 \Omega$.
- (b) For $R = 20 \Omega$, derive expressions for $i(t)$ and $V_L(t)$ for $t > 0$ (Assume that $V_C(0^-) = 0 \text{ V}$ and $i_L(0^-) = 0 \text{ A}$). Plot them versus time.

Series RLC circuit: home work

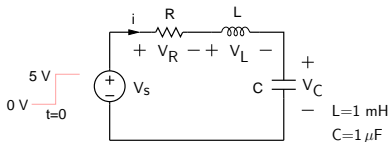


- (a) Show that the condition for critically damped response is $R = 63.2 \Omega$.
- (b) For $R = 20 \Omega$, derive expressions for $i(t)$ and $V_L(t)$ for $t > 0$ (Assume that $V_C(0^-) = 0 \text{ V}$ and $i_L(0^-) = 0 \text{ A}$). Plot them versus time.
- (c) Repeat (b) for $R = 100 \Omega$.

Series RLC circuit: home work

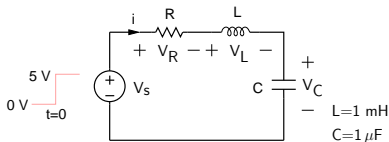

- (a) Show that the condition for critically damped response is $R = 63.2 \Omega$.
- (b) For $R = 20 \Omega$, derive expressions for $i(t)$ and $V_L(t)$ for $t > 0$ (Assume that $V_C(0^-) = 0 \text{ V}$ and $i_L(0^-) = 0 \text{ A}$). Plot them versus time.
- (c) Repeat (b) for $R = 100 \Omega$.
- (d) Compare your results with the following plots.
(SEQUEL file: ee101_rlc_2.sqproj)

Series RLC circuit: home work

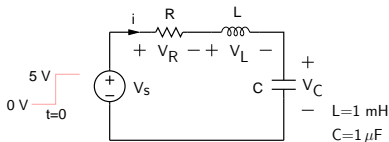

- Show that the condition for critically damped response is $R = 63.2\text{ }\Omega$.
- For $R = 20\text{ }\Omega$, derive expressions for $i(t)$ and $V_L(t)$ for $t > 0$ (Assume that $V_C(0^-) = 0\text{ V}$ and $i_L(0^-) = 0\text{ A}$). Plot them versus time.
- Repeat (b) for $R = 100\text{ }\Omega$.
- Compare your results with the following plots.
(SEQUEL file: ee101_r1c_2.sqproj)

