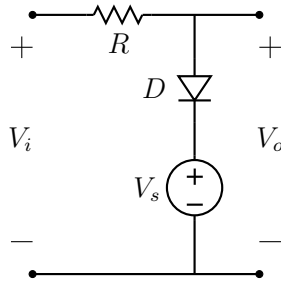


## ee101\_diode\_clipper\_1.sqproj



In the shunt clipper circuit shown in the figure,  $V_s$  is a DC voltage. The diode conducts if  $V_i > V_s + V_{\text{on}}$ , where  $V_{\text{on}} \approx 0.7\text{ V}$  for a silicon diode. In this case, the output voltage is constant,  $V_o = V_s + V_{\text{on}}$ . For  $V_i < V_s + V_{\text{on}}$ , the diode does not conduct, there is no voltage drop across  $R$ , and  $V_o = V_i$ .

The  $V_o$  versus  $V_i$  characteristic for this circuit can be obtained by

- (a) applying a DC voltage at the input, varying it from  $V_{\text{start}}$  to  $V_{\text{end}}$ , and plotting  $V_o$  versus  $V_i$ , or
- (b) applying a periodic input voltage (say, a sinusoidal or triangular voltage), simulating for one cycle, and then plotting  $V_o(t)$  versus  $V_i(t)$ .

### Exercise Set

1. For  $-5\text{ V} < V_i < +5\text{ V}$ , sketch  $V_o$  versus  $V_i$  for  $R = 1\text{ k}\Omega$  and  $V_s = +2, 0, -2\text{ V}$ . Verify your result by simulation in each case.
2. Sketch  $V_o(t)$  for the three cases in (1) if  $V_i(t)$  is a triangular voltage going from  $-5\text{ V}$  to  $+5\text{ V}$ , with frequency  $f = 100\text{ Hz}$ . Verify by simulation.