

Wave Shaping Circuits with Diodes

Aim: To study clipping and clamping circuits.

Part I: Clipping Circuit 1

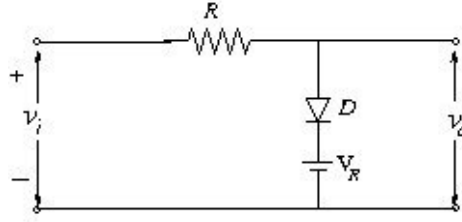


Figure 1(a)

- (a) Analyse the circuit of Fig. 1(a), and plot V_o versus V_i for $-5V < V_i < 5V$. Assume the diode voltage drop to be $0.7V$ when conducting.
- (b) Using the result of (a), plot the waveform $V_o(t)$ versus time for a triangular input voltage $V_i(t)$, varying from $-5V$ to $+5V$, with a frequency of $1kHz$.
- (c) Simulate the circuit and verify your answers of (a) and (b).

Part II: Clipping Circuit 2

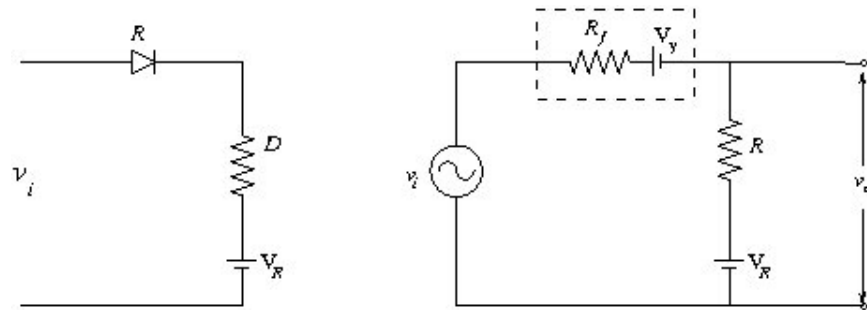


Figure 2(a)

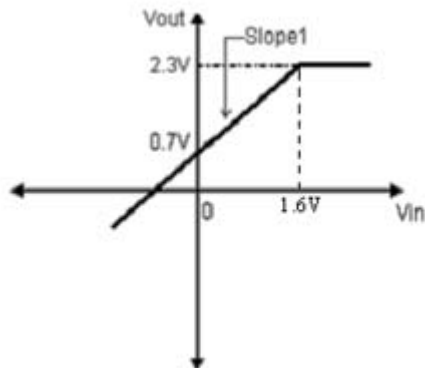


Figure 3 (a)

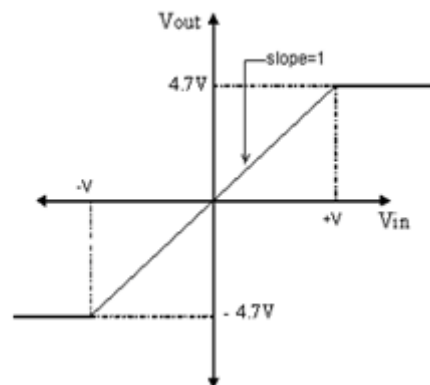


Figure 3 (b)

- Analyse the circuit of Fig. 2 (a), and plot V_o versus V_i for $-5V < V_i < 5V$. Assume the diode voltage drop to be $0.7V$ when conducting.
- Using the result of (a), plot the waveform $V_o(t)$ versus time for a triangular input voltage $V_i(t)$, varying from $-5V$ to $+5V$, with a frequency of 1 kHz .
- Simulate the circuit and verify your answers of (a) and (b).
- Design and simulate the circuit shown in Fig. 3 (a) and 3 (b).

Part III: Clamping Circuit

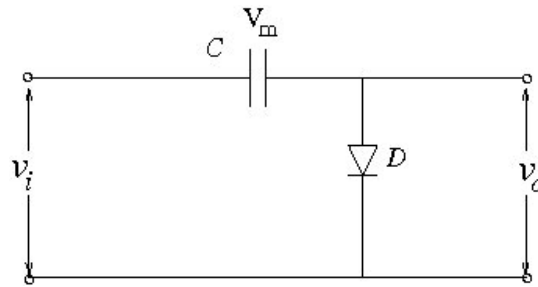


Figure 4 (a)

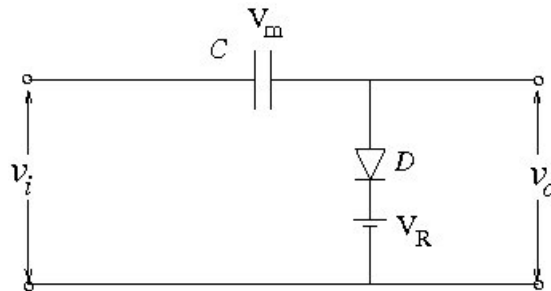


Figure 4 (b)

- Analyse the circuit of Fig. 4 (a), and plot V_o versus V_i for $-5V < V_i < 5V$. Assume the diode voltage drop to be $0.7V$ when conducting.
- Using the result of (a), plot the waveform $V_o(t)$ versus time $V_i(t)$
- Plot the waveform $V_o(t)$ versus time for a sinusoidal input voltage $V_i(t)$, varying from $-5V$ to $+5V$, with a frequency of 1 kHz .
- Simulate the circuit and verify your answers of (a) and (b).
- Repeat (a) – (d) for Fig. 4 (b) with $V_R = +1V$ and $-1V$.