




**M. B. Patil**


mbpatil@ee.iitb.ac.in

Department of Electrical Engineering  
Indian Institute of Technology Bombay

# Capacitors

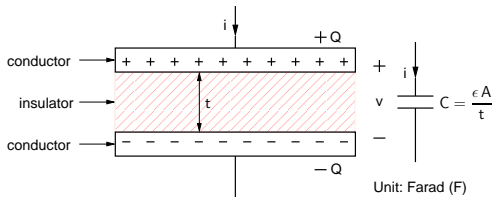


# Capacitors

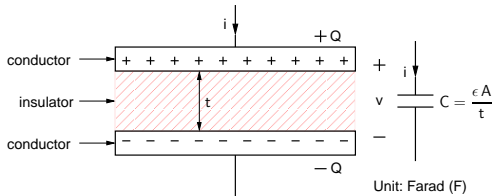


- \* In practice, capacitors are available in a wide range of shapes and values, and they differ significantly in the way they are fabricated.  
(<http://en.wikipedia.org/wiki/Capacitor>)

# Capacitors

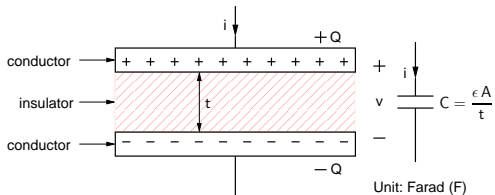

- \* In practice, capacitors are available in a wide range of shapes and values, and they differ significantly in the way they are fabricated. (<http://en.wikipedia.org/wiki/Capacitor>)
- \* To make  $C$  larger, we need (a) high  $\epsilon$ , (b) large area, (c) small thickness.


# Capacitors

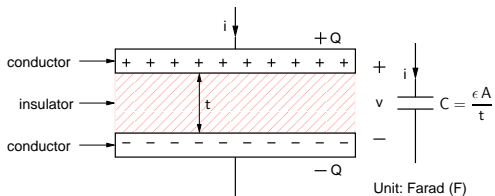

- \* In practice, capacitors are available in a wide range of shapes and values, and they differ significantly in the way they are fabricated. (<http://en.wikipedia.org/wiki/Capacitor>)
- \* To make  $C$  larger, we need (a) high  $\epsilon$ , (b) large area, (c) small thickness.
- \* For a constant capacitance,

$$Q(t) = C v(t), \quad \frac{dQ}{dt} = C \frac{dv}{dt}, \text{ i.e., } i(t) = C \frac{dv}{dt}.$$


# Capacitors

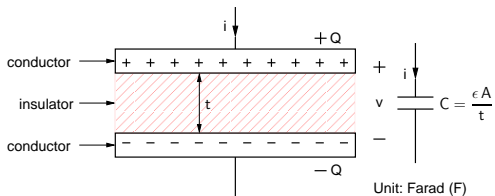

- \* In practice, capacitors are available in a wide range of shapes and values, and they differ significantly in the way they are fabricated.  
(<http://en.wikipedia.org/wiki/Capacitor>)
- \* To make  $C$  larger, we need (a) high  $\epsilon$ , (b) large area, (c) small thickness.
- \* For a constant capacitance,  
$$Q(t) = C v(t), \quad \frac{dQ}{dt} = C \frac{dv}{dt}, \text{ i.e., } i(t) = C \frac{dv}{dt}.$$
- \* If  $v = \text{constant}$ ,  $i = 0$ , i.e., a capacitor behaves like an open circuit in DC conditions as one would expect from two conducting plates separated by an insulator.

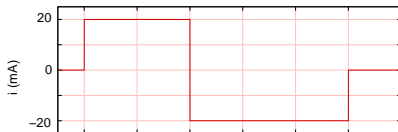
# Example

Plot  $v$ ,  $p$ , and  $W$  versus time  
for the given source current.  
Assume  $v(0) = 0$  V,  $C = 5$  mF.


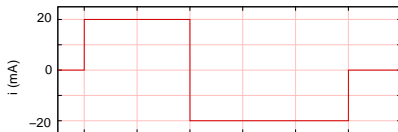
# Example

Plot  $v$ ,  $p$ , and  $W$  versus time  
for the given source current.  
Assume  $v(0) = 0$  V,  $C = 5$  mF.



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$




# Example

Plot  $v$ ,  $p$ , and  $W$  versus time  
for the given source current.  
Assume  $v(0) = 0$  V,  $C = 5$  mF.



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

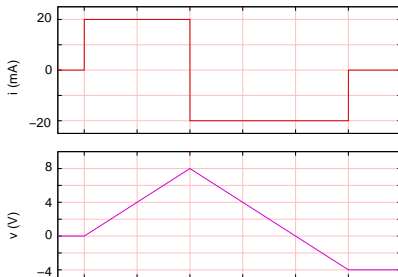

# Example


Plot  $v$ ,  $p$ , and  $W$  versus time for the given source current. Assume  $v(0) = 0$  V,  $C = 5$  mF.



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$p(t) = v(t) \times i(t)$$

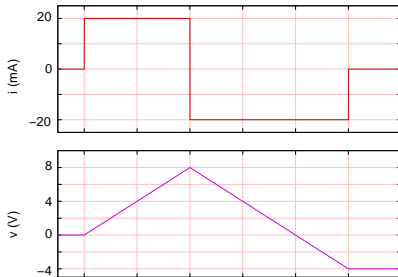

# Example


Plot  $v$ ,  $p$ , and  $W$  versus time  
for the given source current.  
Assume  $v(0) = 0$  V,  $C = 5$  mF.



$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$p(t) = v(t) \times i(t)$$

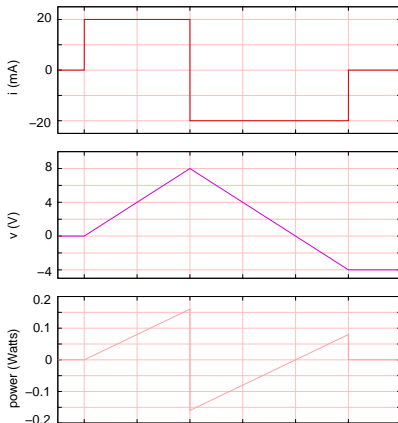

# Example

Plot  $v$ ,  $p$ , and  $W$  versus time for the given source current. Assume  $v(0) = 0$  V,  $C = 5$  mF.




$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$p(t) = v(t) \times i(t)$$

$$W(t) = \int p(t) dt$$

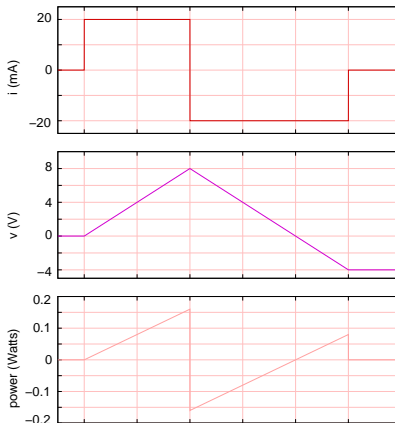

# Example

Plot  $v$ ,  $p$ , and  $W$  versus time  
for the given source current.

Assume  $v(0) = 0$  V,  $C = 5$  mF.




$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$

$$p(t) = v(t) \times i(t)$$

$$W(t) = \int p(t) dt$$

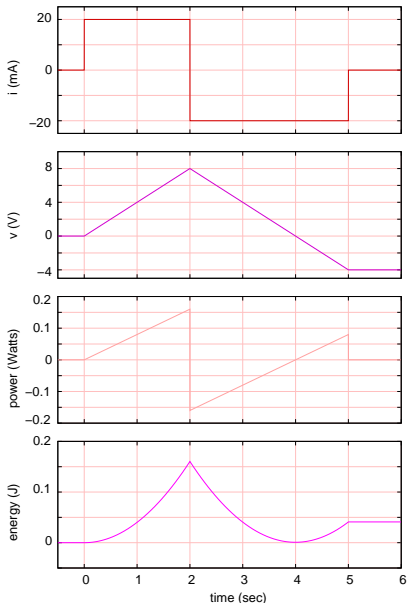

# Example

Plot  $v$ ,  $p$ , and  $W$  versus time  
for the given source current.

Assume  $v(0) = 0$  V,  $C = 5$  mF.




$$i(t) = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int i(t) dt$$


$$p(t) = v(t) \times i(t)$$


$$W(t) = \int p(t) dt$$
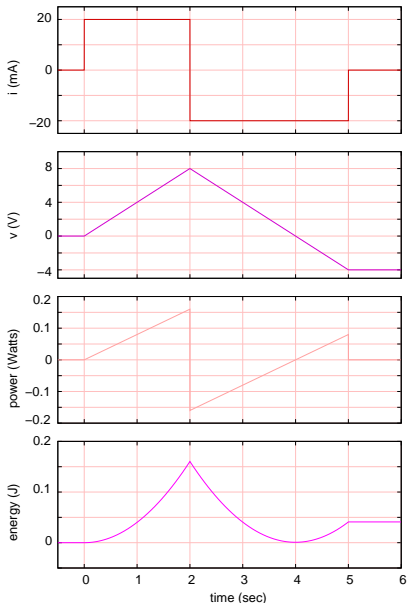
$$\begin{aligned} W(t) &= \int p(t) dt \\ &= C \int v \frac{dv}{dt} dt \\ &= C \int v dv \\ &= \frac{1}{2} C v^2 \end{aligned}$$




# Home work

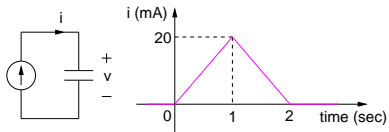

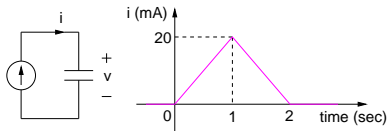


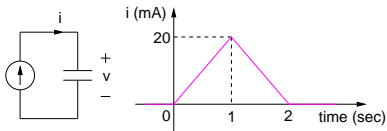- \* For the given source current, plot  $v(t)$ ,  $p(t)$ , and  $W(t)$ , assuming  $v(0) = 0$  V,  $C = 5$  mF.






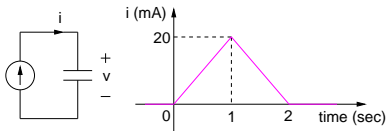
- \* For the given source current, plot  $v(t)$ ,  $p(t)$ , and  $W(t)$ , assuming  $v(0) = 0$  V,  $C = 5$  mF.
- \* Verify your results with SEQUEL.



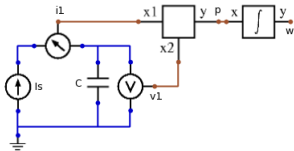
- \* For the given source current, plot  $v(t)$ ,  $p(t)$ , and  $W(t)$ , assuming  $v(0) = 0$  V,  $C = 5$  mF.
- \* Verify your results with SEQUEL.  
(file: ee101\_cap\_power.sqproj)



# Inductors

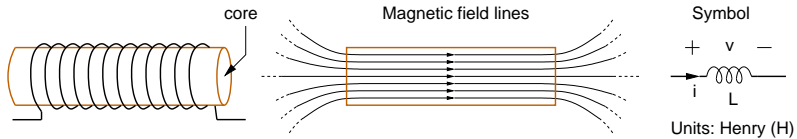


# Inductors

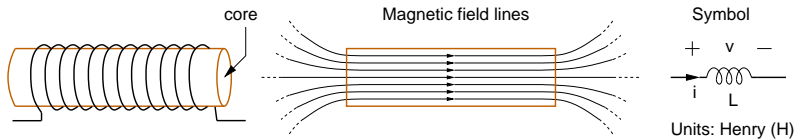

\* An inductor is basically a conducting coil wound around a "core."

# Inductors

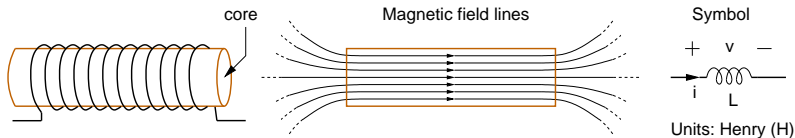


\* An inductor is basically a conducting coil wound around a “core.”

$$* \quad V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} [(\mu H) A] = N \frac{d}{dt} [(\mu N i) A].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$

$$\Rightarrow L = \mu N^2 A = \mu_r \mu_0 N^2 A.$$

# Inductors

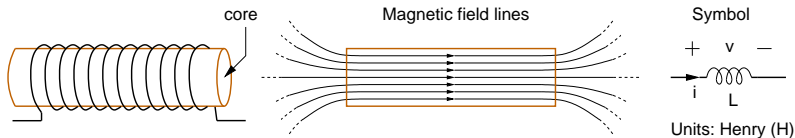

\* An inductor is basically a conducting coil wound around a “core.”


$$* \quad V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} [(\mu H) A] = N \frac{d}{dt} [(\mu N i) A].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$

$$\Rightarrow L = \mu N^2 A = \mu_r \mu_0 N^2 A.$$

\* To make  $L$  larger, we need (a) high  $\mu_r$ , (b) large area, (c) large number of turns.

# Inductors

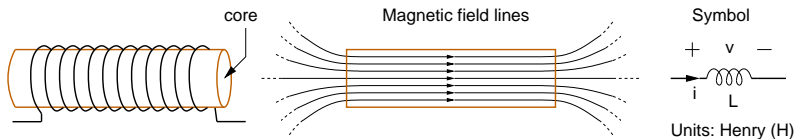

\* An inductor is basically a conducting coil wound around a “core.”

$$* V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} [(\mu H) A] = N \frac{d}{dt} [(\mu N i) A].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$


$$\Rightarrow L = \mu N^2 A = \mu_r \mu_0 N^2 A.$$

\* To make  $L$  larger, we need (a) high  $\mu_r$ , (b) large area, (c) large number of turns.

\* For 99.8 % pure iron,  $\mu_r \simeq 5,000$ .

For “supermalloy” (Ni: 79 %, Mo: 5 %, Fe):  $\mu_r \simeq 10^6$ .

# Inductors

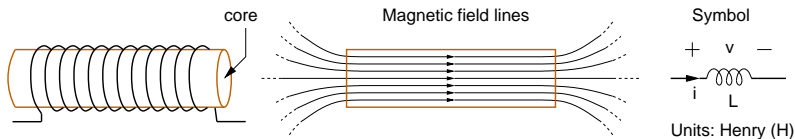

\* An inductor is basically a conducting coil wound around a "core."

$$* V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} [(\mu H) A] = N \frac{d}{dt} [(\mu N i) A].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$

$$\Rightarrow L = \mu N^2 A = \mu_r \mu_0 N^2 A.$$

\* To make  $L$  larger, we need (a) high  $\mu_r$ , (b) large area, (c) large number of turns.


\* For 99.8 % pure iron,  $\mu_r \simeq 5,000$ .

For "supermalloy" (Ni: 79 %, Mo: 5 %, Fe):  $\mu_r \simeq 10^6$ .

\* If  $i = \text{constant}$ ,  $v = 0$ , i.e., an inductor behaves like a short circuit in DC conditions as one would expect from a highly conducting coil.



# Inductors

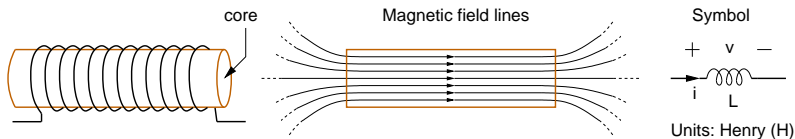

- \* An inductor is basically a conducting coil wound around a “core.”


$$* \quad V = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathbf{B} \cdot \mathbf{A}) = N \frac{d}{dt} [(\mu H) A] = N \frac{d}{dt} [(\mu N i) A].$$

$$\text{Compare with } v = L \frac{di}{dt}.$$


$$\Rightarrow L = \mu N^2 A = \mu_r \mu_0 N^2 A.$$

- \* To make  $L$  larger, we need (a) high  $\mu_r$ , (b) large area, (c) large number of turns.
- \* For 99.8 % pure iron,  $\mu_r \simeq 5,000$ .  
For "supermalloy" (Ni: 79 %, Mo: 5 %, Fe):  $\mu_r \simeq 10^6$ .
- \* If  $i = \text{constant}$ ,  $v = 0$ , i.e., an inductor behaves like a short circuit in DC conditions as one would expect from a highly conducting coil.
- \* Note:  $B = \mu H$  is an approximation. In practice,  $B$  may be a nonlinear function of  $H$ , depending on the core material.


## RC circuits with DC sources

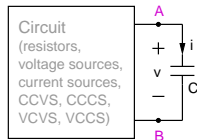

## RC circuits with DC sources

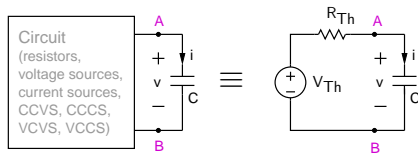


## RC circuits with DC sources

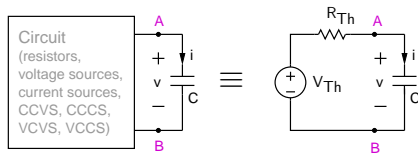

- \* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .


## RC circuits with DC sources

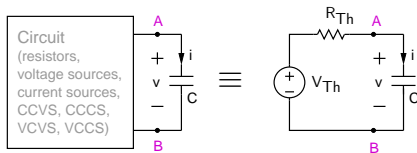

\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$ .

## RC circuits with DC sources

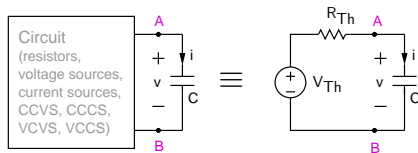

\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .


\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$ .

\* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant."}$$

$$\rightarrow v^{(h)} = K \exp(-t/\tau).$$

## RC circuits with DC sources

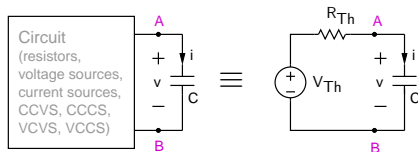

\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$ .


\* Homogeneous solution:

$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant."}$$

$$\rightarrow v^{(h)} = K \exp(-t/\tau).$$

\* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $i = 0$ , and we get  $v^{(p)} = V_{Th}$  as a particular solution (which happens to be simply a constant).


## RC circuits with DC sources

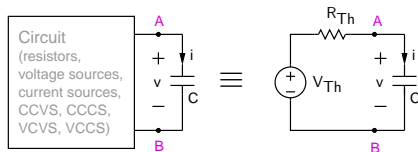

- \* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .
- \* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$ .
- \* Homogeneous solution:  
$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant."}$$
$$\rightarrow v^{(h)} = K \exp(-t/\tau).$$
- \* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $i = 0$ , and we get  $v^{(p)} = V_{Th}$  as a particular solution (which happens to be simply a constant).
- \*  $v = v^{(h)} + v^{(p)} = K \exp(-t/\tau) + V_{Th}$ .




## RC circuits with DC sources

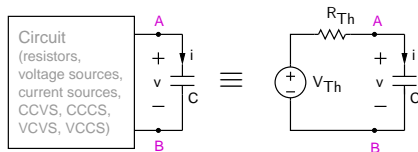


- \* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .
- \* KVL:  $V_{Th} = R_{Th} i + v \rightarrow V_{Th} = R_{Th} C \frac{dv}{dt} + v$ .
- \* Homogeneous solution:  
$$\frac{dv}{dt} + \frac{1}{\tau} v = 0, \text{ where } \tau = R_{Th} C \text{ is the "time constant."}$$
$$\rightarrow v^{(h)} = K \exp(-t/\tau).$$
- \* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $i = 0$ , and we get  $v^{(p)} = V_{Th}$  as a particular solution (which happens to be simply a constant).
- \*  $v = v^{(h)} + v^{(p)} = K \exp(-t/\tau) + V_{Th}$ .
- \* In general,  $v(t) = A \exp(-t/\tau) + B$ , where  $A$  and  $B$  can be obtained from known conditions on  $v$ .
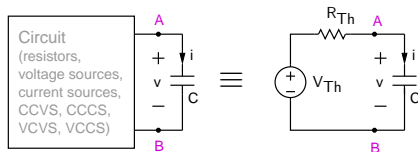
## RC circuits with DC sources (continued)



- \* If all sources are DC (constant), we have  $v(t) = A \exp(-t/\tau) + B$ ,  $\tau = RC$ .
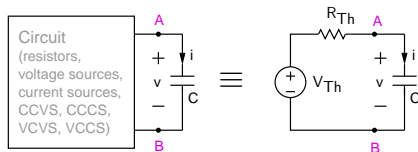
## RC circuits with DC sources (continued)




- \* If all sources are DC (constant), we have

$$v(t) = A \exp(-t/\tau) + B, \tau = RC.$$


$$* i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left( -\frac{1}{\tau} \right) \equiv A' \exp(-t/\tau).$$
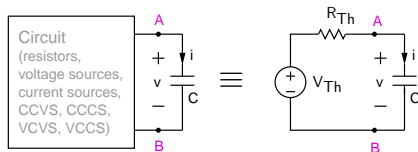
## RC circuits with DC sources (continued)




- \* If all sources are DC (constant), we have  $v(t) = A \exp(-t/\tau) + B$ ,  $\tau = RC$ .
- \*  $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left( -\frac{1}{\tau} \right) \equiv A' \exp(-t/\tau)$ .
- \* As  $t \rightarrow \infty$ ,  $i \rightarrow 0$ , i.e., the capacitor behaves like an open circuit since all derivatives vanish.
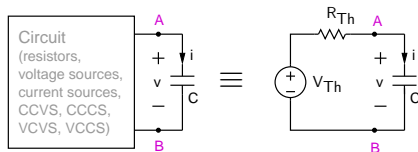
## RC circuits with DC sources (continued)




- \* If all sources are DC (constant), we have  $v(t) = A \exp(-t/\tau) + B$ ,  $\tau = RC$ .
- \*  $i(t) = C \frac{dv}{dt} = C \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$ .
- \* As  $t \rightarrow \infty$ ,  $i \rightarrow 0$ , i.e., the capacitor behaves like an open circuit since all derivatives vanish.
- \* Since the circuit in the black box is linear, *any* variable (current or voltage) in the circuit can be expressed as  $x(t) = K_1 \exp(-t/\tau) + K_2$ , where  $K_1$  and  $K_2$  can be obtained from suitable conditions on  $x(t)$ .


## RL circuits with DC sources

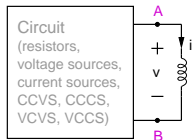

## RL circuits with DC sources

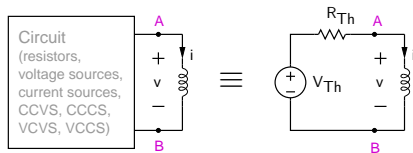


## RL circuits with DC sources

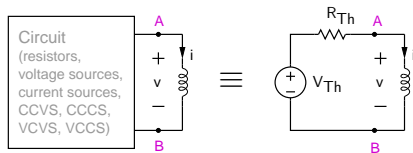

- \* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .




## RL circuits with DC sources

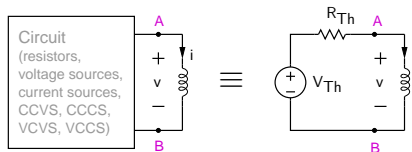

\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .

## RL circuits with DC sources

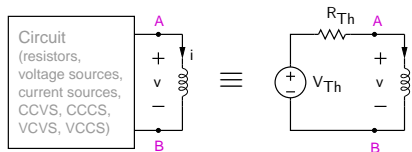

\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .


\* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .

\* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

## RL circuits with DC sources

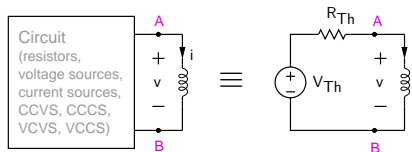

\* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

\* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .


\* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

\* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $v = 0$ , and we get  $i^{(p)} = V_{Th}/R_{Th}$  as a particular solution (which happens to be simply a constant).

## RL circuits with DC sources

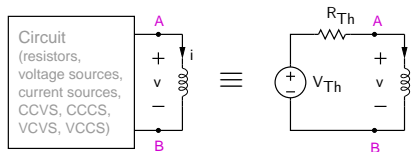

- \* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

- \* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .


- \* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$

$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

- \* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $v = 0$ , and we get  $i^{(p)} = V_{Th}/R_{Th}$  as a particular solution (which happens to be simply a constant).

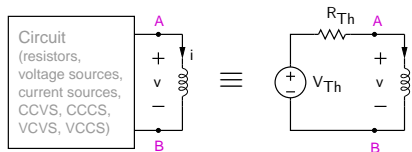- \*  $i = i^{(h)} + i^{(p)} = K \exp(-t/\tau) + V_{Th}/R_{Th}$ .



- \* If all sources are DC (constant),  $V_{Th} = \text{constant}$ .

- \* KVL:  $V_{Th} = R_{Th} i + L \frac{di}{dt}$ .

- \* Homogeneous solution:

$$\frac{di}{dt} + \frac{1}{\tau} i = 0, \text{ where } \tau = L/R_{Th}$$


$$\rightarrow i^{(h)} = K \exp(-t/\tau).$$

- \* Particular solution is a specific function that satisfies the differential equation. We know that all time derivatives will vanish as  $t \rightarrow \infty$ , making  $v = 0$ , and we get  $i^{(p)} = V_{Th}/R_{Th}$  as a particular solution (which happens to be simply a constant).

- \*  $i = i^{(h)} + i^{(p)} = K \exp(-t/\tau) + V_{Th}/R_{Th}$ .


- \* In general,  $i(t) = A \exp(-t/\tau) + B$ , where  $A$  and  $B$  can be obtained from known conditions on  $i$ .
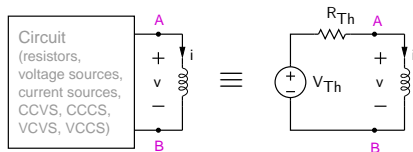
## RL circuits with DC sources (continued)



- \* If all sources are DC (constant), we have  $i(t) = A \exp(-t/\tau) + B$ ,  $\tau = L/R$ .
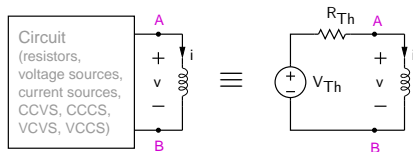
## RL circuits with DC sources (continued)




- \* If all sources are DC (constant), we have

$$i(t) = A \exp(-t/\tau) + B, \tau = L/R.$$

- \* 
$$v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left( -\frac{1}{\tau} \right) \equiv A' \exp(-t/\tau).$$

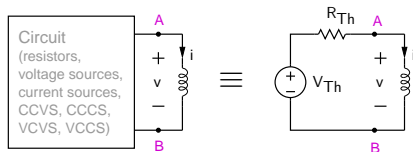
## RL circuits with DC sources (continued)



- \* If all sources are DC (constant), we have  $i(t) = A \exp(-t/\tau) + B$ ,  $\tau = L/R$ .
- \*  $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$ .
- \* As  $t \rightarrow \infty$ ,  $v \rightarrow 0$ , i.e., the inductor behaves like a short circuit since all derivatives vanish.



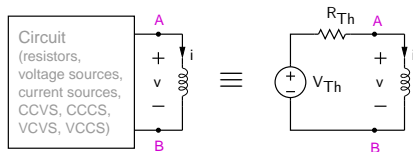
## RL circuits with DC sources (continued)




- \* If all sources are DC (constant), we have  $i(t) = A \exp(-t/\tau) + B$ ,  $\tau = L/R$ .
- \*  $v(t) = L \frac{di}{dt} = L \times A \exp(-t/\tau) \left(-\frac{1}{\tau}\right) \equiv A' \exp(-t/\tau)$ .
- \* As  $t \rightarrow \infty$ ,  $v \rightarrow 0$ , i.e., the inductor behaves like a short circuit since all derivatives vanish.
- \* Since the circuit in the black box is linear, *any* variable (current or voltage) in the circuit can be expressed as  $x(t) = K_1 \exp(-t/\tau) + K_2$ , where  $K_1$  and  $K_2$  can be obtained from suitable conditions on  $x(t)$ .
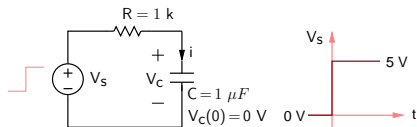
## RC circuits: Can $V_c$ change “suddenly?”



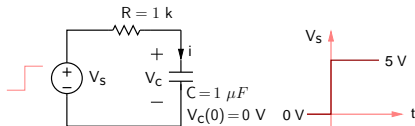
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
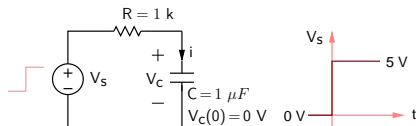
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in  $1\text{ }\mu\text{s}$  at a constant rate of  $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$ ?
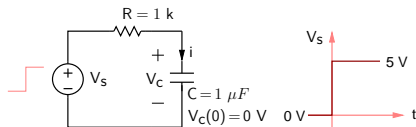
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in  $1\text{ }\mu\text{s}$  at a constant rate of  $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$ ?
- \*  $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}.$
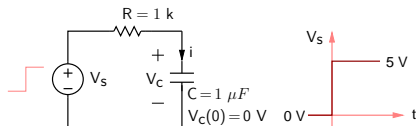
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in  $1\text{ }\mu\text{s}$  at a constant rate of  $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$ ?
- \*  $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$ .
- \* With  $i = 1\text{ A}$ , the voltage drop across  $R$  would be 1000 V! Not allowed by KVL.
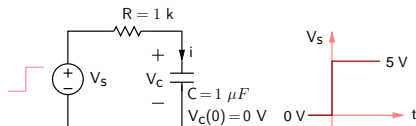
## RC circuits: Can $V_C$ change “suddenly?”



- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in  $1\text{ }\mu\text{s}$  at a constant rate of  $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$ ?
- \*  $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$ .
- \* With  $i = 1\text{ A}$ , the voltage drop across  $R$  would be 1000 V! Not allowed by KVL.
- \* We conclude that  $V_C(0^+) = V_C(0^-) \Rightarrow$  A capacitor does not allow abrupt changes in  $V_C$  if there is a finite resistance in the circuit.
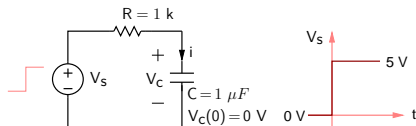
## RC circuits: Can $V_C$ change “suddenly?”




- \*  $V_s$  changes from 0 V (at  $t = 0^-$ ), to 5 V (at  $t = 0^+$ ). As a result of this change,  $V_C$  will rise. How fast can  $V_C$  change?
- \* For example, what would happen if  $V_C$  changes by 1 V in 1  $\mu\text{s}$  at a constant rate of  $1\text{ V}/1\text{ }\mu\text{s} = 10^6\text{ V/s}$ ?
- \*  $i = C \frac{dV_C}{dt} = 1\text{ }\mu\text{F} \times 10^6 \frac{\text{V}}{\text{s}} = 1\text{ A}$ .
- \* With  $i = 1\text{ A}$ , the voltage drop across  $R$  would be 1000 V! Not allowed by KVL.
- \* We conclude that  $V_C(0^+) = V_C(0^-) \Rightarrow$  A capacitor does not allow abrupt changes in  $V_C$  if there is a finite resistance in the circuit.
- \* Similarly, an inductor does not allow abrupt changes in  $i_L$ .


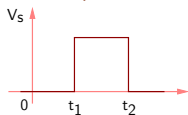
## Analysis of $RC/RL$ circuits with a piece-wise constant source

- \* Identify intervals in which the source voltages/currents are constant.  
For example,



$$(1) t < t_1$$


$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

## Analysis of $RC/RL$ circuits with a piece-wise constant source

- \* Identify intervals in which the source voltages/currents are constant.

For example,

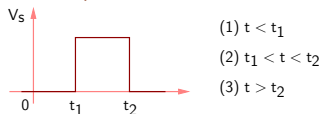

- \* For *any* quantity of interest  $x(t)$ , write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$


$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

## Analysis of $RC/RL$ circuits with a piece-wise constant source

- \* Identify intervals in which the source voltages/currents are constant.

For example,

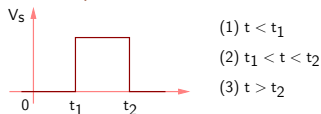


- \* For *any* quantity of interest  $x(t)$ , write general expressions such as,  
$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$
$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$
$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$
- \* Work out suitable conditions on  $x(t)$  at specific time points using

## Analysis of $RC/RL$ circuits with a piece-wise constant source

- \* Identify intervals in which the source voltages/currents are constant.

For example,

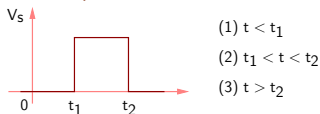

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- \* For *any* quantity of interest  $x(t)$ , write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- \* Work out suitable conditions on  $x(t)$  at specific time points using


- (a) If the source voltage/current has not changed for a “long” time (long compared to  $\tau$ ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$

## Analysis of $RC/RL$ circuits with a piece-wise constant source

- \* Identify intervals in which the source voltages/currents are constant.

For example,

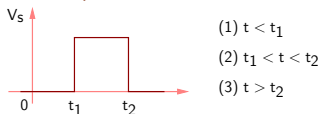

$$(1) t < t_1$$

$$(2) t_1 < t < t_2$$

$$(3) t > t_2$$

- \* For *any* quantity of interest  $x(t)$ , write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- \* Work out suitable conditions on  $x(t)$  at specific time points using

- (a) If the source voltage/current has not changed for a “long” time (long compared to  $\tau$ ), all derivatives are zero.

$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$


- (b) When a source voltage (or current) changes, say, at  $t = t_0$ ,  $V_C(t)$  or  $i_L(t)$  cannot change abruptly, i.e.,

$$V_C(t_0^+) = V_C(t_0^-), \text{ and } i_L(t_0^+) = i_L(t_0^-).$$

## Analysis of $RC/RL$ circuits with a piece-wise constant source

- \* Identify intervals in which the source voltages/currents are constant.

For example,

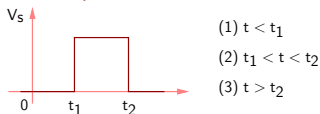

- \* For *any* quantity of interest  $x(t)$ , write general expressions such as,

$$x(t) = A_1 \exp(-t/\tau) + B_1, \quad t < t_1,$$

$$x(t) = A_2 \exp(-t/\tau) + B_2, \quad t_1 < t < t_2,$$

$$x(t) = A_3 \exp(-t/\tau) + B_3, \quad t > t_2.$$

- \* Work out suitable conditions on  $x(t)$  at specific time points using
  - (a) If the source voltage/current has not changed for a “long” time (long compared to  $\tau$ ), all derivatives are zero.


$$\Rightarrow i_C = C \frac{dV_C}{dt} = 0, \text{ and } V_L = L \frac{di_L}{dt} = 0.$$

- (b) When a source voltage (or current) changes, say, at  $t = t_0$ ,  $V_C(t)$  or  $i_L(t)$  cannot change abruptly, i.e.,


$$V_C(t_0^+) = V_C(t_0^-), \text{ and } i_L(t_0^+) = i_L(t_0^-).$$

- \* Compute  $A_1, B_1, \dots$  using the conditions on  $x(t)$ .
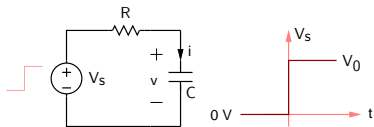
## RC circuits: charging and discharging transients



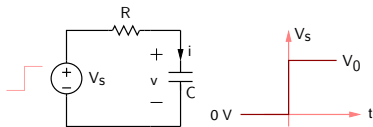
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$


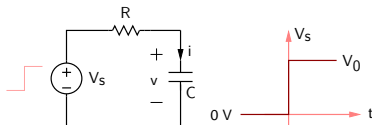
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$


$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$
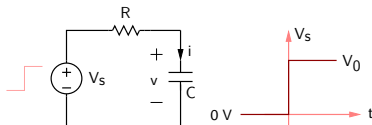
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$
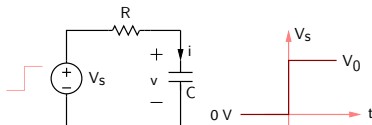
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$

Imposing (1) and (2) on Eq. (A), we get


$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$
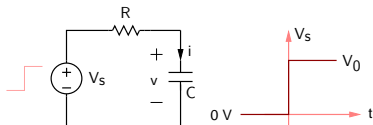
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$


$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

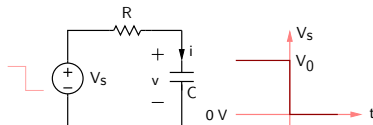
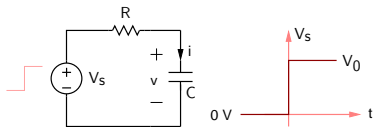
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$


$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

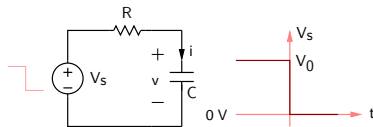

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$
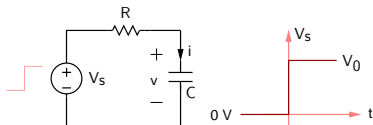
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

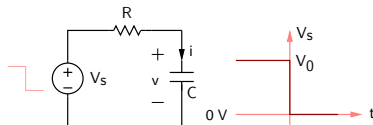

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = V_0$$


$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = 0 \text{ V}$$
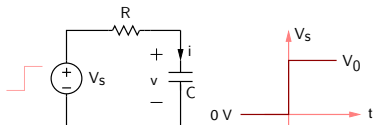
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

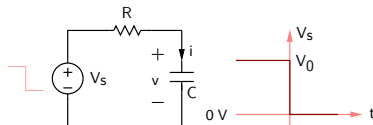

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = 0 \text{ V}$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: V_0 = A + B,$$

$$t \rightarrow \infty: 0 = B.$$

$$\text{i.e., } A = V_0, B = 0$$
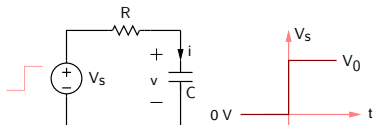
## RC circuits: charging and discharging transients



$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = 0 \text{ V}$$

$$v(0^+) \simeq v(0^-) = 0 \text{ V}$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = V_0$$


Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: 0 = A + B,$$

$$t \rightarrow \infty: V_0 = B.$$

$$\text{i.e., } A = V_0, B = -V_0$$

$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

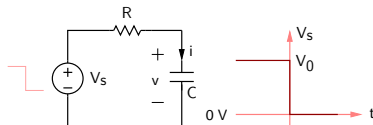

$$\text{Let } v(t) = A \exp(-t/\tau) + B, \quad t > 0 \quad (\text{A})$$

Conditions on  $v(t)$ :

$$(1) \quad v(0^-) = V_s(0^-) = V_0$$

$$v(0^+) \simeq v(0^-) = V_0$$

Note that we need the condition at  $0^+$  (and not at  $0^-$ )

because Eq. (A) applies only for  $t > 0$ .

$$(2) \quad \text{As } t \rightarrow \infty, i \rightarrow 0 \rightarrow v(\infty) = V_s(\infty) = 0 \text{ V}$$

Imposing (1) and (2) on Eq. (A), we get

$$t = 0^+: V_0 = A + B,$$


$$t \rightarrow \infty: 0 = B.$$

$$\text{i.e., } A = V_0, B = 0$$

$$v(t) = V_0 \exp(-t/\tau)$$



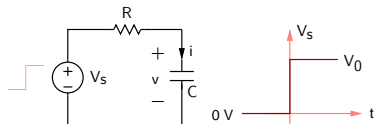
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

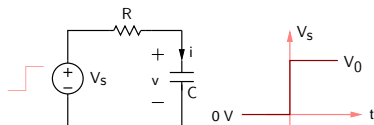
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A) } i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$
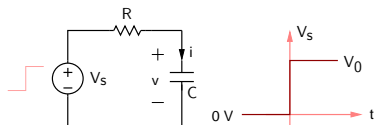
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$

(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .


$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain

$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$
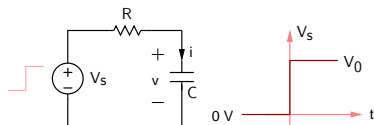
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$


Using these conditions, we obtain
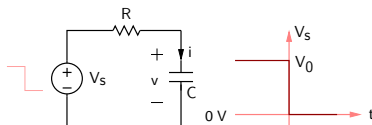
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute  $i(t)$ ,  $t > 0$ .
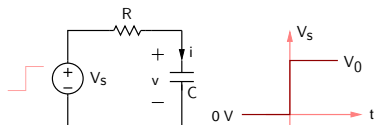
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .

$$t = 0^+: v = 0, V_s = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain

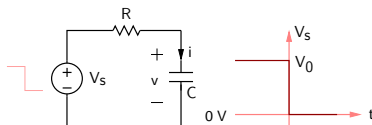
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [\exp(-t/\tau)] \\ &= -\frac{CV_0}{\tau} \exp(-t/\tau) = -\frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$
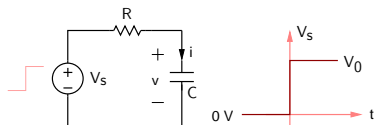
## RC circuits: charging and discharging transients



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [1 - \exp(-t/\tau)] \\ &= \frac{CV_0}{\tau} \exp(-t/\tau) = \frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$


(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .

$$t = 0^+: v = 0, V_S = V_0 \Rightarrow i(0^+) = V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain
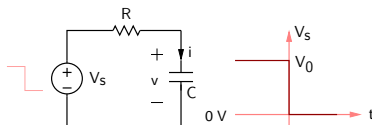
$$A' = \frac{V_0}{R}, B' = 0 \Rightarrow i(t) = \frac{V_0}{R} \exp(-t/\tau)$$



Compute  $i(t)$ ,  $t > 0$ .

$$\begin{aligned} \text{(A)} \quad i(t) &= C \frac{d}{dt} V_0 [\exp(-t/\tau)] \\ &= -\frac{CV_0}{\tau} \exp(-t/\tau) = -\frac{V_0}{R} \exp(-t/\tau) \end{aligned}$$

(B) Let  $i(t) = A' \exp(-t/\tau) + B'$ ,  $t > 0$ .


$$t = 0^+: v = V_0, V_S = 0 \Rightarrow i(0^+) = -V_0/R.$$

$$t \rightarrow \infty: i(t) = 0.$$

Using these conditions, we obtain

$$A' = -\frac{V_0}{R}, B' = 0 \Rightarrow i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

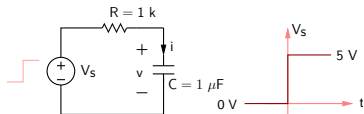
## RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$


$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$
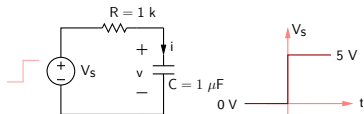
## RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

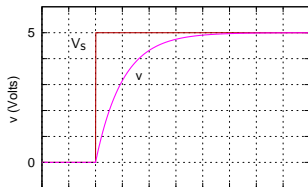




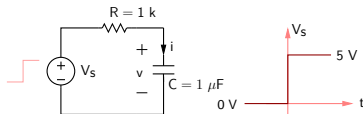
## RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$


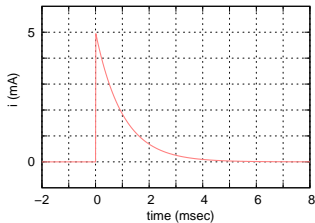
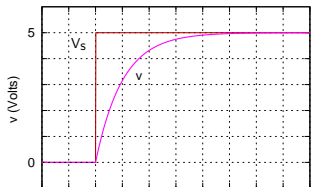

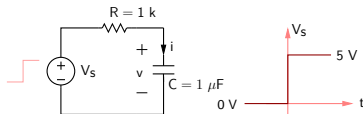
## RC circuits: charging and discharging transients



$$v(t) = V_0 [1 - \exp(-t/\tau)]$$


$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

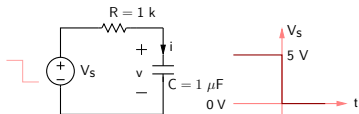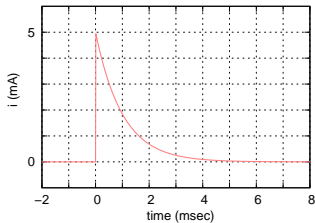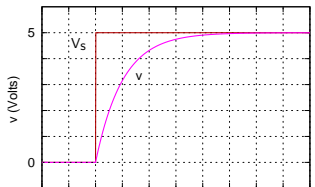

$$v(t) = V_0 \exp(-t/\tau)$$




$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$
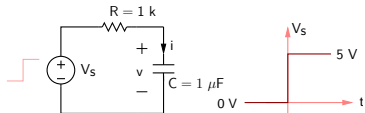
## RC circuits: charging and discharging transients




$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

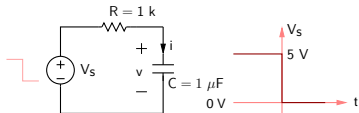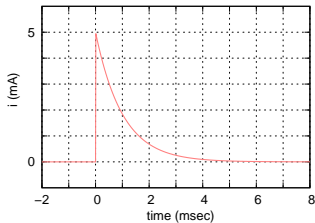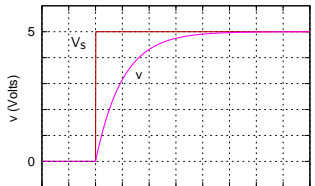


$$v(t) = V_0 \exp(-t/\tau)$$

$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$



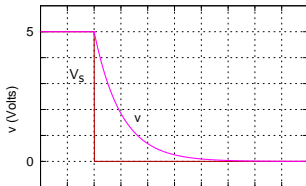

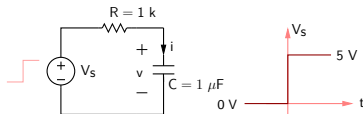
## RC circuits: charging and discharging transients





$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

$$i(t) = \frac{V_0}{R} \exp(-t/\tau)$$

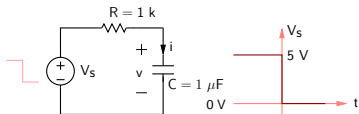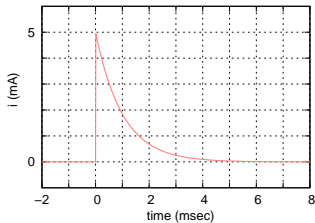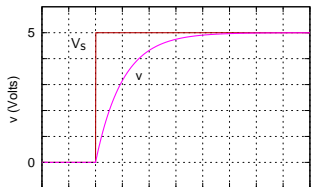

$$v(t) = V_0 \exp(-t/\tau)$$

$$i(t) = -\frac{V_0}{R} \exp(-t/\tau)$$

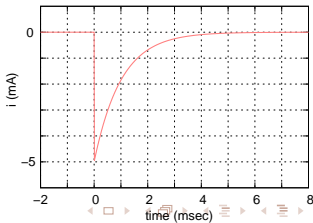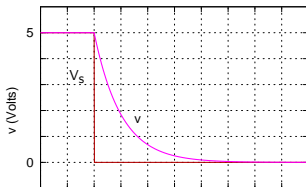

## Significance of the time constant ( $\tau$ )

$x$	$e^{-x}$	$1 - e^{-x}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	$4.9787 \times 10^{-2}$	0.9502
4.0	$1.8315 \times 10^{-2}$	0.9817
5.0	$6.7379 \times 10^{-3}$	0.9933

## Significance of the time constant ( $\tau$ )

$x$	$e^{-x}$	$1 - e^{-x}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	$4.9787 \times 10^{-2}$	0.9502
4.0	$1.8315 \times 10^{-2}$	0.9817
5.0	$6.7379 \times 10^{-3}$	0.9933

\* For  $x = 5$ ,  $e^{-x} \simeq 0$ ,  $1 - e^{-x} \simeq 1$ .


## Significance of the time constant ( $\tau$ )

$x$	$e^{-x}$	$1 - e^{-x}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	$4.9787 \times 10^{-2}$	0.9502
4.0	$1.8315 \times 10^{-2}$	0.9817
5.0	$6.7379 \times 10^{-3}$	0.9933

- \* For  $x = 5$ ,  $e^{-x} \simeq 0$ ,  $1 - e^{-x} \simeq 1$ .
- \* In  $RC$  circuits,  $x = t/\tau \Rightarrow$  When  $t = 5\tau$ , the charging (or discharging) process is almost complete.

## Significance of the time constant ( $\tau$ )


$x$	$e^{-x}$	$1 - e^{-x}$
0.0	1.0	0.0
1.0	0.3679	0.6321
2.0	0.1353	0.8647
3.0	$4.9787 \times 10^{-2}$	0.9502
4.0	$1.8315 \times 10^{-2}$	0.9817
5.0	$6.7379 \times 10^{-3}$	0.9933

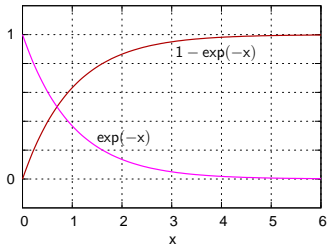



- \* For  $x = 5$ ,  $e^{-x} \simeq 0$ ,  $1 - e^{-x} \simeq 1$ .
- \* In  $RC$  circuits,  $x = t/\tau \Rightarrow$  When  $t = 5\tau$ , the charging (or discharging) process is almost complete.



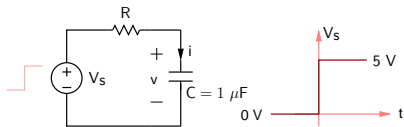
## RC circuits: charging and discharging transients





$$v(t) = V_0 [1 - \exp(-t/\tau)]$$

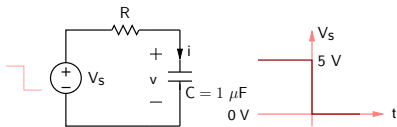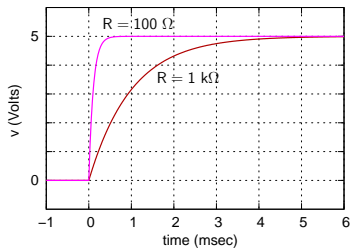

$$v(t) = V_0 \exp(-t/\tau)$$

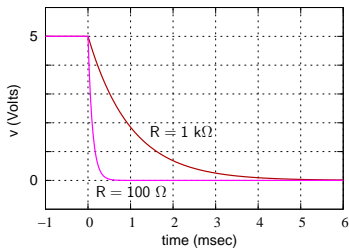

## *RL* circuit: example

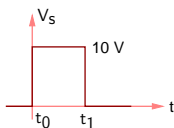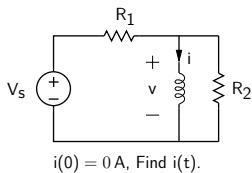

$$R_1 = 10 \Omega$$



$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

## RL circuit: example

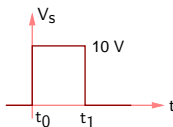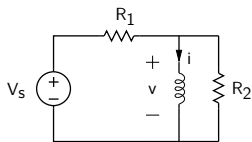

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$ , Find  $i(t)$ .



There are three intervals of constant  $V_S$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

(3)  $t > t_1$

## RL circuit: example

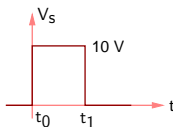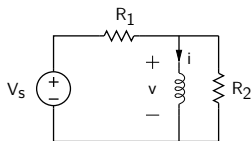

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$ , Find  $i(t)$ .


There are three intervals of constant  $V_S$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

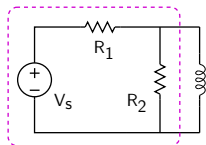(3)  $t > t_1$



$R_{Th}$  seen by  $L$  is the same in all intervals:



$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned}\tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s}\end{aligned}$$

## RL circuit: example

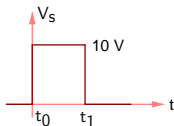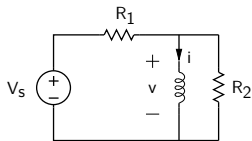

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$ , Find  $i(t)$ .


There are three intervals of constant  $V_s$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

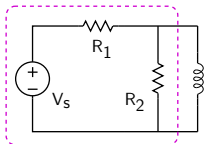(3)  $t > t_1$

$R_{Th}$  seen by  $L$  is the same in all intervals:





$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned}\tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s}\end{aligned}$$

At  $t = t_0^-$ ,  $v = 0 \text{ V}$ ,  $V_s = 0 \text{ V}$ .

$\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}$ .

## RL circuit: example

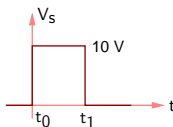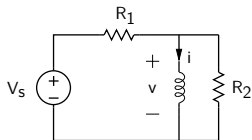

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$ , Find  $i(t)$ .


There are three intervals of constant  $V_s$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

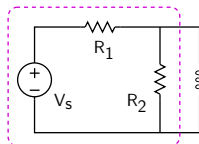(3)  $t > t_1$

$R_{Th}$  seen by  $L$  is the same in all intervals:




$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

At  $t = t_0^-$ ,  $v = 0 \text{ V}$ ,  $V_s = 0 \text{ V}$ .



$$\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}.$$

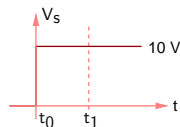If  $V_s$  did not change at  $t = t_1$ , we would have



$$v(\infty) = 0 \text{ V}, i(\infty) = 10 \text{ V}/10 \Omega = 1 \text{ A}.$$

## RL circuit: example

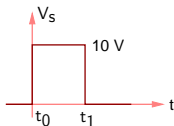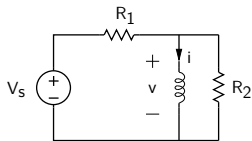

$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

$i(0) = 0 \text{ A}$ , Find  $i(t)$ .


There are three intervals of constant  $V_S$ :

(1)  $t < t_0$

(2)  $t_0 < t < t_1$

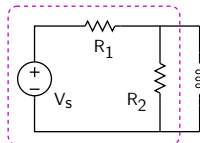(3)  $t > t_1$

$R_{Th}$  seen by  $L$  is the same in all intervals:




$$R_{Th} = R_1 \parallel R_2 = 8 \Omega$$

$$\begin{aligned} \tau &= L/R_{Th} \\ &= 0.8 \text{ H}/8 \Omega \\ &= 0.1 \text{ s} \end{aligned}$$

At  $t = t_0^-$ ,  $v = 0 \text{ V}$ ,  $V_S = 0 \text{ V}$ .

$$\Rightarrow i(t_0^-) = 0 \text{ A} \Rightarrow i(t_0^+) = 0 \text{ A}.$$


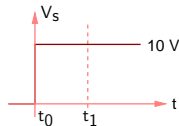
If  $V_S$  did not change at  $t = t_1$ , we would have



$$v(\infty) = 0 \text{ V}, i(\infty) = 10 \text{ V}/10 \Omega = 1 \text{ A}.$$

Using  $i(t_0^+)$  and  $i(\infty)$ , we can obtain  $i(t)$ ,  $t > 0$  (See next slide).

## RL circuit: example

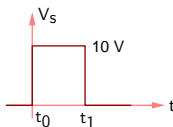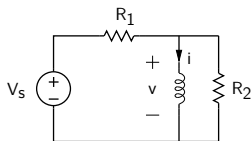


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$



$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

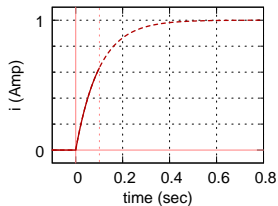



## RL circuit: example

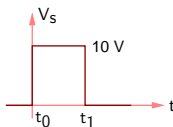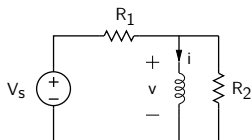


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$



$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

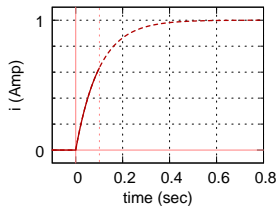

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

## RL circuit: example

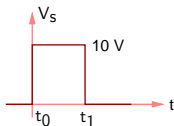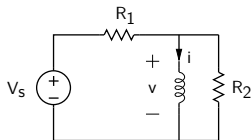


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$


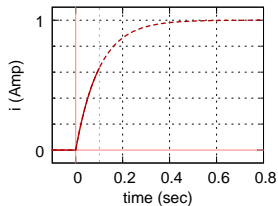


For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.

Consider  $t > t_1$ .

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

## RL circuit: example

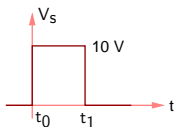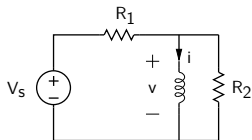


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

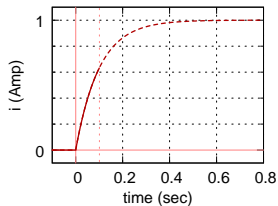

For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.



Consider  $t > t_1$ .

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

## RL circuit: example

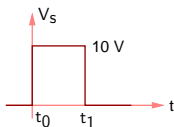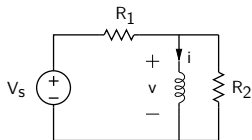


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

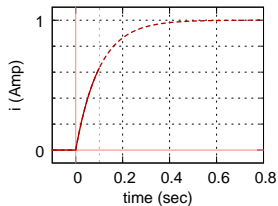

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.



Consider  $t > t_1$ .

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$

## RL circuit: example

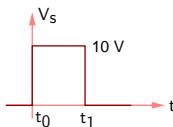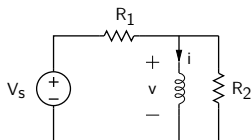


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

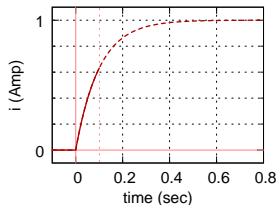

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.

Consider  $t > t_1$ .

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$



$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$

It is convenient to rewrite  $i(t)$  as

$$i(t) = A' \exp[-(t - t_1)/\tau] + B.$$

## RL circuit: example

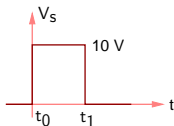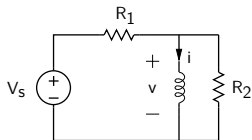


$$R_1 = 10 \Omega$$

$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$

$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$

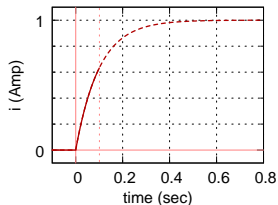

In reality,  $V_s$  changes at  $t = t_1$ ,  
and we need to work out the  
solution for  $t > t_1$  separately.

For  $t_0 < t < t_1$ ,  $i(t) = 1 - \exp(-t/\tau)$  Amp.

Consider  $t > t_1$ .

$$i(t_1^+) = i(t_1^-) = 1 - e^{-1} = 0.632 \text{ A (Note: } t_1/\tau = 1).$$

$$i(\infty) = 0 \text{ A.}$$

$$\text{Let } i(t) = A \exp(-t/\tau) + B.$$



It is convenient to rewrite  $i(t)$  as

$$i(t) = A' \exp[-(t - t_1)/\tau] + B.$$

Using  $i(t_1^+)$  and  $i(\infty)$ , we get

$$i(t) = 0.693 \exp[-(t - t_1)/\tau] \text{ A.}$$

## RL circuit: example

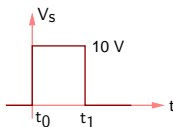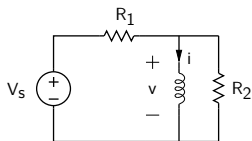

$$R_1 = 10 \Omega$$


$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$



$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$
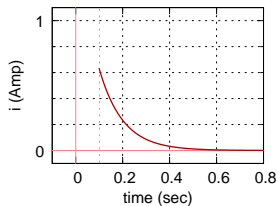
$$i(t) = 0.693 \exp[-(t - t_1)/\tau] \text{ A.}$$



## RL circuit: example

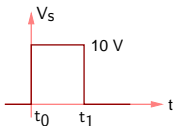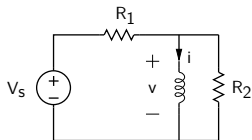

$$R_1 = 10 \Omega$$


$$R_2 = 40 \Omega$$

$$L = 0.8 \text{ H}$$


$$t_0 = 0$$

$$t_1 = 0.1 \text{ s}$$
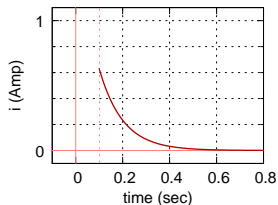
$$i(t) = 0.693 \exp[-(t - t_1)/\tau] \text{ A.}$$



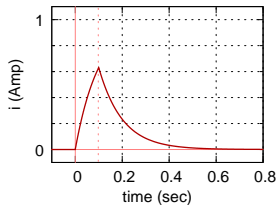
Combining the solutions for  $t_0 < t < t_1$  and  $t > t_1$ , we get




(SEQUEL file: ee101\_rl1.sqproj)




## RC circuit: example

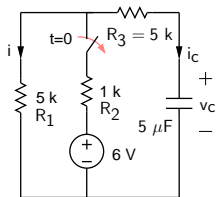

## RC circuit: example

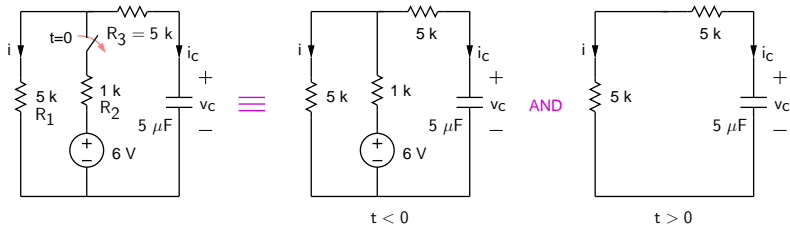


## RC circuit: example

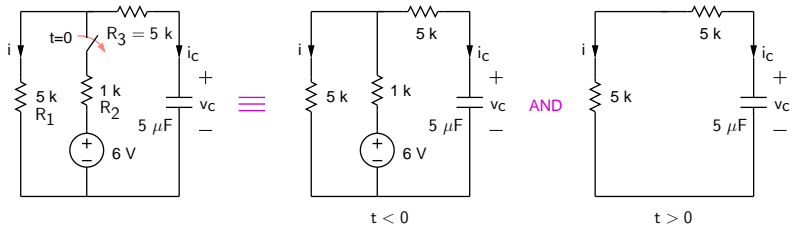

$t = 0^-$ : capacitor is an open circuit,  $\Rightarrow i(0^-) = 6\text{ V} / (5\text{ k} + 1\text{ k}) = 1\text{ mA}$ .


## RC circuit: example

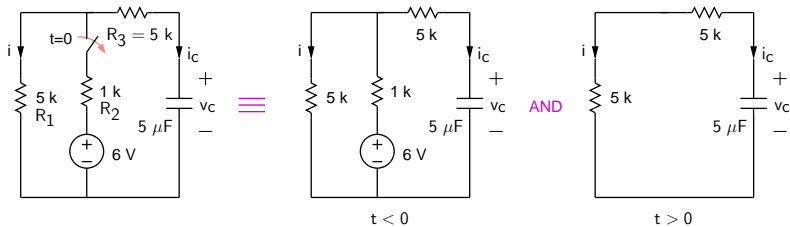

$t = 0^-$ : capacitor is an open circuit,  $\Rightarrow i(0^-) = 6\text{ V} / (5\text{ k} + 1\text{ k}) = 1\text{ mA}$ .

$v_c(0^-) = 6\text{ V} - 1\text{ mA} \times R_2 = 5\text{ V} \Rightarrow v_c(0^+) = 5\text{ V}$ .

## RC circuit: example

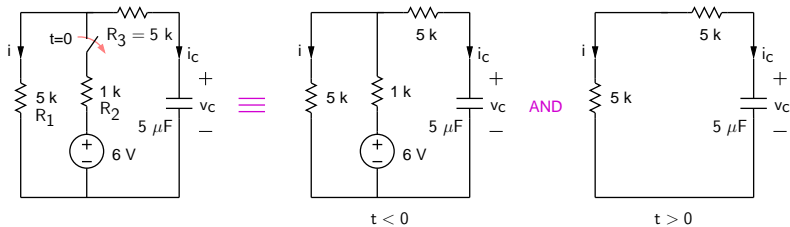


$t = 0^-$ : capacitor is an open circuit,  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .

$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$ .

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .

## RC circuit: example

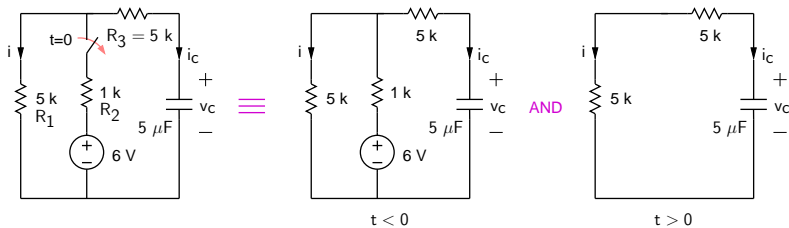


$t = 0^-$ : capacitor is an open circuit,  $\Rightarrow i(0^-) = 6\text{ V} / (5\text{ k} + 1\text{ k}) = 1\text{ mA}$ .

$v_c(0^-) = 6\text{ V} - 1\text{ mA} \times R_2 = 5\text{ V} \Rightarrow v_c(0^+) = 5\text{ V}$ .

$\Rightarrow i(0^+) = 5\text{ V} / (5\text{ k} + 5\text{ k}) = 0.5\text{ mA}$ .

Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10\text{ k} \times 5\text{ }\mu\text{F} = 50\text{ ms}$ .

## RC circuit: example

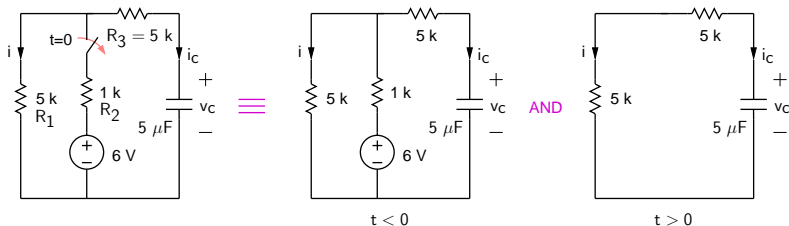

$t = 0^-$ : capacitor is an open circuit,  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .

$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$ .


$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .

Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$ .

Using  $i(0^+)$  and  $i(\infty) = 0 \text{ A}$ , we get

$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$ .

## RC circuit: example

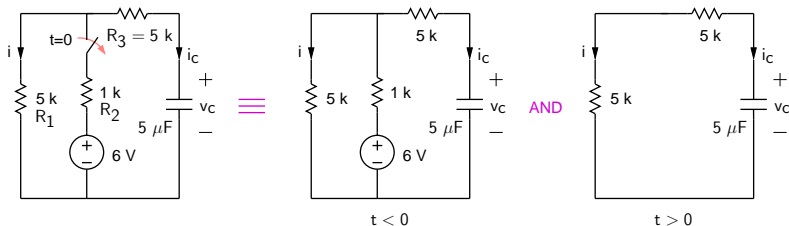

$t = 0^-$ : capacitor is an open circuit,  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .


$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$ .

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .

Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$ .


Using  $i(0^+)$  and  $i(\infty) = 0 \text{ A}$ , we get

$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$ .

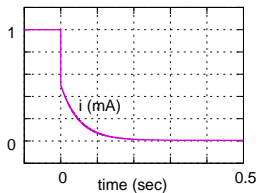



## RC circuit: example

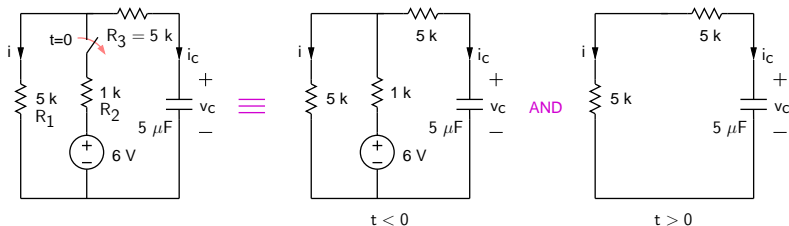

$t = 0^-$ : capacitor is an open circuit,  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .




$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$ .

$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .


Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$ .

Using  $i(0^+)$  and  $i(\infty) = 0 \text{ A}$ , we get

$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$ .

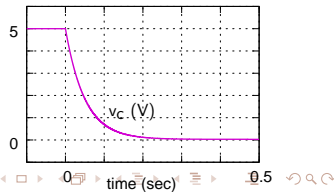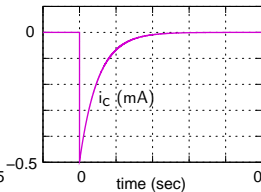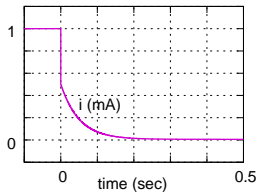

## RC circuit: example

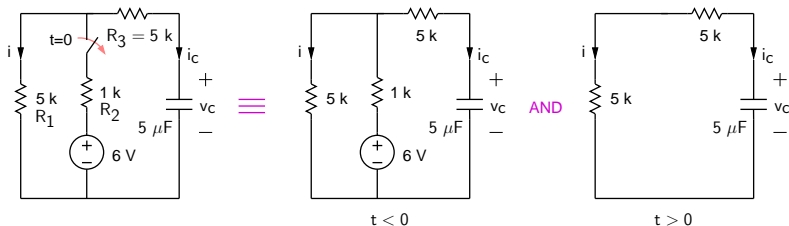

$t = 0^-$ : capacitor is an open circuit,  $\Rightarrow i(0^-) = 6 \text{ V} / (5 \text{ k} + 1 \text{ k}) = 1 \text{ mA}$ .

$v_c(0^-) = 6 \text{ V} - 1 \text{ mA} \times R_2 = 5 \text{ V} \Rightarrow v_c(0^+) = 5 \text{ V}$ .




$\Rightarrow i(0^+) = 5 \text{ V} / (5 \text{ k} + 5 \text{ k}) = 0.5 \text{ mA}$ .

Let  $i(t) = A \exp(-t/\tau) + B$  for  $t > 0$ , with  $\tau = 10 \text{ k} \times 5 \mu\text{F} = 50 \text{ ms}$ .


Using  $i(0^+)$  and  $i(\infty) = 0 \text{ A}$ , we get


$i(t) = 0.5 \exp(-t/\tau) \text{ mA}$ .

(SEQUEL file: ee101\_rc2.sqproj)

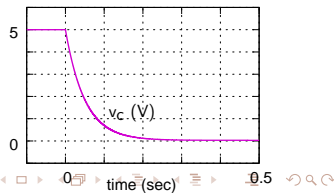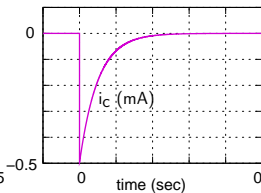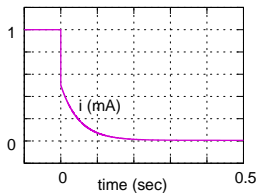


## RC circuits: home work

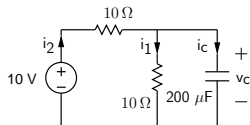


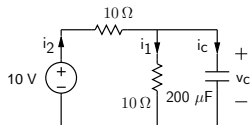

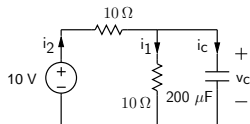- \* Given  $v_c(0) = 0\text{ V}$ , find  $v_c(t)$  for  $t > 0$ . Using this  $v_c(t)$ , find  $i_1$ ,  $i_2$ ,  $i_c$  for  $t > 0$ . Plot  $v_c$ ,  $i_1$ ,  $i_2$ ,  $i_c$  versus  $t$ .





- \* Given  $v_c(0) = 0\text{ V}$ , find  $v_c(t)$  for  $t > 0$ . Using this  $v_c(t)$ , find  $i_1$ ,  $i_2$ ,  $i_c$  for  $t > 0$ . Plot  $v_c$ ,  $i_1$ ,  $i_2$ ,  $i_c$  versus  $t$ .
- \* Find  $i_1$ ,  $i_2$ ,  $i_c$  directly (i.e., without getting  $v_c$ ) by finding the initial and final conditions for each of them ( $i_1(0^+)$  and  $i_1(\infty)$ , etc.) and then using them to compute the coefficients in the general expression,  $x(t) = A \exp(-t/\tau) + B$ .

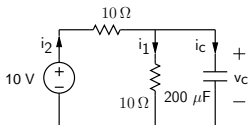

- \* Given  $v_c(0) = 0\text{ V}$ , find  $v_c(t)$  for  $t > 0$ . Using this  $v_c(t)$ , find  $i_1$ ,  $i_2$ ,  $i_c$  for  $t > 0$ . Plot  $v_c$ ,  $i_1$ ,  $i_2$ ,  $i_c$  versus  $t$ .
- \* Find  $i_1$ ,  $i_2$ ,  $i_c$  directly (i.e., without getting  $v_c$ ) by finding the initial and final conditions for each of them ( $i_1(0^+)$  and  $i_1(\infty)$ , etc.) and then using them to compute the coefficients in the general expression,  $x(t) = A \exp(-t/\tau) + B$ .
- \* Verify your results with SEQUEL (file: ee101\_rc3.sqproj).


## RC circuits: home work

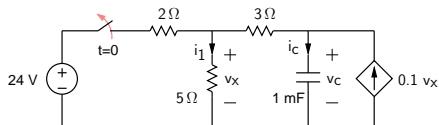

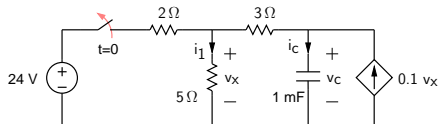


\* Find  $v_c(0^-)$ ,  $v_c(\infty)$ .




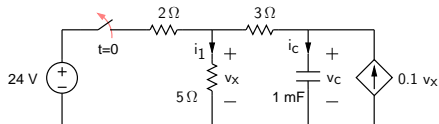

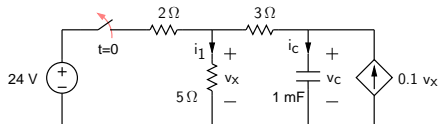
- \* Find  $v_c(0^-)$ ,  $v_c(\infty)$ .
- \* Find  $R_{Th}$  as seen by the capacitor for  $t > 0$ .




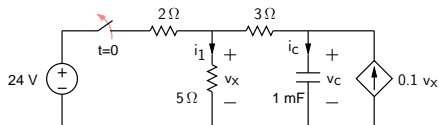- \* Find  $v_c(0^-)$ ,  $v_c(\infty)$ .
- \* Find  $R_{Th}$  as seen by the capacitor for  $t > 0$ .
- \* Solve for  $v_c(t)$  and  $i_1(t)$ ,  $t > 0$ .




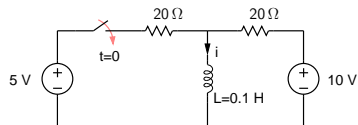- \* Find  $v_c(0^-)$ ,  $v_c(\infty)$ .
- \* Find  $R_{Th}$  as seen by the capacitor for  $t > 0$ .
- \* Solve for  $v_c(t)$  and  $i_1(t)$ ,  $t > 0$ .
- \* Verify your results with SEQUEL (file: ee101\_rc4.sqproj).




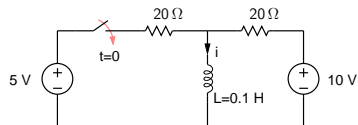


\* Find  $i(0^-)$ ,  $i(\infty)$ .

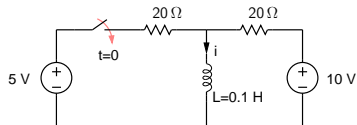

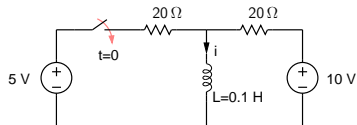- \* Find  $i(0^-)$ ,  $i(\infty)$ .
- \* Find  $R_{Th}$  as seen by the inductor for  $t > 0$ .



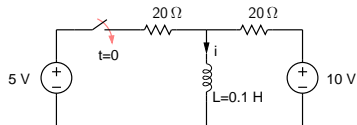- \* Find  $i(0^-)$ ,  $i(\infty)$ .
- \* Find  $R_{Th}$  as seen by the inductor for  $t > 0$ .
- \* Solve for  $i(t)$ ,  $t > 0$ .



- \* Find  $i(0^-)$ ,  $i(\infty)$ .
- \* Find  $R_{Th}$  as seen by the inductor for  $t > 0$ .
- \* Solve for  $i(t)$ ,  $t > 0$ .
- \* Verify your results with SEQUEL (file: ee101\_r12.sqproj).