

`bjt_inverter.sqproj`

Description

The BJT circuit shown in Fig. 1 acts as an inverter: When the input voltage is low, the transistor does not conduct, there is no current through R_C , and the collector voltage (output) is pulled up to V_{CC} . When the input voltage is increased, the transistor begins to conduct, the voltage drop across R_C starts increasing, and the output voltage falls. Finally, when the input voltage is high enough to drive the transistor into saturation, there is a fixed small drop ($V_{CE}=0.1$ to 0.2 V) across the transistor, and the output voltage saturates to this low value. The transfer characteristic is shown in Fig. 2.

Assignments

1. Write V_C as a function of V_{BB} for the transition region in Fig. 2. Assume that V_{BE} is approximately 0.7 V in this region.
2. If R_B is doubled, how will the plot change?
3. If R_C is doubled, how will the plot change?

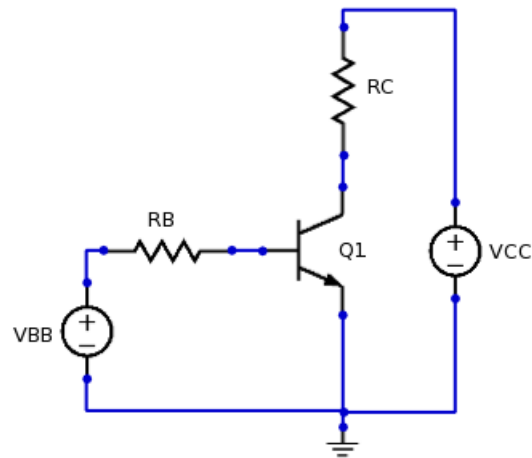


Figure 1: Circuit schematic for BJT inverter.

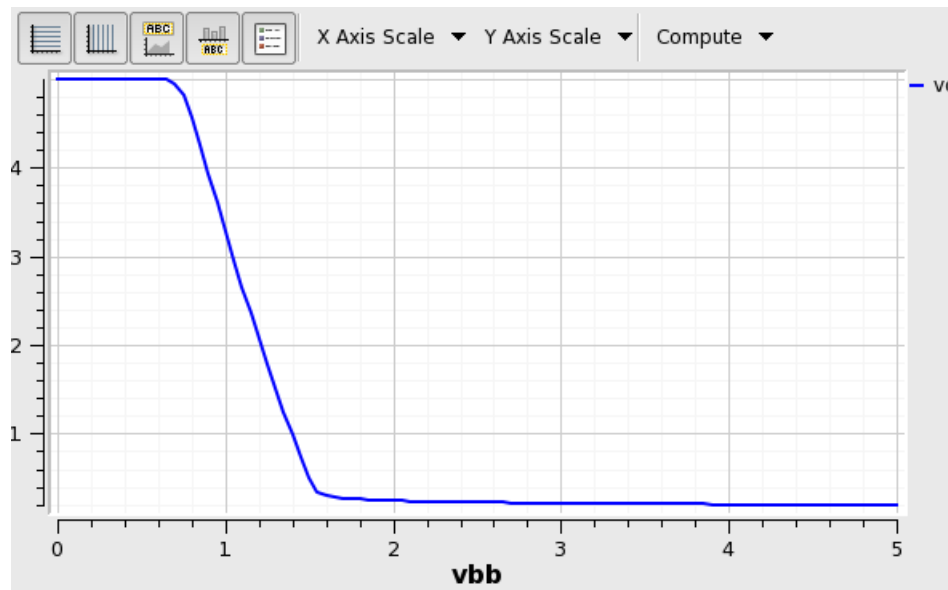


Figure 2: Output voltage versus input voltage for the BJT inverter in Fig. 1.