

## ee101\_zener\_regulator.sqproj

### Description

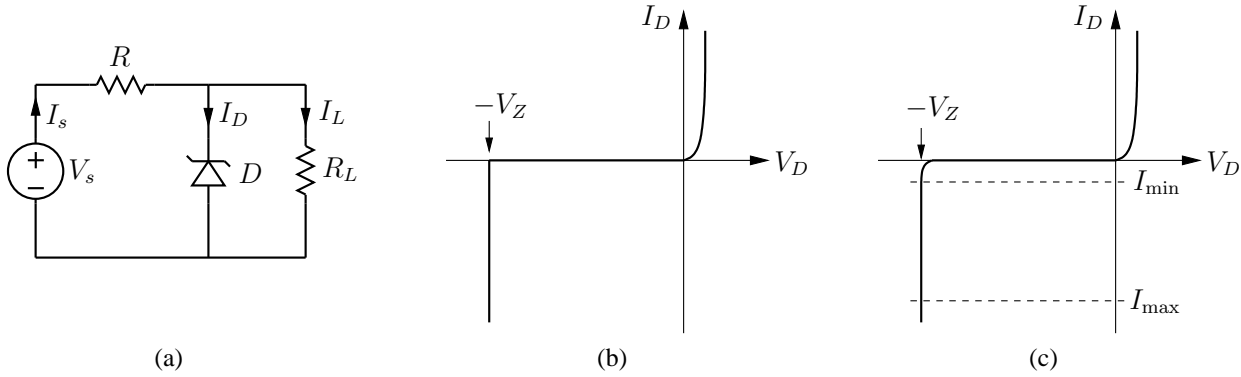


Figure 1: (a) Zener diode voltage regulator, (b) ideal Zener diode  $I - V$  curve, (c) practical Zener diode  $I - V$  curve.

A Zener diode can be used to provide a constant output voltage which is independent of the supply voltage  $V_s$  and load resistance  $R_L$  (see Fig. 1 (a)). If the Zener behaved ideally, as shown in Fig. 1 (b), there would be no restrictions on the values of  $V_s$  and  $R_L$ , as long as  $V_s > V_Z$ . However, for a practical Zener diode, the breakdown is not sharp, and it is desirable to ensure a minimum current ( $I_{\min}$  in Fig. 1 (c)) through the Zener diode so that the diode voltage is indeed  $V_Z$ . Further, the maximum diode current ( $I_{\max}$  in Fig. 1 (c)) is also limited because of power dissipation and heating considerations. As a result, a practical voltage regulator circuit is designed with the constraint,

$$I_{\min} < I_D < I_{\max} . \quad (1)$$

Typically,  $I_{\min}$  is taken as 10% of  $I_{\max}$ .

### Exercise Set

1. For  $V_s = 24\text{ V}$ ,  $R = 300\ \Omega$ ,  $V_Z = 6\text{ V}$ ,  $I_{\max} = 50\text{ mA}$ , what is the range of  $R_L$  for which the diode current stays within the above limits?
2. For  $R_L = 1\text{ k}\Omega$ ,  $R = 300\ \Omega$ ,  $V_Z = 6\text{ V}$ ,  $I_{\max} = 50\text{ mA}$ , what is the range of  $V_s$  for which the diode current stays within the above limits?

In each case, plot  $I_s$ ,  $I_D$ , and  $I_L$  versus  $R_L$  by simulation, and compare with your answers.