

diode_iv.sqproj


Description

The SPICE diode model is based on the Shockley diode equation [1]. The saturation current I_s is a key parameter in deciding the diode current.

Exercise

Simulate the circuit shown in the figure, and plot I_D versus V_D , i.e., the diode $I-V$ characteristic.

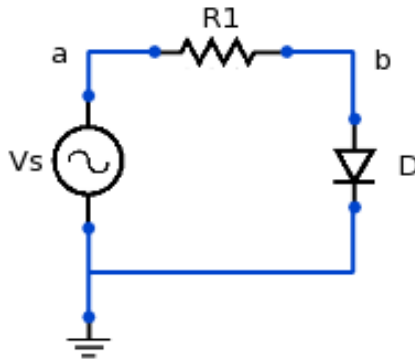- (a) Change I_s by a factor of 2, 5, 10, and see its effect on the $I-V$ characteristic.
- (b) Simulate the circuit at $T = 300\text{ K}$, 320 K , 350 K . How does the $I-V$ curve change?
Explain the results on the basis of the Shockley equation.



References:

1. P. Antognetti and G. Massabrio, *Semiconductor device modeling with SPICE*, McGraw-Hill: New York, 1988.