

## bjt\_mirror\_1.sqproj

### Description

Shown in Fig. 1 is a simple current mirror. Since the base-emitter voltage ( $V_{BE}$ ) for the two BJTs is the same in this circuit, the reference current  $I_{C1}$  of  $Q_1$  is “mirrored” on the transistor  $Q_2$ , i.e.,  $I_{C2}$  is made equal to  $I_{C1}$ . This allows us to change  $I_{C2}$  *irrespective* of the voltage  $V_{C2}$  by simply changing the resistance  $R_1$ , since

$$I_{C1} \approx \frac{V_{CC} - 0.7 \text{ V}}{R_1} . \quad (1)$$

In practice, the current  $I_{C2}$  is not quite independent of  $V_{C2}$  because the transistor  $Q_2$  has a finite output resistance due to the Early effect. Thus,  $I_{C2}$  is found to increase slightly with  $V_{C2}$  (see Fig. 2), and the slope  $\partial I_{C2}/\partial V_{C2}$  is an important figure of merit (smaller the better) for any current mirror.

The other non-ideality is due to the requirement that the transistors must remain in the active region; therefore the circuit will not work as desired when  $V_{C2}$  is not sufficiently large.

### Assignments

1. Plot  $I_{C1}$  and  $I_{C2}$  as a function of  $V_{C2}$  ( $V_{C2}$  can be varied by varying the resistance  $R_2$ ) and comment on the plot.
2. Change  $R_1$  to  $R_1/2$ , and repeat (1).
3. Double the value of the Early voltage ( $V_A$ ) of  $Q_2$  and observe the effect on the slope of the  $I_{C2}$  versus  $V_{C2}$  curve.

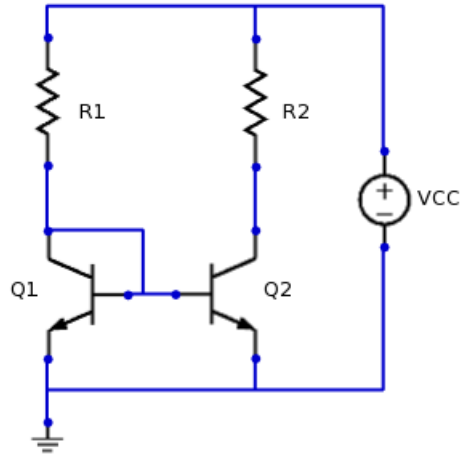


Figure 1: Circuit schematic for simple current mirror.

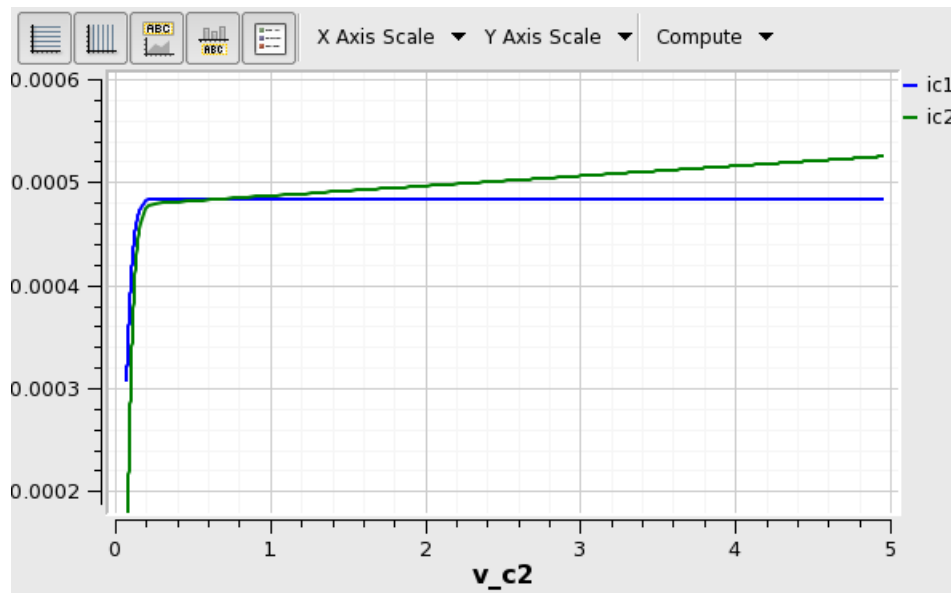


Figure 2:  $I_{C1}$  and  $I_{C2}$  versus  $V_{C2}$  for the current mirror of Fig. 1.