

# EE101: Op Amp circuits (Part 1)

---



**M. B. Patil**

[mbpatil@ee.iitb.ac.in](mailto:mbpatil@ee.iitb.ac.in)

Department of Electrical Engineering  
Indian Institute of Technology Bombay

- \* The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.

- \* The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- \* The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.

- \* The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- \* The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.
- \* The characteristics of an Op Amp are nearly ideal  $\rightarrow$  Op Amp circuits can be expected to perform as per theoretical design in most cases.

- \* The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- \* The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.
- \* The characteristics of an Op Amp are nearly ideal  $\rightarrow$  Op Amp circuits can be expected to perform as per theoretical design in most cases.
- \* Amplifiers built with Op Amps work with DC input voltages as well  $\rightarrow$  useful in sensor applications (e.g., temperature, pressure)

# Op Amps: introduction


- \* The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- \* The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.
- \* The characteristics of an Op Amp are nearly ideal → Op Amp circuits can be expected to perform as per theoretical design in most cases.
- \* Amplifiers built with Op Amps work with DC input voltages as well → useful in sensor applications (e.g., temperature, pressure)
- \* The user can generally carry out circuit design without a thorough knowledge of the intricate details (next slide) of an Op Amp. This makes the design process simple.

# Op Amps: introduction


- \* The Operational Amplifier (Op Amp) is a versatile building block that can be used for realizing several electronic circuits.
- \* The use of Op Amps frees the user from cumbersome details such as transistor biasing and coupling capacitors.
- \* The characteristics of an Op Amp are nearly ideal → Op Amp circuits can be expected to perform as per theoretical design in most cases.
- \* Amplifiers built with Op Amps work with DC input voltages as well → useful in sensor applications (e.g., temperature, pressure)
- \* The user can generally carry out circuit design without a thorough knowledge of the intricate details (next slide) of an Op Amp. This makes the design process simple.
- \* However, as Einstein has said, we should “make everything as simple as possible, but not simpler.” → need to know where the ideal world ends, and the real one begins.

# Op Amp 741

Actual circuit

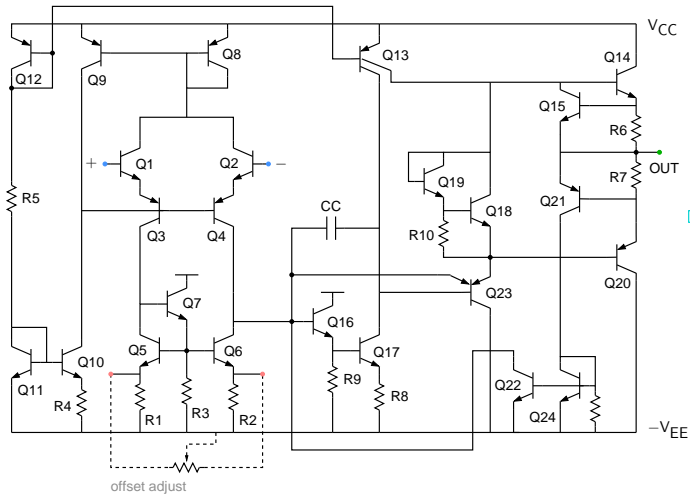


Symbol

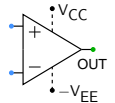




# Op Amp: equivalent circuit

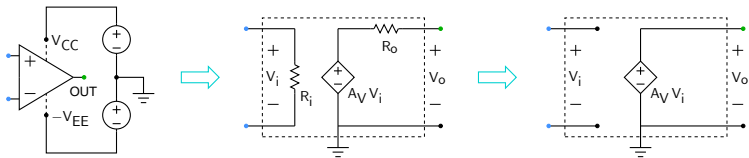


## Op Amp: equivalent circuit

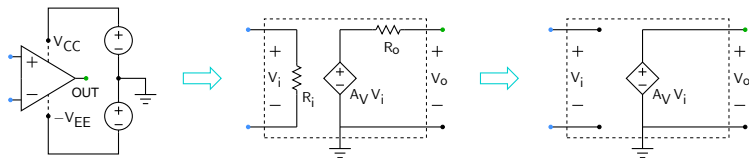


- \* The external resistances ( $\sim$  a few  $k\Omega$ ) are generally much larger than  $R_o$  and much smaller than  $R_i \rightarrow$  we can assume  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$  without significantly affecting the analysis.

## Op Amp: equivalent circuit

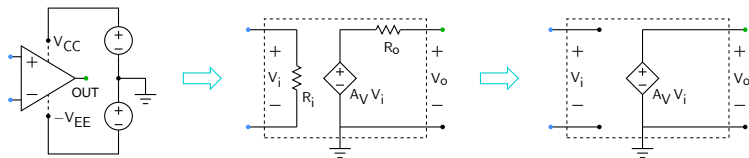

- \* The external resistances ( $\sim$  a few  $k\Omega$ ) are generally much larger than  $R_o$  and much smaller than  $R_i \rightarrow$  we can assume  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$  without significantly affecting the analysis.
- \*  $V_{CC}$  and  $-V_{EE}$  ( $\sim \pm 5\text{ V}$  to  $\pm 15\text{ V}$ ) must be supplied; an Op Amp will not work without them!


## Op Amp: equivalent circuit

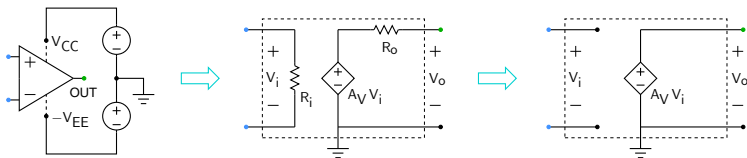

- \* The external resistances ( $\sim$  a few  $k\Omega$ ) are generally much larger than  $R_o$  and much smaller than  $R_i \rightarrow$  we can assume  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$  without significantly affecting the analysis.
- \*  $V_{CC}$  and  $-V_{EE}$  ( $\sim \pm 5\text{ V}$  to  $\pm 15\text{ V}$ ) must be supplied; an Op Amp will not work without them!

In Op Amp circuits, the supply voltages are often not shown explicitly.

## Op Amp: equivalent circuit

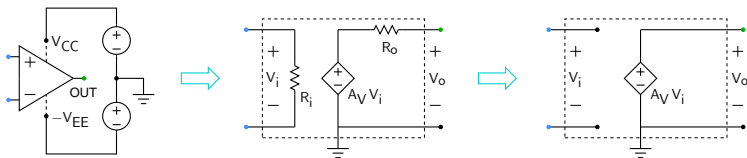




- \* The external resistances ( $\sim$  a few  $k\Omega$ ) are generally much larger than  $R_o$  and much smaller than  $R_i \rightarrow$  we can assume  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$  without significantly affecting the analysis.
- \*  $V_{CC}$  and  $-V_{EE}$  ( $\sim \pm 5\text{ V}$  to  $\pm 15\text{ V}$ ) must be supplied; an Op Amp will not work without them!

In Op Amp circuits, the supply voltages are often not shown explicitly.




\*

Parameter	Ideal Op Amp	741
$A_V$	$\infty$	$10^5$ (100 dB)
$R_i$	$\infty$	2 M $\Omega$
$R_o$	0	75 $\Omega$

# Op Amp: equivalent circuit

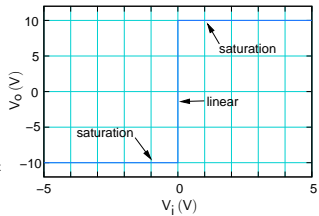
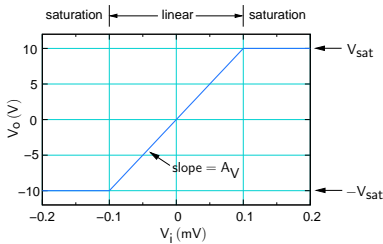
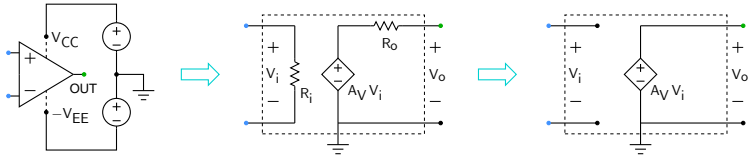


# Op Amp: equivalent circuit

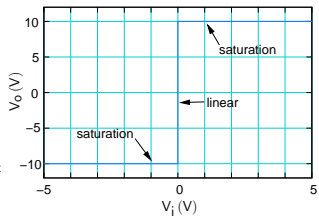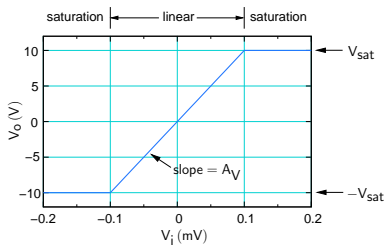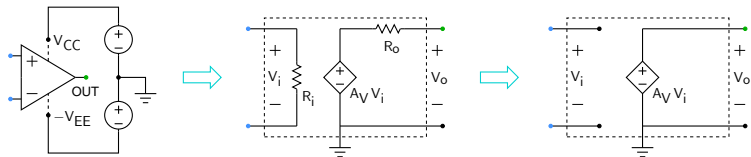

- \* The output voltage  $V_o$  is limited to  $\pm V_{sat}$ , where  $V_{sat} \sim 1.5 \text{ V}$  less than  $V_{CC}$ .




# Op Amp: equivalent circuit

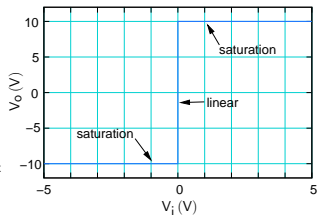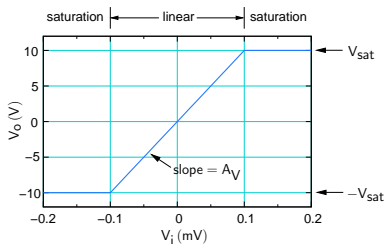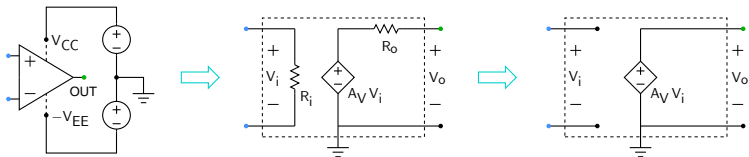


- \* The output voltage  $V_o$  is limited to  $\pm V_{sat}$ , where  $V_{sat} \sim 1.5 \text{ V}$  less than  $V_{CC}$ .
- \* For  $-V_{sat} < V_o < V_{sat}$ ,  $V_i = V_+ - V_- = V_o/A_V$ , which is very small  $\rightarrow V_+$  and  $V_-$  are *virtually* the same.



# Op Amp circuits

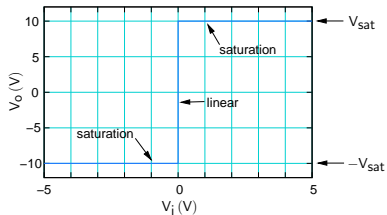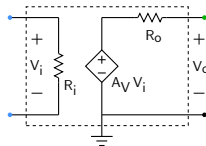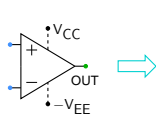


# Op Amp circuits

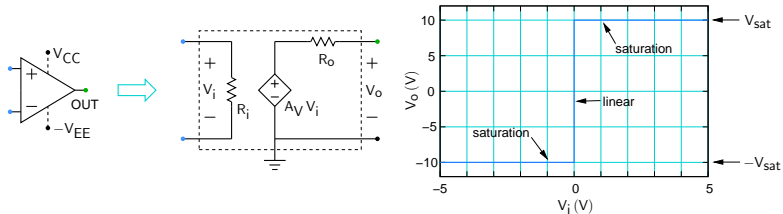


\* Broadly, Op Amp circuits can be divided into two categories:

# Op Amp circuits

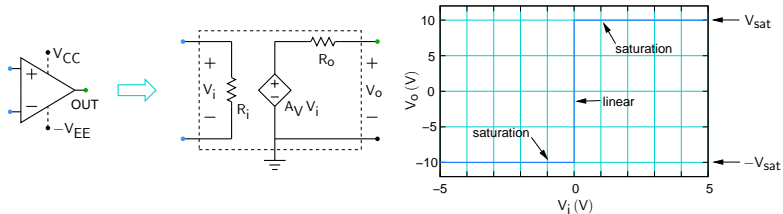

- \* Broadly, Op Amp circuits can be divided into two categories:
  - Op Amp operating in the linear region


# Op Amp circuits

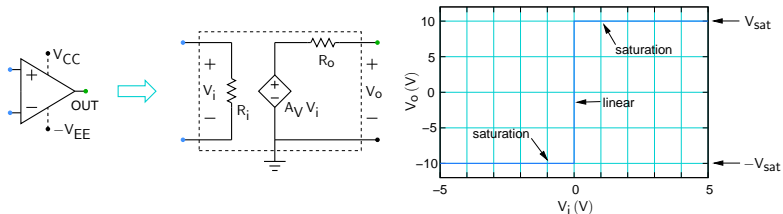

\* Broadly, Op Amp circuits can be divided into two categories:


- Op Amp operating in the linear region
- Op Amp operating in the saturation region

# Op Amp circuits

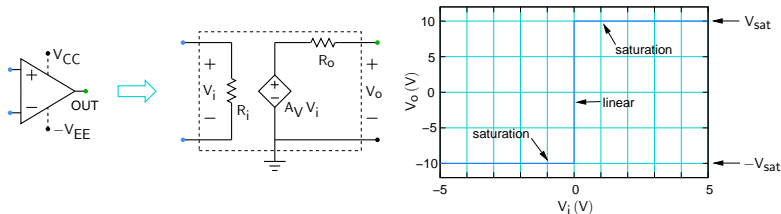


- \* Broadly, Op Amp circuits can be divided into two categories:
  - Op Amp operating in the linear region
  - Op Amp operating in the saturation region
- \* Whether an Op Amp in a given circuit will operate in linear or saturation region depends on

# Op Amp circuits

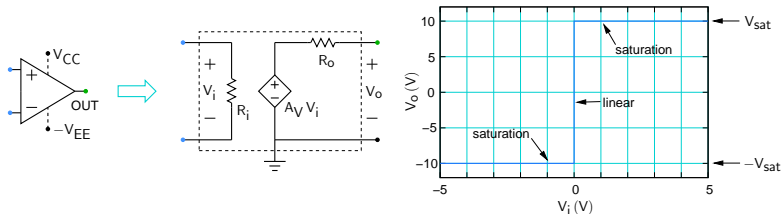



- \* Broadly, Op Amp circuits can be divided into two categories:
  - Op Amp operating in the linear region
  - Op Amp operating in the saturation region
- \* Whether an Op Amp in a given circuit will operate in linear or saturation region depends on
  - input voltage magnitude

# Op Amp circuits

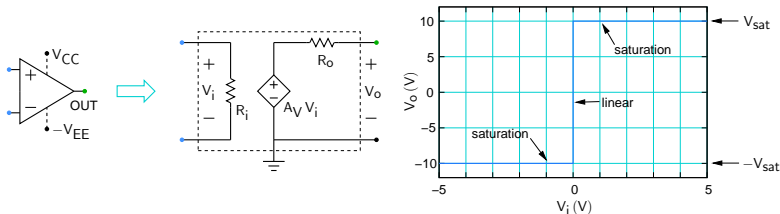



- \* Broadly, Op Amp circuits can be divided into two categories:
  - Op Amp operating in the linear region
  - Op Amp operating in the saturation region
- \* Whether an Op Amp in a given circuit will operate in linear or saturation region depends on
  - input voltage magnitude
  - type of feedback (negative or positive)  
(We will take a qualitative look at feedback later.)

# Op Amp circuits (linear region)

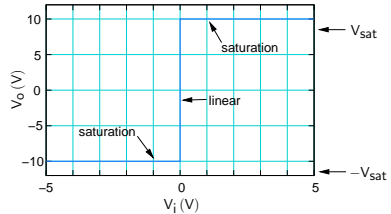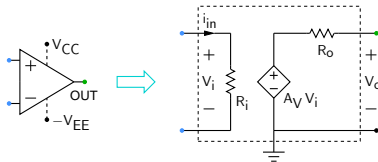



# Op Amp circuits (linear region)

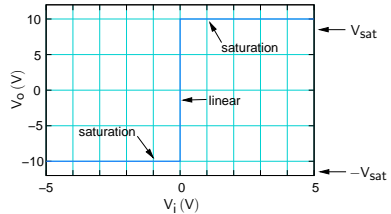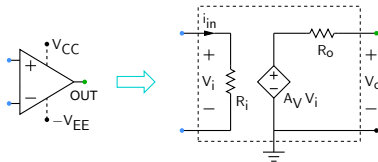


In the linear region,

\*  $V_+ - V_- = V_o/A_V$ , which is very small

→  $V_+ \approx V_-$

# Op Amp circuits (linear region)

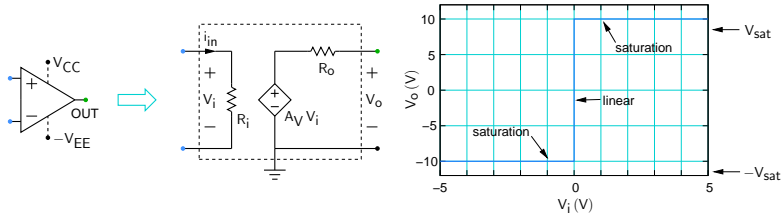

In the linear region,


- \*  $V_+ - V_- = V_o / A_V$ , which is very small

$$\rightarrow V_+ \approx V_-$$

- \* Since  $R_i$  is typically much larger than other resistances in the circuit, we can assume  $R_i \rightarrow \infty$ .

$$\rightarrow i_{in} \approx 0$$

# Op Amp circuits (linear region)

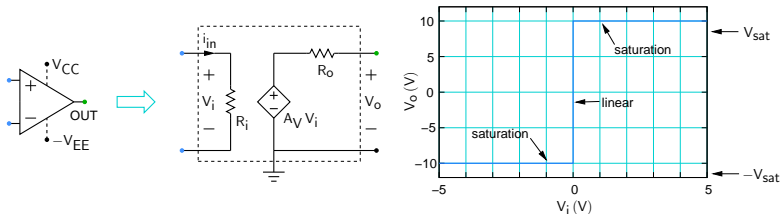

In the linear region,

- \*  $V_+ - V_- = V_o/A_V$ , which is very small


$$\rightarrow V_+ \approx V_-$$

- \* Since  $R_i$  is typically much larger than other resistances in the circuit, we can assume  $R_i \rightarrow \infty$ .


$$\rightarrow i_{in} \approx 0$$

These two “golden rules” enable us to understand several Op Amp circuits.

## Op Amp circuits (linear region)

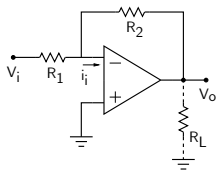


## Op Amp circuits (linear region)

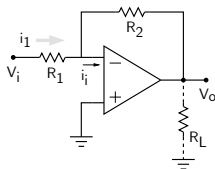

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

## Op Amp circuits (linear region)

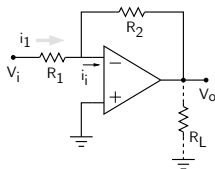


Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the Op Amp) is zero,  $i_1$  goes through  $R_2$ .

## Op Amp circuits (linear region)

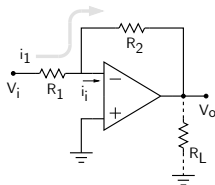


Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the Op Amp) is zero,  $i_1$  goes through  $R_2$ .

## Op Amp circuits (linear region)

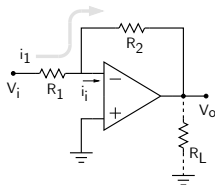

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$ .


(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the Op Amp) is zero,  $i_1$  goes through  $R_2$ .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left( \frac{V_i}{R_1} \right) R_2 = - \left( \frac{R_2}{R_1} \right) V_i.$$



## Op Amp circuits (linear region)

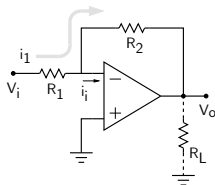

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$ .


(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)

Since  $i_i$  (current entering the Op Amp) is zero,  $i_1$  goes through  $R_2$ .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left( \frac{V_i}{R_1} \right) R_2 = - \left( \frac{R_2}{R_1} \right) V_i.$$

The circuit is called an “inverting amplifier.”

## Op Amp circuits (linear region)

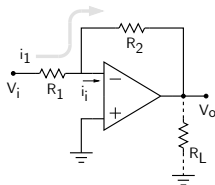

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)


Since  $i_i$  (current entering the Op Amp) is zero,  $i_1$  goes through  $R_2$ .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left( \frac{V_i}{R_1} \right) R_2 = - \left( \frac{R_2}{R_1} \right) V_i.$$

The circuit is called an “inverting amplifier.”

Where does the current go?

## Op Amp circuits (linear region)

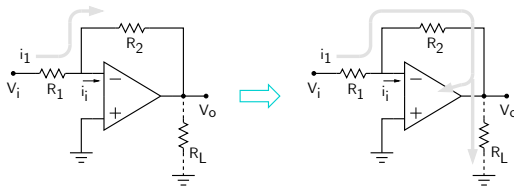

Since  $V_+ \approx V_-$ ,  $V_- \approx 0\text{ V} \rightarrow i_1 = (V_i - 0)/R = V_i/R$ .

(The non-inverting input is at *real* ground here, and the inverting input is at *virtual* ground.)



Since  $i_i$  (current entering the Op Amp) is zero,  $i_1$  goes through  $R_2$ .

$$\rightarrow V_o = V_- - i_1 R_2 = 0 - \left( \frac{V_i}{R_1} \right) R_2 = - \left( \frac{R_2}{R_1} \right) V_i.$$


The circuit is called an “inverting amplifier.”

Where does the current go?

# Op Amp circuits: inverting amplifier

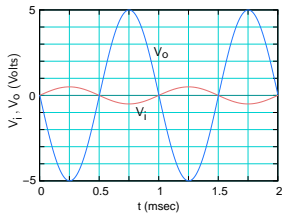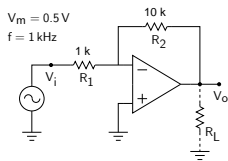


## Op Amp circuits: inverting amplifier

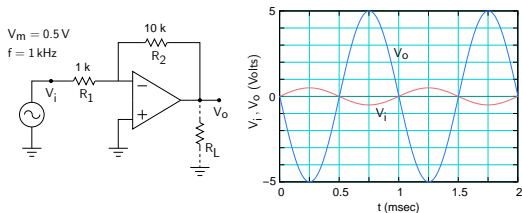


- \* The gain of the inverting amplifier is  $-R_2/R_1$ . It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the Op Amp which is  $\sim 10^5$ ).

## Op Amp circuits: inverting amplifier

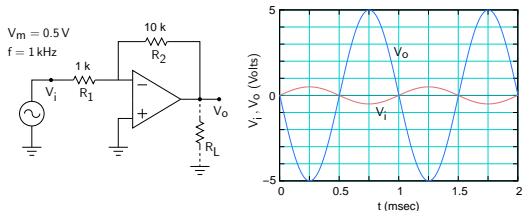


- \* The gain of the inverting amplifier is  $-R_2/R_1$ . It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the Op Amp which is  $\sim 10^5$ ).
- \* The gain can be adjusted simply by changing  $R_1$  or  $R_2$  !

## Op Amp circuits: inverting amplifier

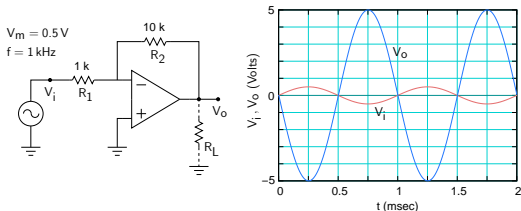

- \* The gain of the inverting amplifier is  $-R_2/R_1$ . It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the Op Amp which is  $\sim 10^5$ ).
- \* The gain can be adjusted simply by changing  $R_1$  or  $R_2$  !
- \* For the common-emitter amplifier, on the other hand, the gain  $-g_m (R_C \parallel R_L)$  depends on how the BJT is biased (since  $g_m$  depends on  $I_C$ ).

## Op Amp circuits: inverting amplifier


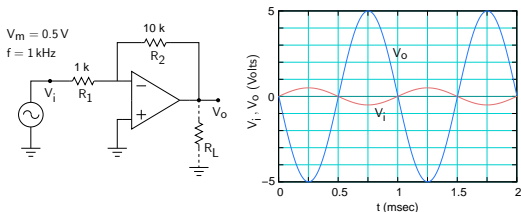


- \* The gain of the inverting amplifier is  $-R_2/R_1$ . It is called the “closed-loop gain” (to distinguish it from the “open-loop gain” of the Op Amp which is  $\sim 10^5$ ).
- \* The gain can be adjusted simply by changing  $R_1$  or  $R_2$  !
- \* For the common-emitter amplifier, on the other hand, the gain  $-g_m (R_C \parallel R_L)$  depends on how the BJT is biased (since  $g_m$  depends on  $I_C$ ).


(SEQUEL file: ee101\_inv\_amp\_1.sqproj)



# Op Amp circuits: inverting amplifier

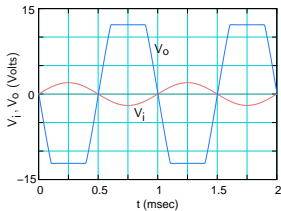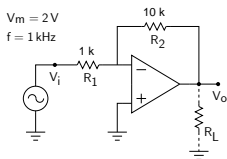


## Op Amp circuits: inverting amplifier

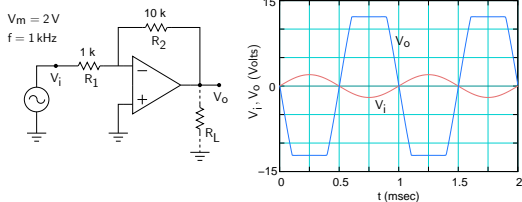



- \* The output voltage is limited to  $\pm V_{\text{sat}}$ .

## Op Amp circuits: inverting amplifier

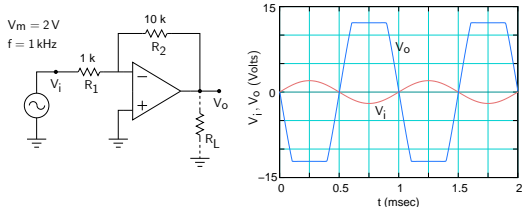


- \* The output voltage is limited to  $\pm V_{\text{sat}}$ .
- \*  $V_{\text{sat}}$  is  $\sim 1.5\text{ V}$  less than the supply voltage  $V_{\text{CC}}$ .

# Op Amp circuits: inverting amplifier

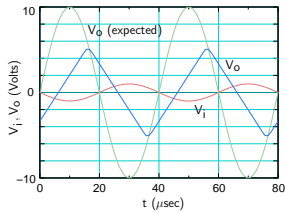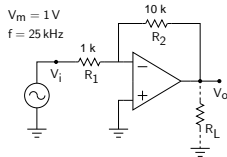


## Op Amp circuits: inverting amplifier

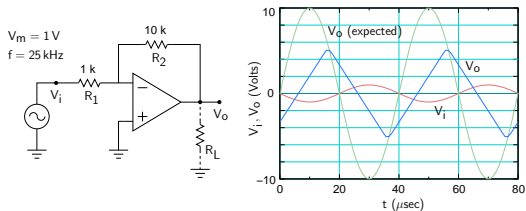


- \* If the signal frequency is too high, a practical Op Amp cannot keep up with the input due to its “slew rate” limitation.

## Op Amp circuits: inverting amplifier

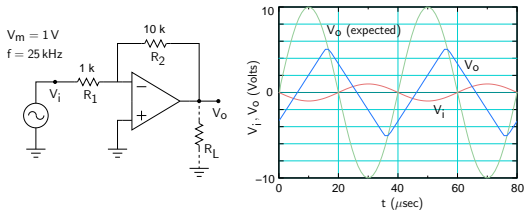


- \* If the signal frequency is too high, a practical Op Amp cannot keep up with the input due to its “slew rate” limitation.
- \* The slew rate of an Op Amp is the maximum rate at which the Op Amp output can rise (or fall).

## Op Amp circuits: inverting amplifier

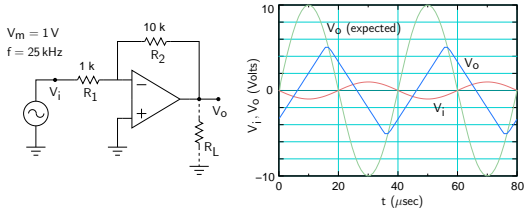

- \* If the signal frequency is too high, a practical Op Amp cannot keep up with the input due to its “slew rate” limitation.
- \* The slew rate of an Op Amp is the maximum rate at which the Op Amp output can rise (or fall).
- \* For the 741, the slew rate is  $0.5\text{ V}/\mu\text{sec}$ .

## Op Amp circuits: inverting amplifier

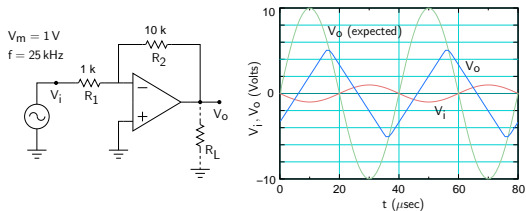


- \* If the signal frequency is too high, a practical Op Amp cannot keep up with the input due to its “slew rate” limitation.
- \* The slew rate of an Op Amp is the maximum rate at which the Op Amp output can rise (or fall).
- \* For the 741, the slew rate is  $0.5\text{ V}/\mu\text{sec}$ .

(SEQUEL file: ee101\_inv\_amp\_2.sqproj)




## Op Amp circuits: inverting amplifier

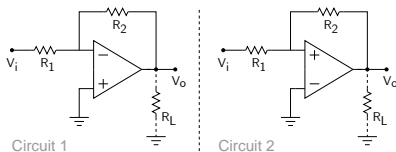

What if the + (non-inverting) and - (inverting) inputs of the Op Amp are interchanged?


## Op Amp circuits: inverting amplifier

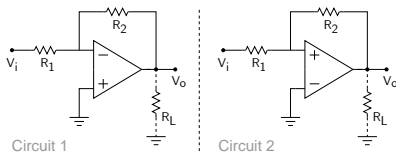

What if the + (non-inverting) and - (inverting) inputs of the Op Amp are interchanged?

Our previous analysis would once again give us  $V_o = -\frac{R_2}{R_1} V_i$ .

## Op Amp circuits: inverting amplifier

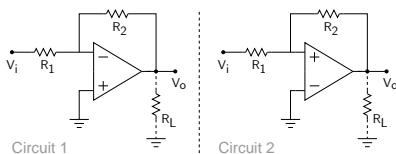


What if the + (non-inverting) and - (inverting) inputs of the Op Amp are interchanged?

Our previous analysis would once again give us  $V_o = -\frac{R_2}{R_1} V_i$ .

However, from Circuit 1 to Circuit 2, the nature of the feedback changes from negative to positive.

→ Our assumption that the Op Amp is working in the linear region does not hold for Circuit 2, and  $V_o = -\frac{R_2}{R_1} V_i$  does not apply any more.

## Op Amp circuits: inverting amplifier

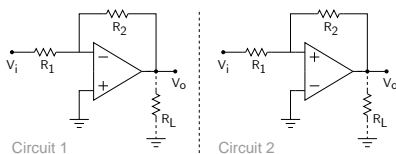

What if the + (non-inverting) and - (inverting) inputs of the Op Amp are interchanged?


Our previous analysis would once again give us  $V_o = -\frac{R_2}{R_1} V_i$ .

However, from Circuit 1 to Circuit 2, the nature of the feedback changes from negative to positive.

→ Our assumption that the Op Amp is working in the linear region does not hold for Circuit 2, and  $V_o = -\frac{R_2}{R_1} V_i$  does not apply any more.


(Circuit 2 is also useful, and we will discuss it later.)

## Op Amp circuits (linear region)

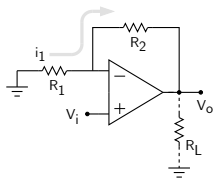

\*  $V_+ \approx V_- = V_i$


## Op Amp circuits (linear region)

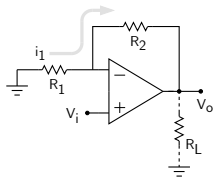

$$* \quad V_+ \approx V_- = V_i$$

$$\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1 .$$

## Op Amp circuits (linear region)

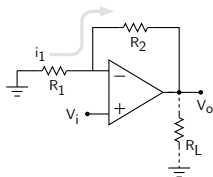


$$* V_+ \approx V_- = V_i$$

$$\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1.$$

$$* V_o = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right).$$


## Op Amp circuits (linear region)

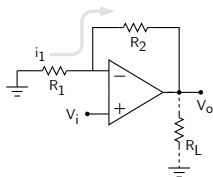

- \*  $V_+ \approx V_- = V_i$   
 $\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1$ .
- \*  $V_o = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right)$ .
- \* This circuit is known as the “non-inverting amplifier.”




## Op Amp circuits (linear region)

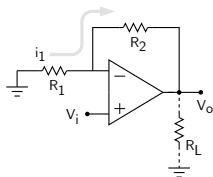


- \*  $V_+ \approx V_- = V_i$   
 $\rightarrow i_1 = (0 - V_i)/R_1 = -V_i/R_1$ .
- \*  $V_o = V_+ - i_1 R_2 = V_i - \left(-\frac{V_i}{R_1}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right)$ .
- \* This circuit is known as the “non-inverting amplifier.”
- \* Again, interchanging + and - changes the nature of the feedback from negative to positive, and the circuit operation becomes completely different.



# Inverting or non-inverting?

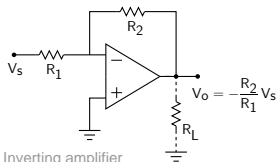

Inverting amplifier




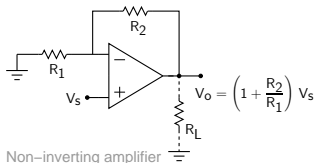


Non-inverting amplifier

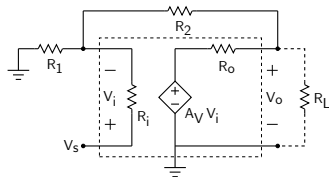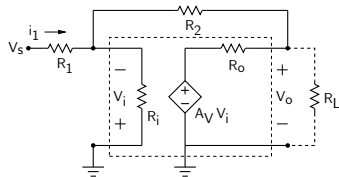





- \* If the sign of the output voltage is not a concern, which configuration should be preferred?

# Inverting or non-inverting?

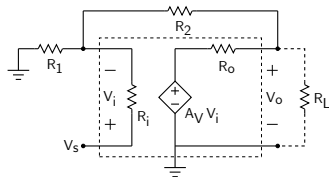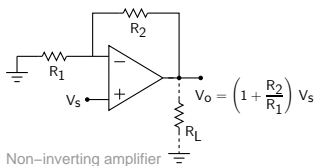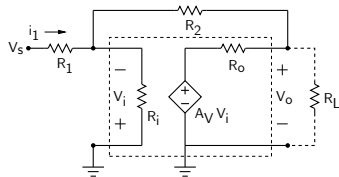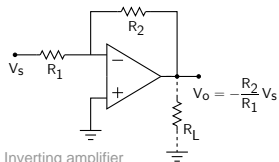


- \* If the sign of the output voltage is not a concern, which configuration should be preferred?
- \* For the inverting amplifier, since  $V_- \approx 0\text{ V}$ ,  $i_1 = V_s/R_1 \rightarrow R_{in} = V_s/i_1 = R_1$ .

# Inverting or non-inverting?

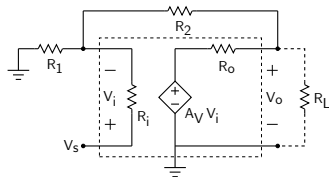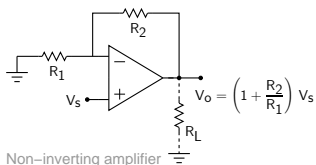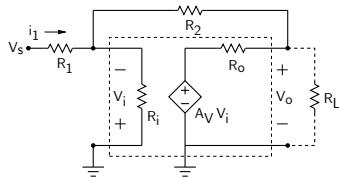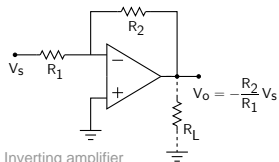


- \* If the sign of the output voltage is not a concern, which configuration should be preferred?
- \* For the inverting amplifier, since  $V_- \approx 0\text{ V}$ ,  $i_1 = V_s/R_1 \rightarrow R_{in} = V_s/i_1 = R_1$ .
- \* For the non-inverting amplifier,  $R_{in} \sim R_i$  of the Op Amp, which is a few  $\text{M}\Omega$ .  
 → Non-inverting amplifier is better if a large  $R_{in}$  is required.

# Non-inverting amplifier

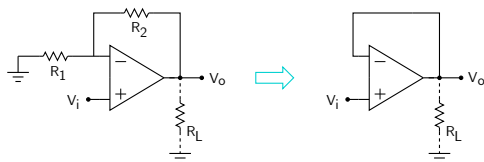

Consider  $R_1 \rightarrow \infty$ ,  $R_2 \rightarrow 0$ .


# Non-inverting amplifier

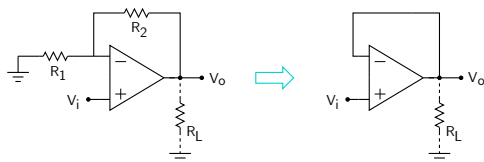

Consider  $R_1 \rightarrow \infty$ ,  $R_2 \rightarrow 0$ .

$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

## Non-inverting amplifier

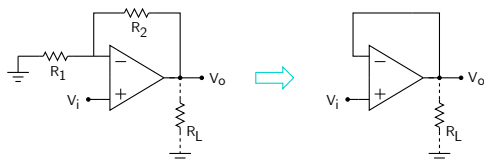


Consider  $R_1 \rightarrow \infty$ ,  $R_2 \rightarrow 0$ .

$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

This circuit is known as unity-gain amplifier/voltage follower/buffer.

## Non-inverting amplifier

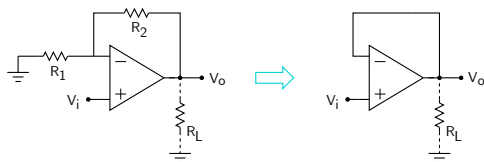

Consider  $R_1 \rightarrow \infty$ ,  $R_2 \rightarrow 0$ .


$$\frac{V_o}{V_i} \rightarrow 1 + \frac{R_2}{R_1} \rightarrow 1, \text{ i.e., } V_o = V_i.$$

This circuit is known as unity-gain amplifier/voltage follower/buffer.

What has been achieved?




## Loading effects

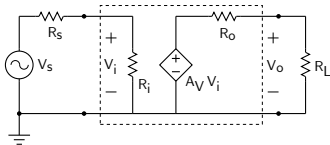

Consider an amplifier of gain  $A_V$ . We would like to have  $V_o = A_V V_s$ .

## Loading effects

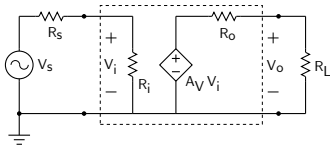


Consider an amplifier of gain  $A_V$ . We would like to have  $V_o = A_V V_s$ .

However, the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} \times A_V V_i = A_V \times \frac{R_L}{R_o + R_L} \times \frac{R_i}{R_i + R_s} V_s.$$

## Loading effects

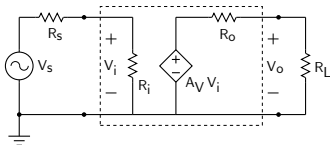


Consider an amplifier of gain  $A_V$ . We would like to have  $V_o = A_V V_s$ .

However, the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} \times A_V V_i = A_V \times \frac{R_L}{R_o + R_L} \times \frac{R_i}{R_i + R_s} V_s.$$

To obtain the desired  $V_o$ , we need  $R_i \rightarrow \infty$  and  $R_o \rightarrow 0$ .

## Loading effects

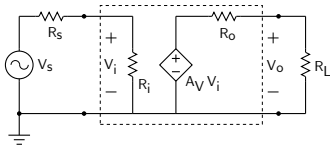

Consider an amplifier of gain  $A_V$ . We would like to have  $V_o = A_V V_s$ .


However, the actual output voltage is,

$$V_o = \frac{R_L}{R_o + R_L} \times A_V V_i = A_V \times \frac{R_L}{R_o + R_L} \times \frac{R_i}{R_i + R_s} V_s.$$

To obtain the desired  $V_o$ , we need  $R_i \rightarrow \infty$  and  $R_o \rightarrow 0$ .

The buffer (voltage follower) provides this feature (next slide).


# Op Amp buffer

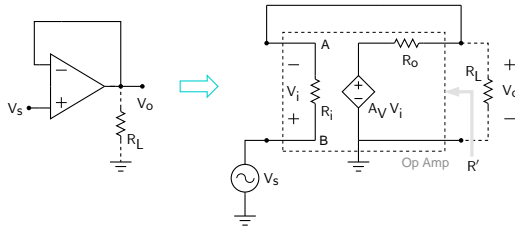

- \* The current drawn from the source ( $V_s$ ) is small (since  $R_i$  of the Op Amp is large)  $\rightarrow$  the buffer has a large input resistance.




# Op Amp buffer

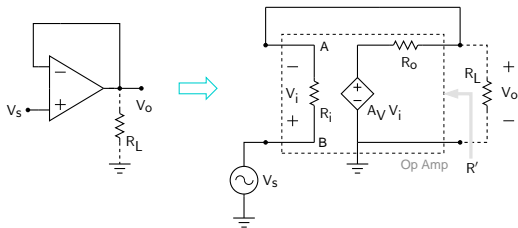


- \* The current drawn from the source ( $V_s$ ) is small (since  $R_i$  of the Op Amp is large)  $\rightarrow$  the buffer has a large input resistance.
- \* As we have seen earlier,  $A_V$  is large  $\rightarrow V_i \approx 0\text{ V} \rightarrow V_A = V_B = V_s$ .
- \* The resistance seen by  $R_L$  is  $R' \approx R_o$ , which is small  $\rightarrow$  the buffer has a small output resistance. (To find  $R'$ , deactivate the input voltage source ( $V_s$ )  $\rightarrow A_V V_i = 0\text{ V}$ .)

# Op Amp buffer

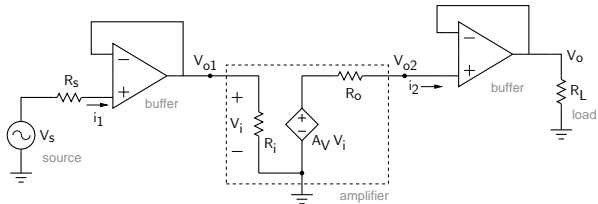




## Op Amp buffer

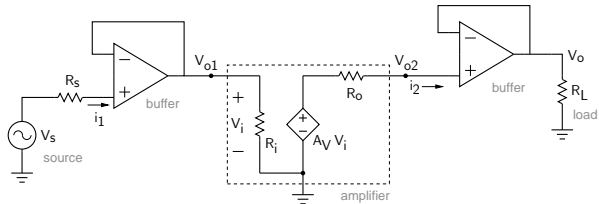

Since the buffer has a large input resistance,  $i_1 \approx 0$  A,  
and  $V_+$  (on the source side)  $= V_s \rightarrow V_{o1} = V_s$ .


## Op Amp buffer

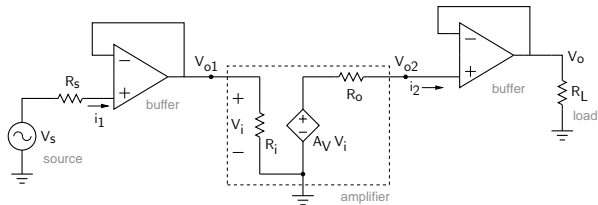

Since the buffer has a large input resistance,  $i_1 \approx 0\text{ A}$ ,  
and  $V_+$  (on the source side)  $= V_s \rightarrow V_{o1} = V_s$ .

Similarly,  $i_2 \approx 0\text{ A}$ , and  $V_{o2} = A_V V_s$ .

# Op Amp buffer

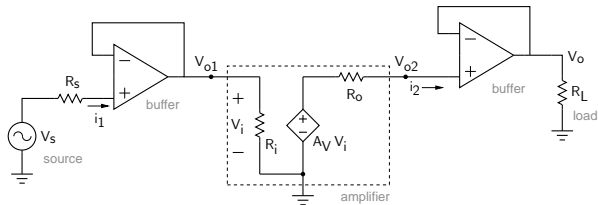


Since the buffer has a large input resistance,  $i_1 \approx 0\text{ A}$ ,

and  $V_+$  (on the source side)  $= V_s \rightarrow V_{o1} = V_s$ .


Similarly,  $i_2 \approx 0\text{ A}$ , and  $V_{o2} = A_V V_s$ .

Finally,  $V_o = V_{o2} = A_V V_s$ , as desired, *irresepective* of  $R_S$  and  $R_L$ .

## Op Amp circuits (linear region)

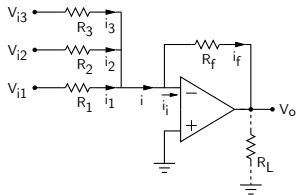


## Op Amp circuits (linear region)

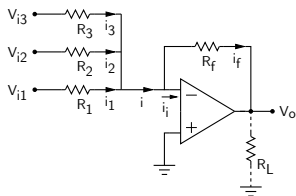

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$


## Op Amp circuits (linear region)

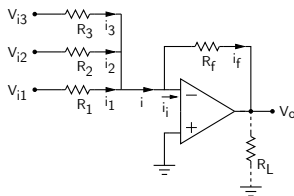

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

## Op Amp circuits (linear region)

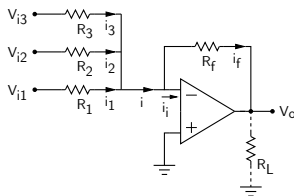


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Because of the large input resistance of the Op Amp,  $i_i \approx 0 \rightarrow i_f = i$ , which gives,

## Op Amp circuits (linear region)

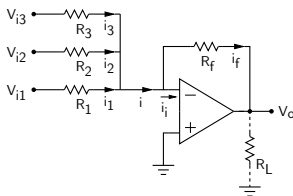

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$


Because of the large input resistance of the Op Amp,  $i_i \approx 0 \rightarrow i_f = i$ , which gives,

$$V_o = V_- - i_f R_f = 0 - \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right) R_f = - \left( \frac{R_f}{R_1} V_{i1} + \frac{R_f}{R_2} V_{i2} + \frac{R_f}{R_3} V_{i3} \right),$$

i.e.,  $V_o$  is a *weighted sum* of  $V_{i1}$ ,  $V_{i2}$ ,  $V_{i3}$ .



## Op Amp circuits (linear region)

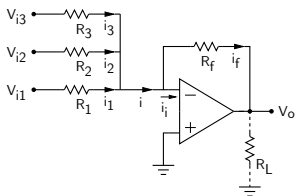

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_{i1}/R_1, i_2 = V_{i2}/R_2, i_3 = V_{i3}/R_3.$$

$$i = i_1 + i_2 + i_3 = \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right).$$

Because of the large input resistance of the Op Amp,  $i_i \approx 0 \rightarrow i_f = i$ , which gives,

$$V_o = V_- - i_f R_f = 0 - \left( \frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right) R_f = - \left( \frac{R_f}{R_1} V_{i1} + \frac{R_f}{R_2} V_{i2} + \frac{R_f}{R_3} V_{i3} \right),$$


i.e.,  $V_o$  is a *weighted sum* of  $V_{i1}$ ,  $V_{i2}$ ,  $V_{i3}$ .

If  $R_1 = R_2 = R_3 = R$ , the circuit acts as a summer, giving

$V_o = -K (V_{i1} + V_{i2} + V_{i3})$

 with  $K = R_f/R$ .


# Summer example

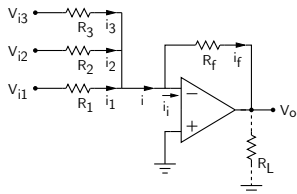


$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

$$R_f = 2 \text{ k}\Omega$$
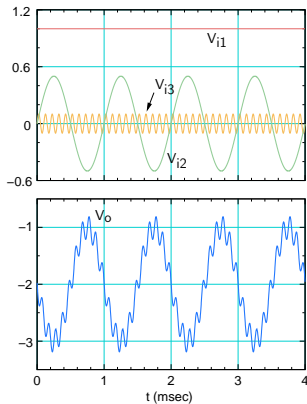
$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$




## Summer example

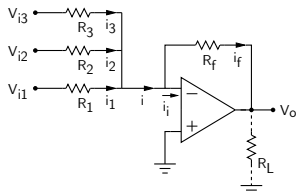

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$


$$R_f = 2 \text{ k}\Omega$$
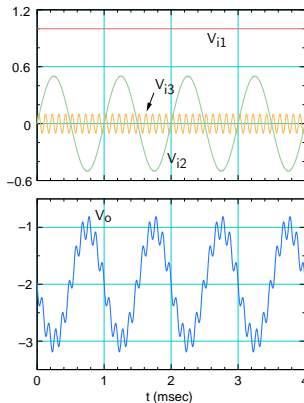
$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$



- \* Note that the summer also works with DC inputs. This is true about the inverting and non-inverting amplifiers as well.


## Summer example

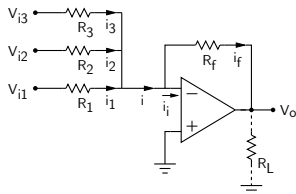

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$


$$R_f = 2 \text{ k}\Omega$$
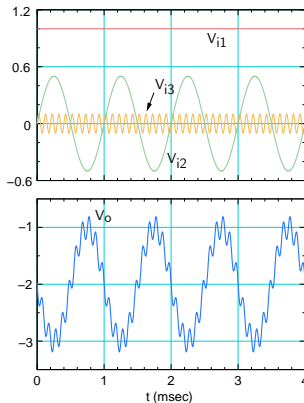
$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$



- \* Note that the summer also works with DC inputs. This is true about the inverting and non-inverting amplifiers as well.
- \* Op Amps make life simpler! Think of adding voltages in any other way.


## Summer example

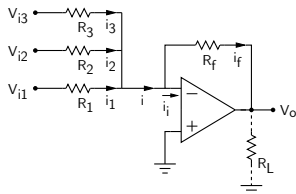

$$R_1 = R_2 = R_3 = 1 \text{ k}\Omega$$

$$R_f = 2 \text{ k}\Omega$$
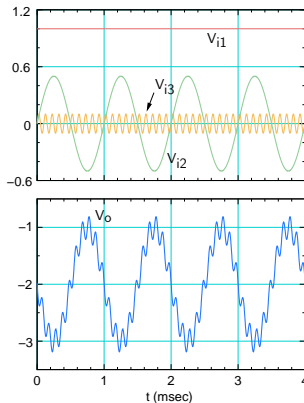
$$\rightarrow V_o = -2(V_{i1} + V_{i2} + V_{i3})$$



- \* Note that the summer also works with DC inputs. This is true about the inverting and non-inverting amplifiers as well.
- \* Op Amps make life simpler! Think of adding voltages in any other way.

(SEQUEL file: ee101\_summer.sqproj)