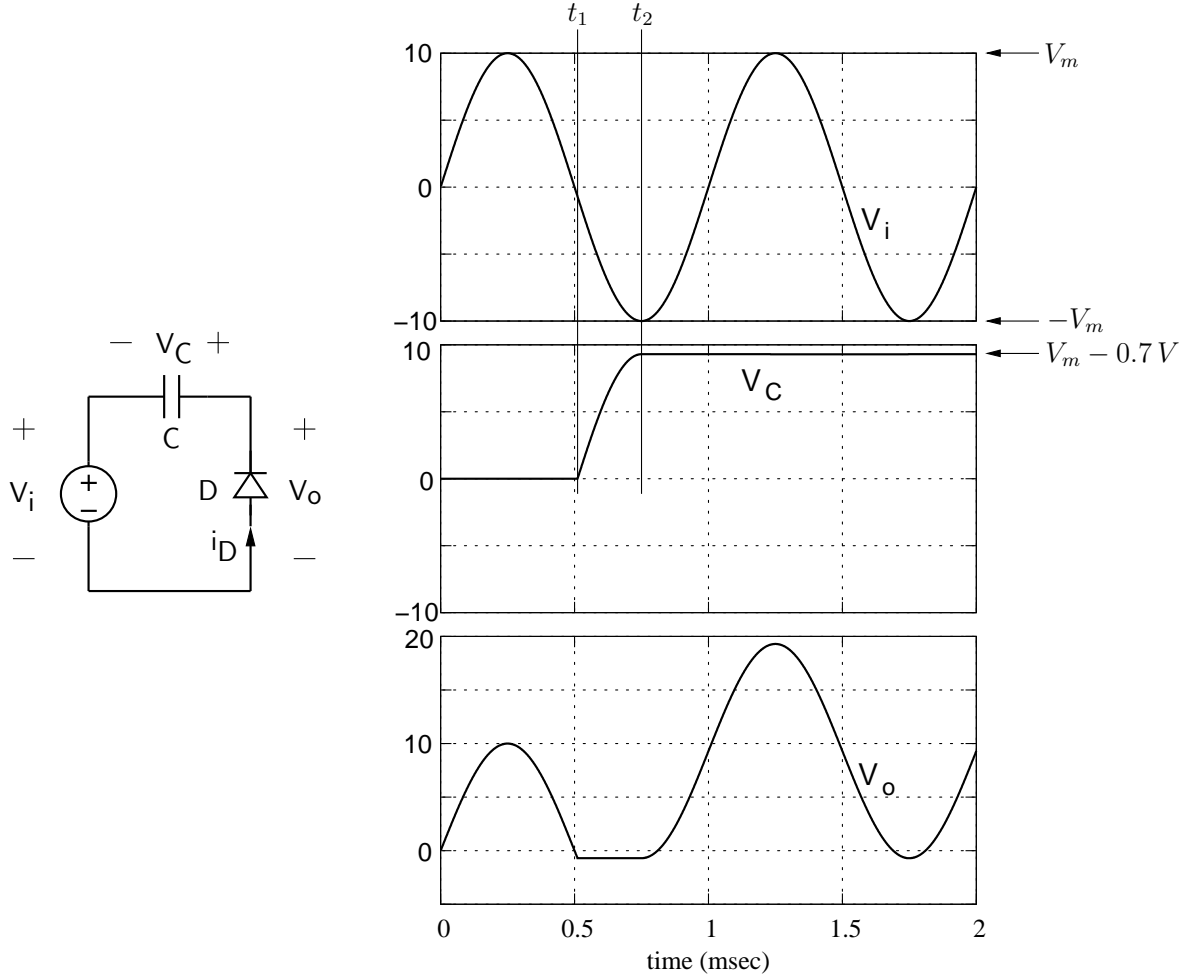


ee101_diode_circuit_6.sqproj

Description



In the circuit shown in the figure, let V_C be 0 V at $t=0$, and V_D , the diode on voltage, be 0.7 V. Up to time t_1 , the diode does not conduct, and the capacitor voltage remains at 0 V. At $t=t_1$, the diode starts conducting, and the capacitor charges. The charging process is instantaneous because of the very small diode resistance. In other words, $V_C(t) = -V_i(t) + 0.7$ V. At $t=t_2$, V_C has reached its maximum value. The capacitor subsequently holds this voltage since any decrease in V_C would require the diode to conduct in the reverse direction, which is not possible. As a result, beyond $t=t_2$, we have

$$V_o(t) = V_i(t) + V_C(t) = V_m \sin \omega t + (V_m - 0.7), \quad (1)$$

i.e., the output voltage gets clamped at a minimum value of -0.7 V .

Exercise Set

1. Simulate the circuit and observe the V_C and V_o waveforms along with V_i for $C = 1\text{ }\mu\text{F}$, $V_m = 10\text{ V}$, $f = 1\text{ kHz}$.
2. How will the waveforms change if C is decreased by a factor of 2? Increased by a factor of 2?
3. How will the waveforms change if the input voltage V_i has an offset voltage of 5 V ? An offset voltage of -5 V ?

Verify your answers with simulation.