

# ic555b.sqproj

## Description

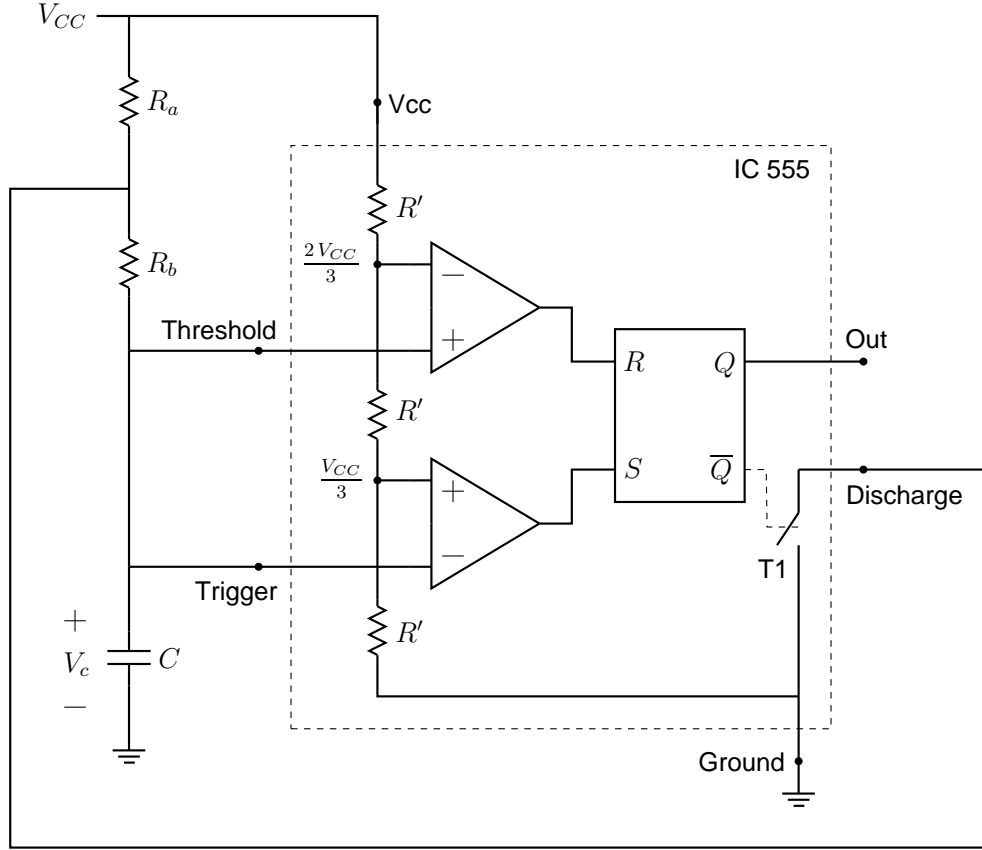


Figure 1: Astable operation of the 555 timer.

The purpose of the astable circuit shown in Fig. 1 is to produce oscillations whose frequency can be controlled by  $R_a$ ,  $R_b$ , and  $C$ . The trigger and threshold inputs are tied together in this circuit, and we have  $V_{\text{trigger}} = V_{\text{threshold}} = V_c$ . The circuit operation can be understood by realizing that the following conditions hold:

$V_{CC}/3 < V_c(t) < 2V_{CC}/3$	$R = 0, S = 0$	flip-flop holds its state.
$V_c(t) < V_{CC}/3$	$R = 0, S = 1$	flip-flop is set ( $Q = 1$ ).
$V_c(t) > 2V_{CC}/3$	$R = 1, S = 0$	flip-flop is reset ( $Q = 0$ ).

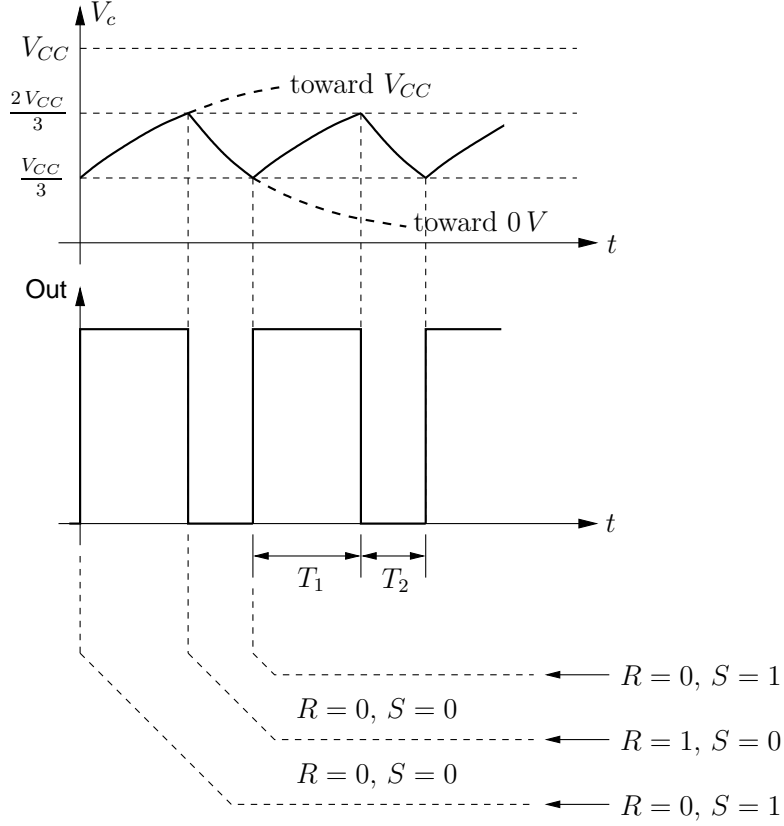


Figure 2: Waveforms for astable operation of the 555 timer.

Consider the interval marked  $T_1$  in Fig. 2. During this time,  $Q = 1$ , the switch T1 is open, and the capacitor charges toward  $V_{CC}$  through  $(R_a + R_b)$ . However, as soon as  $V_c$  reaches  $2V_{CC}/3$ ,  $R$  becomes 1 ( $S$  is still 0), and the flip-flop gets reset to  $Q = 0$ .

When  $Q$  becomes 0,  $\bar{Q}$  becomes 1, and the switch T1 closes. The capacitor now starts discharging toward  $0V$  through  $R_b$ . However, when  $V_c$  crosses  $V_{CC}/3$ ,  $S$  becomes 1 ( $R$  is still 0), and the flip-flop gets set to  $Q = 1$ , bringing us back to the  $T_1$  phase. The output keeps oscillating between 0 and 1, as shown in Fig. 2.

The intervals  $T_1$  and  $T_2$  can be computed using the limits  $V_{CC}/3$ ,  $S$ ,  $2V_{CC}/3$ ,  $S$  on  $V_c(t)$  and the appropriate time constants ( $\tau_1 = (R_a + R_b)C$  during the charging phase, and  $\tau_2 = R_b C$  during the discharging phase). The result is,

$$T_1 = (R_a + R_b)C \ln 2, \quad (1)$$

$$T_2 = R_b C \ln 2. \quad (2)$$

## Exercise Set

1. For  $R_a = 0.5 \text{ k}\Omega$ ,  $R_b = 0.5 \text{ k}\Omega$ , and  $C = 0.5 \mu\text{F}$ , calculate  $T_1$  and  $T_2$ . Verify by simulation.
2. By simulation, obtain waveforms for  $V_c$  and  $Q$ . Compare with the expected waveforms shown in Fig. 2.
3. How will you make the output waveform nearly symmetric (i.e.,  $T_1 \approx T_2$ )? Verify by simulation.